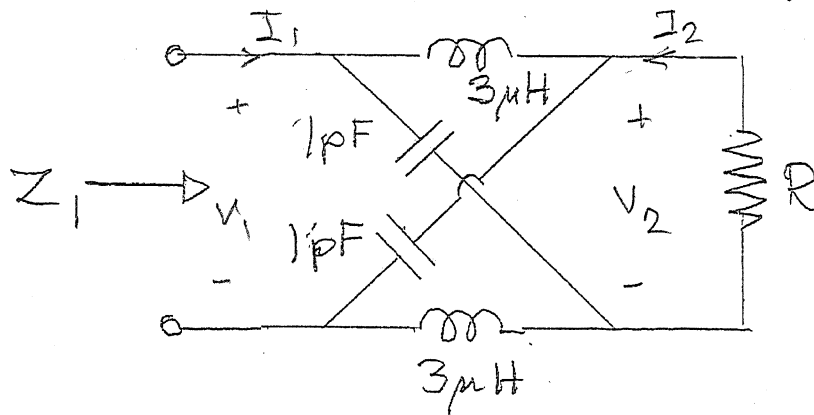


1. In the terminated two-port shown below, the input impedance is Z_1 .

a. At what frequencies is $Z_1 = R$ for all values of R ?

b. For what value of R does $Z_1 = R$ hold at all frequencies? Why?




$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$V_2 = -I_2 R$$
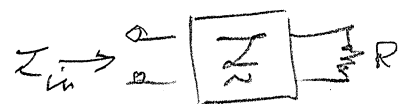
$$Z_1 = \frac{V_1}{I_1} = z_{11} - \frac{z_{12} z_{21}}{z_{22} + R}$$



$$1. \quad z_{11} = \frac{1}{2} \left[\frac{1}{sC} + sL \right] = z_{22}$$

$$z_{12} = \frac{1}{2} \left[\frac{1}{sC} - sL \right] = z_{21} \quad \text{reciprocal}$$

$$Z_1 = z_{11} - \frac{z_{12} z_{21}}{z_{22} + R} = R \left(\frac{z_{11} + (L/C)/R}{z_{11} + R} \right)$$

a. By inspection, $z_{11} \rightarrow \infty$ for $s = 0$ or $s \rightarrow \infty$, so $Z_1 \rightarrow R$ for $f = 0, \infty$

b. If $(L/C)/R = R$, or $L/C = R^2$,


$$Z_1(s) = R \quad \forall s, \quad R \approx 1.732 \text{ k}\Omega$$

Or


$$b. \quad R = z_{11} - \frac{z_{12}^2}{z_{11} + R}, \quad R - z_{11} = -\frac{z_{12}^2}{R + z_{11}}$$

$$R^2 - z_{11}^2 = -z_{12}^2, \quad R^2 = sL \cdot 1/sC = L/C$$

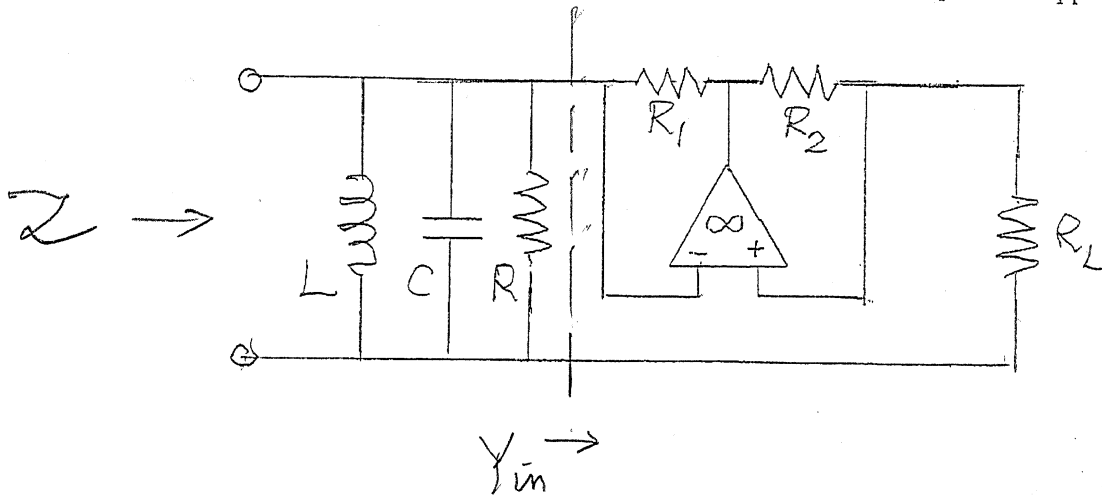2. What is the input impedance of the circuit shown below? What are its possible applications?



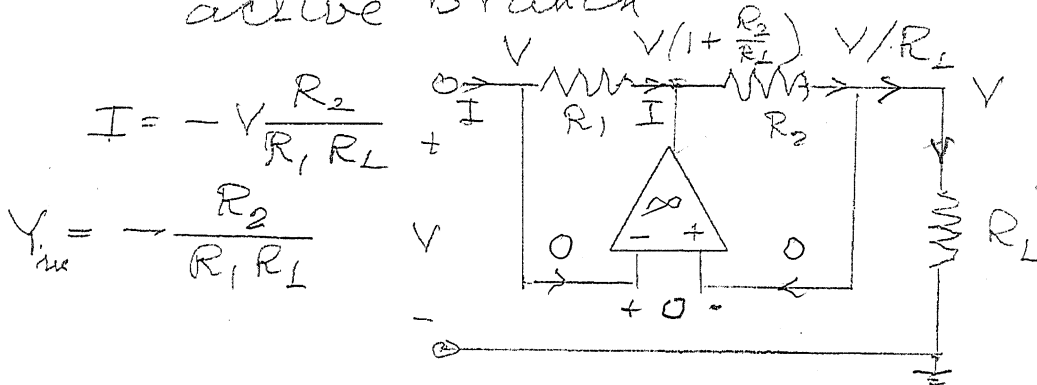2. The input admittance of the active branch



Riordan

$$Y_{in} = -\frac{R_2}{R_1 R_L}$$


Negative conductance may cancel $1/R \rightarrow$ oscillator, high-Q filter

Overall

$$Z_1 = \frac{1}{1/sL + sC + 1/R - R_2/(R_1 R_L)}$$

Q booster, oscillator

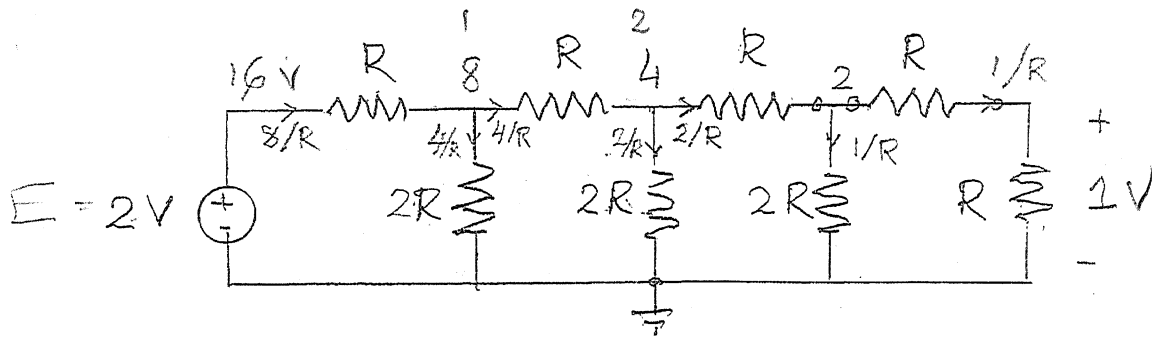3. (Extra credit) Find all node voltages in the circuit shown below.



$$1 \rightarrow 2/16 = 1/8 \text{ V}$$

So the node voltages are

$$2, 1, 0.5, 0.25 \text{ and } 0.125 \text{ V}$$

Or: Resistance after node = $2R$
 before " " = R

So, at second node, $V_2 = V_1/2 = E/2$,
 at 3rd node, $V_3 = E/4$, etc.

R-2R DAC!