


FINAL EXAMINATION
December 7, 18:00-19:50 pm

OPEN BOOK - ALL PROBLEMS EQUALLY WEIGHTED


Prof. G. Temes

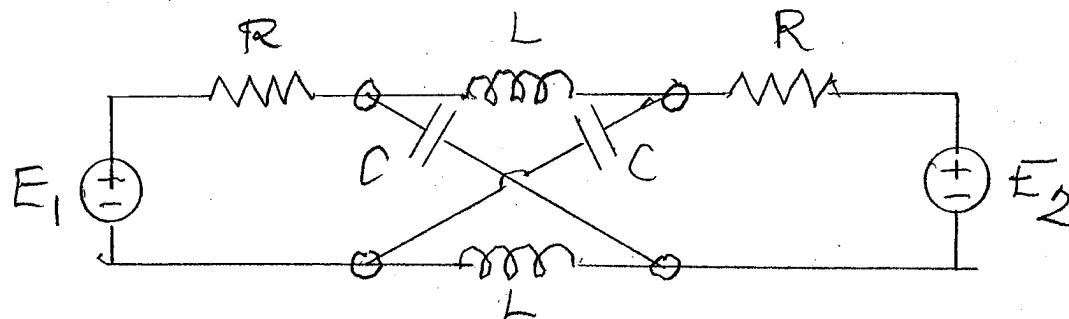1. For the terminated two-port shown, $L = 1 \mu\text{H}$ and $C = 4 \text{ pF}$. The scattering parameter S_{11} is equal to 0 for all frequencies.


- What are the impedance parameters z_{ij} of the twoport? What is the value of R ?
- What are the absolute values of the other three scattering parameters? Why?
- Derive $S_{12}(s)$ and $S_{21}(s)$!



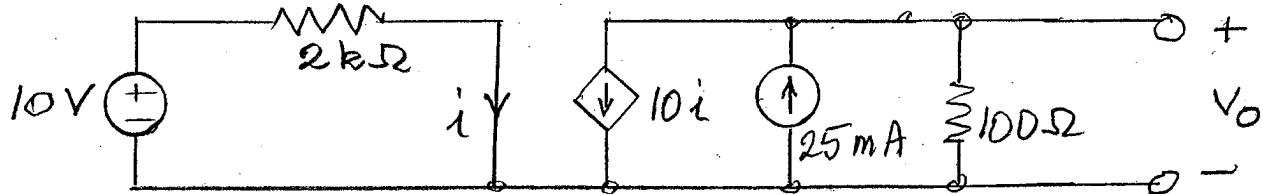2. Find the Thevenin equivalent of the circuit shown using the adjoint network method.



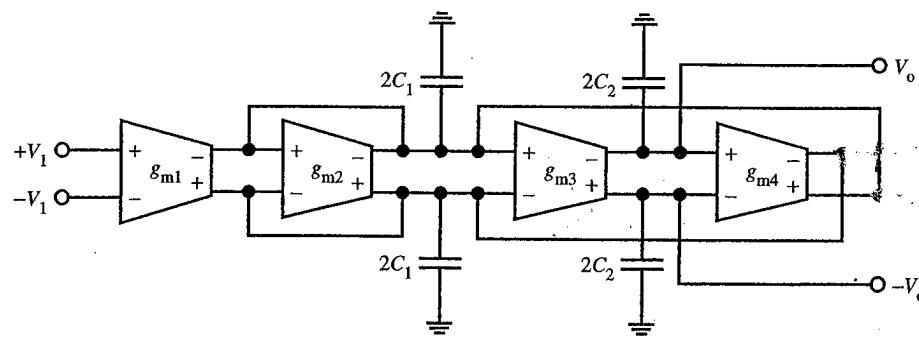3. Find the transfer function of the filter shown.



1.a.

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = -R I_2 = z_{21} I_1 + z_{22} I_2 \rightarrow I_2 = \frac{-z_{21} I_1}{z_{22} + R}$$


$$V_1 = I_1 \left[z_{11} - \frac{z_{12} z_{21}}{z_{22} + R} \right] = z_{in} I_1$$

$$z_{in} = \frac{z_{11}^2 - z_{12}^2 + R z_{11}}{z_{11} + R} = R$$

$$z_{11}^2 - z_{12}^2 = R^2 = (z_{11} + z_{12})(z_{11} - z_{12})$$

$$z_{11} = \frac{z_A + z_B}{2}, \quad z_{21} = z_{11} \frac{z_B - z_A}{z_B + z_A} = \frac{z_B - z_A}{2}$$
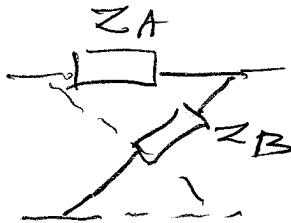
$$R^2 = z_A z_B = \frac{sL}{sC} = \frac{L}{C} \rightarrow R = \sqrt{\frac{L}{C}} = 500 \Omega$$



$$z_{11} = \frac{s^2 LC + 1}{2sC} = z_{22}$$

$$z_{12} = \frac{1 - s^2 LC}{2sC} = z_{21}$$

$$z_{11}, z_{12} = \frac{1 \pm 4 \cdot 10^{-18} s^2}{8 \times 10^{-12} s}$$

b. By symmetry, $S_{22} = 0$.

Since both ports are matched, and twoport is lossless, $|S_{12}| = |S_{21}| = 1$,

B

1. c

$$Z_{11} = Z_{22} = \frac{Z_A + Z_B}{2}$$

$$Z_{12} = Z_{21} = \frac{Z_B - Z_A}{Z_B + Z_A} Z_{11} = \frac{Z_B - Z_A}{2}$$

$$V_1 = \frac{E_1}{2} = Z_{11} \frac{E_1}{2R} - Z_{12} \frac{V_2}{R}$$

$$V_2 \frac{Z_{12}}{R} = \frac{E_1}{2R} [Z_{11} - R]$$

$$S_{21} = \frac{\frac{V_2}{R}}{\frac{E_1/2}{R}} = \frac{Z_{11} - R}{Z_{12}} = \frac{Z_A + Z_B - 2R}{Z_B - Z_A} = S_{12}$$


$$= \frac{sL + 1/sC - \sqrt{LC}}{1/sC - sL} = \frac{s^2LC - 2s\sqrt{LC} + 1}{1 - s^2LC}$$

$$S_{12} = \frac{(s\sqrt{LC} - 1)^2}{(1+sT)(1-sT)} = \frac{1-sT}{1+sT} \quad T \triangleq \sqrt{LC}$$

$$T = 2\pi$$

$$|S_{21}(j\omega)| = \left| \frac{1-j\omega T}{1+j\omega T} \right| = 1 \quad \forall \omega$$

2. The adjoint network is

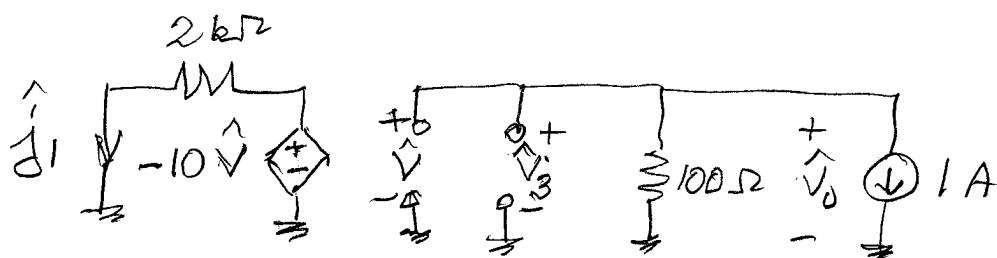


$$\hat{V} = \hat{V}_3 = \hat{V}_o = -100 \text{ V} \quad , \quad \hat{j}_1 = \frac{+10 \times 100}{2000} = +0.5 \text{ A}$$


$$V_o = -\hat{j}_1 e + \hat{V}_3 i = -0.5 \times 10 + (-100)(-0.025) = -2.5 \text{ V}$$

(From eq. 9-87)
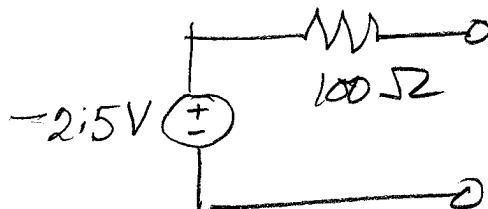
$$Z_{Th} = Z_{Th} = -\hat{V}_o = 100 \Omega$$



Easy to check from \mathcal{W} !

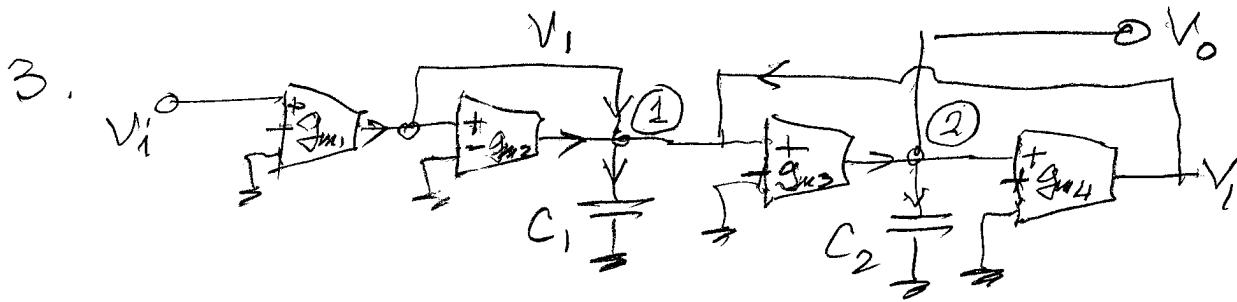

KCL @ ① :

$$-g_{m1}V_i - g_{m2}V_1 + g_{m4}V_o = sC_1 V$$

$$V_1 = (g_{m4}V_o - g_{m1}V_i) / (sC_1 + g_{m2})$$

KCL @ ②

$$-g_{m3}V_1 = sC_2 V_o$$

$$g_{m4}V_o - g_{m1}V_i = (sC_1 + g_{m2}) \frac{sC_2}{-g_{m3}} V_o$$

$$[g_{m3}g_{m4} + (sC_1 + g_{m2})sC_2] V_o = g_{m1}g_{m3}V_i$$

$$\frac{V_o}{V_i} = g_{m1}g_{m3} / (s^2C_1C_2 + s g_{m2}C_2 + g_{m3}g_{m4})$$