

$$T = RC$$

$$\frac{V}{V_{in}} = \frac{1}{1 + ST}$$

$$\frac{V^-}{V_{in}} = \frac{ST}{1 + ST}$$

$$\frac{V^+ - V^-}{V_{in}} = \frac{-1 + j\omega T}{1 + j\omega T}$$

$$\frac{V^+}{V_{in}}$$

$$\frac{V^-}{V_{in}}$$

$$H(s) = -2 \tan^{-1}(\omega T)$$

$$H \approx 2\omega T, \quad T_{gr} \approx T_p \approx 2T \approx 2RC$$

$$|H| \equiv 1$$

$$\frac{dLH}{dw} = -2T$$

2. Gyrator:  $\underline{J}$

$$V_1 = -RI_2$$

$$V_1 = AV_2 - BI_2$$


$$V_2 = RI_1$$

$$I_1 = CV_2 - DI_2$$

Hence  $A = 0, B = R$

$$C = 1/R, D = 0$$
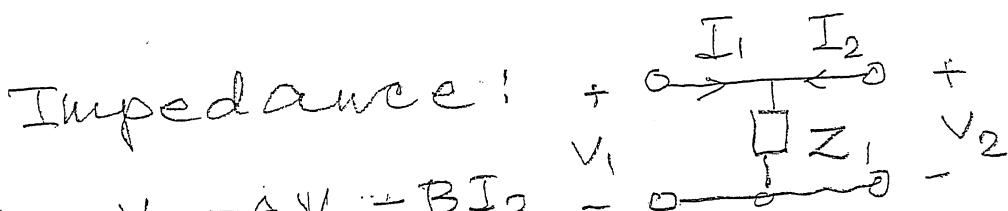
$$\underline{J} = \begin{bmatrix} 0 & R \\ 1/R & 0 \end{bmatrix}$$



$$V_1 = V_2 = AV_2 - BI_2$$



$$I_1 = V_2/Z_1 - I_2 = CV_2 - DI_2$$

$$A_i = 1, B_i = 0$$

$$C_i = 1/Z_1, D_i = 1 : \quad \underline{J}_{\text{imp}} = \begin{bmatrix} 1 & 0 \\ VZ_1 & 1 \end{bmatrix}$$

$$\underline{J}_1 = \underline{J} \underline{J}_{\text{imp}} \underline{J} = \begin{bmatrix} 1 & R^2/Z_1 \\ 0 & 1 \end{bmatrix}$$
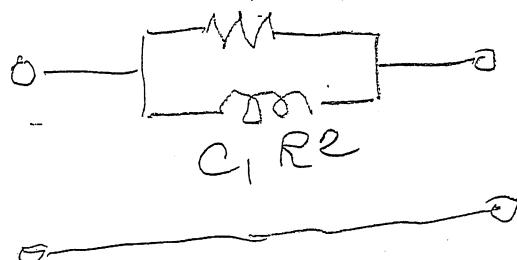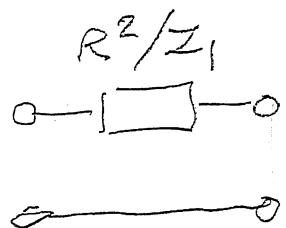
$$Z_1 \rightarrow \infty, Y_1 = \frac{Z_1}{R^2} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$




3

ECE 580


## MIDTERM EXAMINATION

October 24, 2018


1. a. Find the voltage ratio  $V_2/V_1$  of the lattice two-port shown.  
 b. Calculate the gain  $|V_2/V_1|$  and the phase shift between  $V_2$  and  $V_1$  as functions of  $\omega$ .

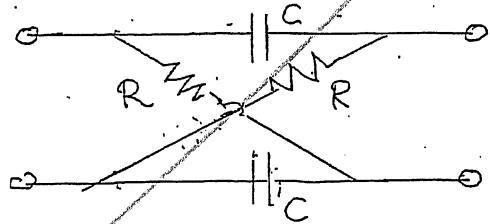

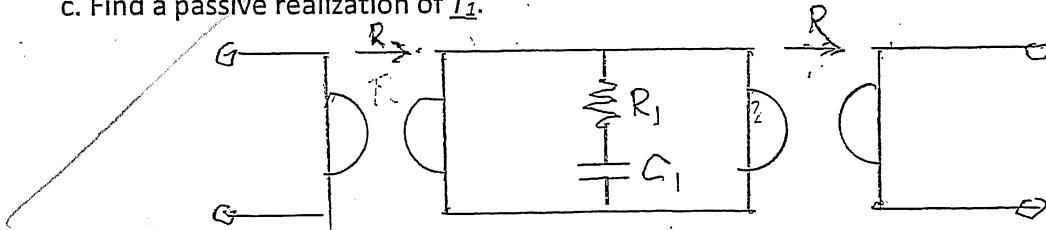2. a. Find the chain matrix  $T$  of a gyrator with gyration resistance  $R$ .  
 b. Use your result to find the chain matrix  $T_1$  of the two-port shown below.  
 c. Find a passive realization of  $T_1$ .



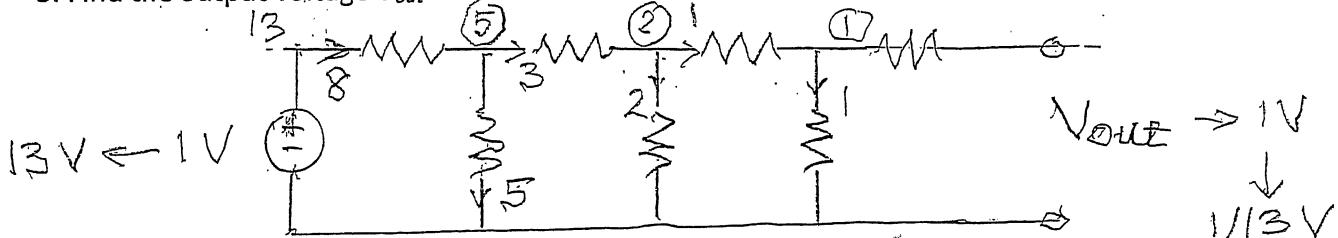3. Find the output voltage  $V_{out}$  of the ladder shown below. All resistors are  $1 \text{ k}\Omega$ .



4. (Extra credit) A two-port  $T_a$  has a hybrid matrix  $H_a$  and another one  $T_b$  has a hybrid matrix  $H_b$ .
- Show how the matrices should be interconnected so that resulting two-port has a hybrid matrix  $H_a + H_b$ .
  - Derive a test which indicates whether the interconnection gives the correct result.

(4) We need

$$\underline{\underline{y}} = \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} H_a & H_b \\ H_a & H_b \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \underline{\underline{H}} \underline{\underline{x}}$$

$$y_a = H_a x_a$$


$$y_b = H_b x_b$$

If  $x_a = x_b \rightarrow I_{1a} = I_{1b}$  and  $V_{2a} = V_{2b}$

and  $\underline{\underline{y}} = \underline{\underline{y}}_a + \underline{\underline{y}}_b \rightarrow V_1 = V_{1a} + V_{1b}$  and  
 $I_2 = I_{2a} + I_{2b}$

then  $\underline{\underline{H}} = \underline{\underline{H}}_a + \underline{\underline{H}}_b$ .

Hence

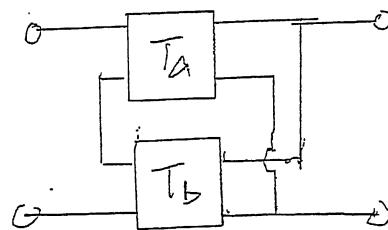

Tests

