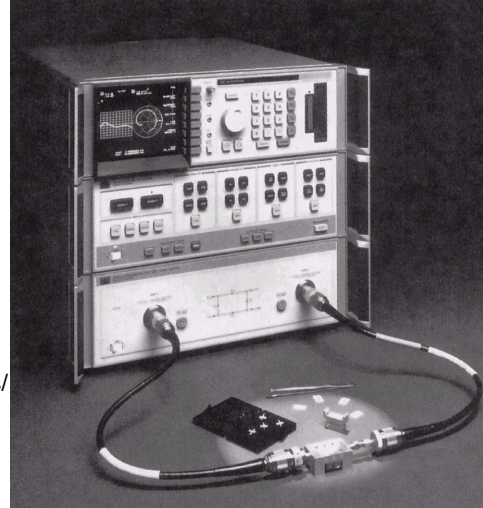


Scattering Parameters

Motivation


- Difficult to implement open and short circuit conditions in high frequencies measurements due to parasitic L 's and C 's
- Potential stability problems for active devices when measured in non-operating conditions
- Difficult to measure V and I at microwave frequencies
- Direct measurement of amplitudes/ power and phases of incident and reflected traveling waves



Scattering Parameters

Motivation


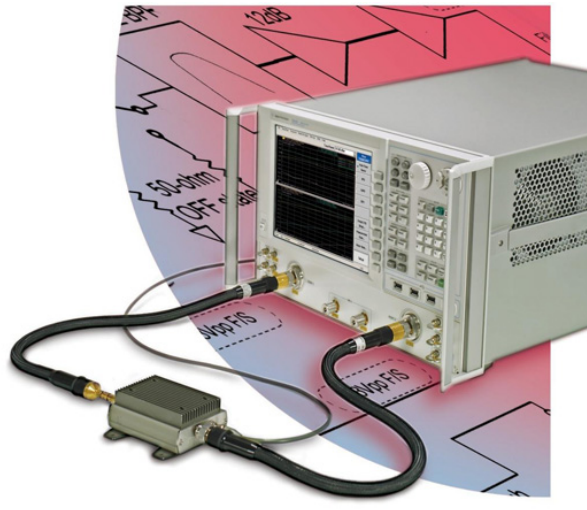
- Difficult to implement short circuit condition frequencies measure parasitic L 's and C 's
- Potential stability problems for active devices when non-operating conditions
- Difficult to measure V and I at microwave frequencies
- Direct measurement of power and phases of reflected traveling waves



General Network Formulation

Port Voltages and Currents
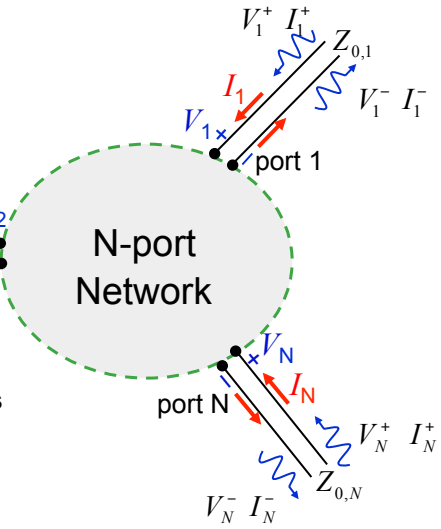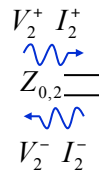
$$V_k = V_k^+ + V_k^- \quad I_k = I_k^+ + I_k^-$$




Characteristic (Port) Impedances

$$Z_{0,k} = \frac{V_k^+}{I_k^+} = -\frac{V_k^-}{I_k^-}$$

Note: all current components are defined positive with direction into the positive terminal at each port

Impedance Matrix

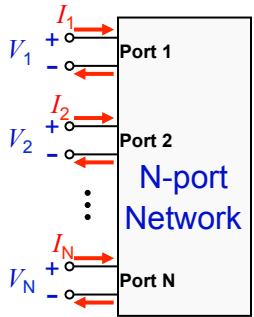


$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix}$$


$$[V] = [Z][I]$$

Open-Circuit Impedance Parameters
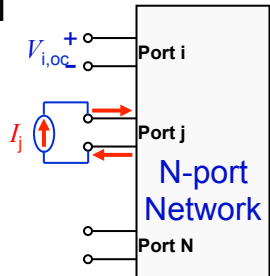
$$Z_{ij} = \frac{V_{i,oc}}{I_j} \quad I_k = 0 \text{ for } k \neq j$$



Admittance Matrix

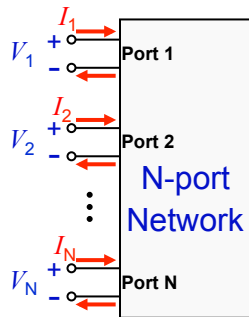


$$\begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} & \cdots & Y_{1N} \\ Y_{21} & Y_{22} & \cdots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \cdots & Y_{NN} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{bmatrix}$$

$$[I] = [Y][V]$$

Short-Circuit Admittance Parameters

$$Y_{ij} = \frac{I_{i,sc}}{V_j} \quad \left| \quad V_k = 0 \text{ for } k \neq j \right.$$

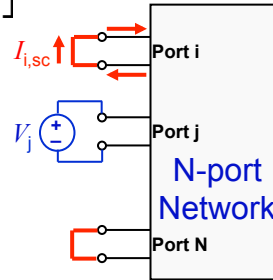


The Scattering Matrix

The scattering matrix relates incident and reflected voltage waves at the network ports as (assume $Z_{0,n} = Z_0$):

$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & S_{22} & \cdots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix} \quad \text{or} \quad [V^-] = [S][V^+]$$

with voltage and current at port n :
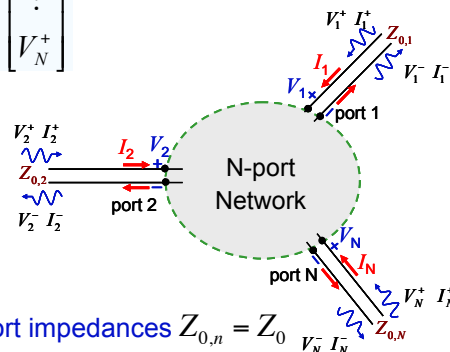
$$\begin{aligned} V_n &= V_n^+ + V_n^- \\ I_n &= I_n^+ - I_n^- \\ &= (V_n^+ - V_n^-) / Z_0 \end{aligned}$$



Note: S-parameters depend on port impedances $Z_{0,n} = Z_0$


The Scattering Matrix

The scattering matrix relates incident and reflected voltage waves at the network ports as (assume $Z_{0,n} = Z_0$):

$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & S_{22} & \cdots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix} \quad \text{or} \quad [V^-] = [S][V^+]$$

with $V_n = (v_n - v_n^-) / Z_0$


Interpretation?
Power relationships?

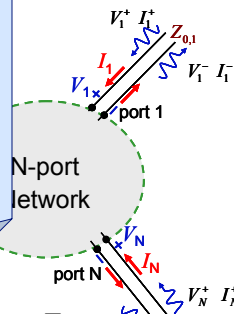

Note: S-parameters depend on port impedances $Z_{0,n} = Z_0$

Transmission Line Basics

Lossless Transmission Line

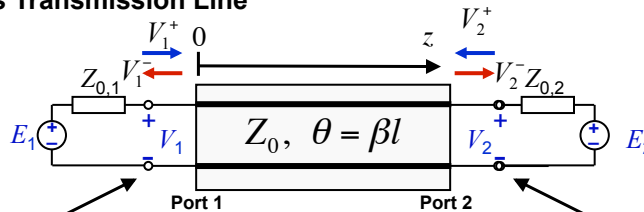

$$\begin{aligned} V_1 &= V_1^+ + V_1^- \\ I_1 &= I_1^+ + I_1^- \end{aligned}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$


$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

$$\begin{aligned} V_2 &= V_2^+ + V_2^- \\ I_2 &= I_2^+ + I_2^- \end{aligned}$$

Phase Constant: $\beta = \omega \sqrt{LC}$

Characteristic Impedance: $Z_0 = \sqrt{\frac{L}{C}} = \frac{V_0^+}{I_0^+} = -\frac{V_0^-}{I_0^-}$

Net Power Flow on Lossless Line

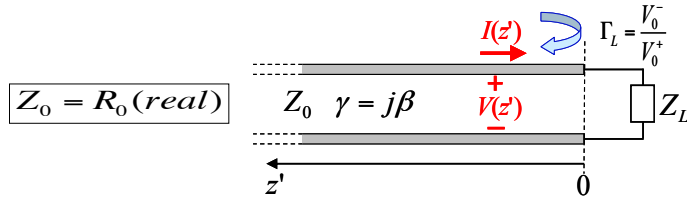


$$V(z') = V_0^+ (e^{+j\beta z'} + \Gamma_L e^{-j\beta z'})$$

$$I(z') = \frac{V_0^+}{Z_0} (e^{+j\beta z'} - \Gamma_L e^{-j\beta z'})$$

$$P_{\text{ave}}(z) = \frac{1}{2} \text{Re} \{ V(z) (I(z))^* \} = \frac{|V_0^+|^2}{2R_0} [1 - |\Gamma_L|^2] = \text{const.}$$

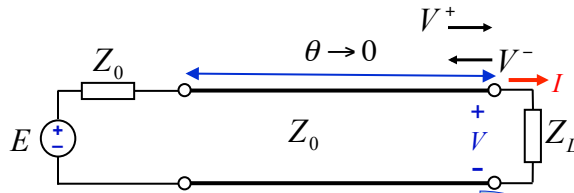Generalized Scattering Parameters considerations and definitions



$$V^+ = \frac{E}{2}$$

$$\Gamma = \frac{V^-}{V^+} = \frac{Z_L - Z_0}{Z_L + Z_0}$$


$$V = \frac{Z_L}{Z_L + Z_0} E = \frac{1}{2}(1 + \Gamma)E$$

$$V^+ = Z_0 I^+ \quad V^- = -Z_0 I^-$$

$$V = V^+ + V^- \quad I = I^+ + I^-$$

$$V^+ = \frac{1}{2}(V + Z_0 I)$$

$$V^- = \frac{1}{2}(V - Z_0 I)$$

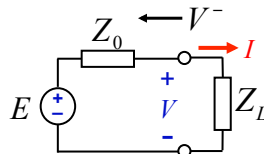

$$P^+ = \frac{1}{2} \text{Re} \{ V^+ (I^+)^* \} = \frac{1}{2} |V^+|^2 / R_0 = P_{\text{max}}$$


(assuming Z_0 is real $Z_0 = R_0$)

Normalized Wave Quantities

- It is useful to express power P **without** characteristic impedance (port impedance) $Z_0 = R_0$ (but P still depends on R_0)

$$P^+ = \frac{1}{2} \operatorname{Re}\{V^+ (I^+)^*\} = \frac{1}{2} |V^+|^2 / R_0 \quad \Rightarrow \quad a = \frac{V^+}{\sqrt{R_0}}$$


$$P^- = -\frac{1}{2} \operatorname{Re}\{V^- (I^-)^*\} = \frac{1}{2} |V^-|^2 / R_0 \quad \Rightarrow \quad b = \frac{V^-}{\sqrt{R_0}}$$

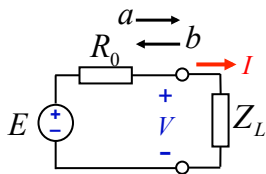

$$P_L = P^+ - P^- = \frac{|V^+|^2}{2R_0} - \frac{|V^-|^2}{2R_0} = \frac{1}{2} \{|a|^2 - |b|^2\}$$

(assuming real Z_0)

Scattering Matrix

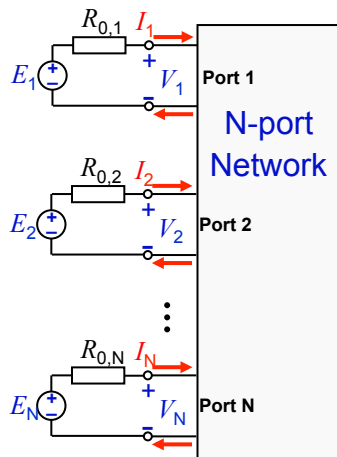

$$\begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & S_{22} & \cdots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ \vdots \\ a_N \end{bmatrix}$$

$$S_{ij} = \frac{b_i}{a_j} \Big|_{a_k=0 \text{ for } k \neq j}$$

$$S_{ij} = \frac{V_i^- / \sqrt{R_{0,i}}}{E_j / (2\sqrt{R_{0,j}})} \Big|_{E_k=0 \text{ for all } k \neq j} = \frac{V_i / \sqrt{R_{0,i}}}{E_j / (2\sqrt{R_{0,j}})} \Big|_{E_k=0 \text{ for all } k \neq j} \quad (i \neq j)$$

Scattering Parameters


Physical meaning of $|S_{ij}|^2$ ($Z_0 = R_0 = \text{real}$)

$$|S_{ij}|^2 = \frac{P_i^-}{P_{\max,j}} \Big|_{\substack{E_k=0 \\ k \neq j}} = \frac{\text{actual power leaving port } i}{\text{maximum power from port } j} \Big|_{\substack{E_k=0 \\ k \neq j}} \quad (i \neq j)$$

Physical meaning of $|S_{jj}|^2$

$$S_{jj} = \frac{b_j}{a_j} \Big|_{\substack{a_k=0 \\ k \neq j}} = \frac{V_j^- / \sqrt{R_{0,j}}}{V_j^+ / \sqrt{R_{0,j}}} = \frac{Z_{L,j} - R_{0,j}}{Z_{L,j} + R_{0,j}}$$

$$P_{L,j} = P_j^+ - P_j^- = P_{\max} \left\{ 1 - |S_{jj}|^2 \right\}$$

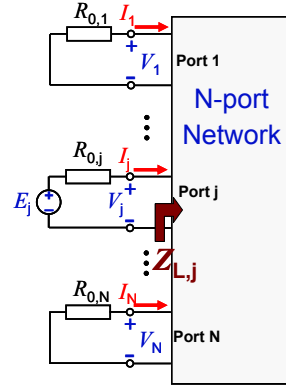

Relation to Z-Matrix

Impedance matrix:

$$\mathbf{V} = \mathbf{Z}\mathbf{I} \quad \text{with } \mathbf{Z} = \begin{bmatrix} Z_{11} & \cdots & Z_{1N} \\ \vdots & & \vdots \\ Z_{N1} & \cdots & Z_{NN} \end{bmatrix}$$

Express \mathbf{V}, \mathbf{I} in terms of \mathbf{a} and \mathbf{b}

$$\mathbf{R}_0^{1/2} (\mathbf{a} + \mathbf{b}) = \mathbf{Z} \mathbf{R}_0^{-1/2} (\mathbf{a} - \mathbf{b}) \quad \mathbf{b} = (\mathbf{Z}_n + \mathbf{U})^{-1} (\mathbf{Z}_n - \mathbf{U}) \mathbf{a}$$

with normalized impedance matrix $\mathbf{Z}_n = \mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2}$

($Z_0 = R_0 = \text{real}$)

$$\text{and port impedance matrix } \mathbf{R}_0^{1/2} = \begin{bmatrix} \sqrt{R_{0,1}} & 0 & 0 \\ 0 & \ddots & 0 \\ 0 & 0 & \sqrt{R_{0,N}} \end{bmatrix} \quad \mathbf{R}_0^{-1/2} = (\mathbf{R}_0^{1/2})^{-1}$$


$$\Rightarrow \mathbf{S} = (\mathbf{Z}_n + \mathbf{U})^{-1} (\mathbf{Z}_n - \mathbf{U}) = (\mathbf{Z}_n - \mathbf{U}) (\mathbf{Z}_n + \mathbf{U})^{-1}$$

Scattering Parameters

- Port n is said to be **matched** when it is terminated with a load having the same impedance as the port impedance $Z_{0,n}$.
- Often, all port impedances are chosen to be equal and $Z_{0,n} = 50 \Omega$.
- The values of the scattering (S-) parameters depend on the chosen port impedances.
- S-parameters can be algebraically renormalized to different and unequal port impedances. (see later)

Two-Port Networks

Insertion and Return Loss

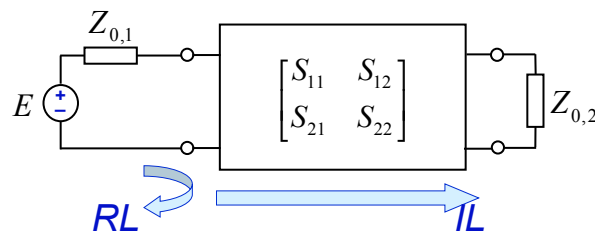

Return Loss

indicates the extent of mismatch in a network in dB

port 1: $RL = -20 \log_{10} |S_{11}|$ in dB


Insertion Loss

measure of transmitted fraction of power in dB

from port 1 to port 2: $IL = -20 \log_{10} |S_{21}|$ in dB

Example

Lossless Transmission Line:

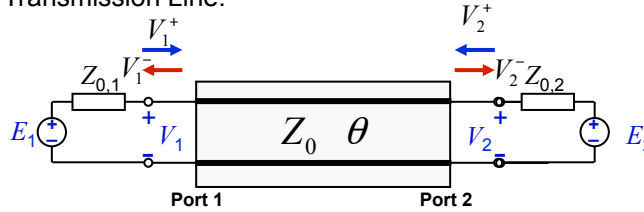

If $Z_{0,1} = Z_{0,2} = Z_0$, the scattering parameters can be easily obtained by inspection:

$$S_{11} = S_{22} = 0$$

$$S_{12} = S_{21} = e^{-j\theta}$$

$$[U] \pm [S] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \pm \begin{bmatrix} 0 & e^{-j\theta} \\ e^{-j\theta} & 0 \end{bmatrix}$$



$$[Z] = Z_0 ([U] + [S])([U] - [S])^{-1} =$$

$$([U] - [S])^{-1} = \begin{bmatrix} 1 & -e^{-j\theta} \\ -e^{-j\theta} & 1 \end{bmatrix}^{-1} = \frac{1}{1 - e^{-j2\theta}} \begin{bmatrix} 1 & e^{-j\theta} \\ e^{-j\theta} & 1 \end{bmatrix}$$


$$= \frac{Z_0}{1 - e^{-j2\theta}} \begin{bmatrix} 1 & e^{-j\theta} \\ e^{-j\theta} & 1 \end{bmatrix} \begin{bmatrix} 1 & e^{-j\theta} \\ e^{-j\theta} & 1 \end{bmatrix} =$$

$$= \frac{Z_0}{1 - e^{-j2\theta}} \begin{bmatrix} 1 + e^{-j2\theta} & 2e^{-j\theta} \\ 2e^{-j\theta} & 1 + e^{-j2\theta} \end{bmatrix} = \begin{bmatrix} -jZ_0 \cot \theta & -jZ_0 / \sin \theta \\ -jZ_0 / \sin \theta & -jZ_0 \cot \theta \end{bmatrix}$$

50Ω Transmission Line - 50Ω References

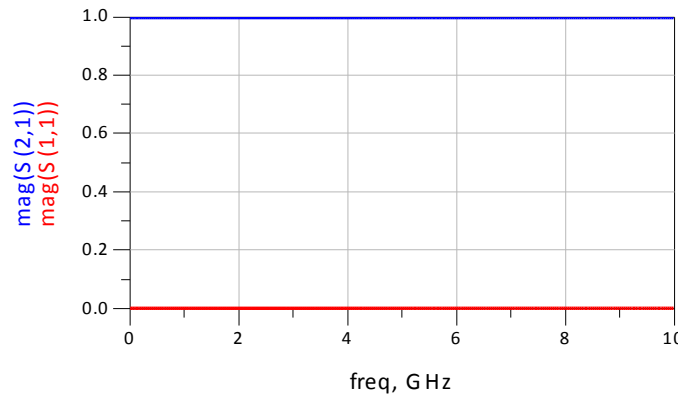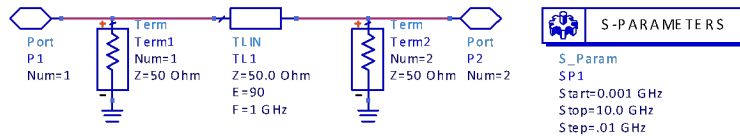

50Ω Transmission Line - 100Ω References

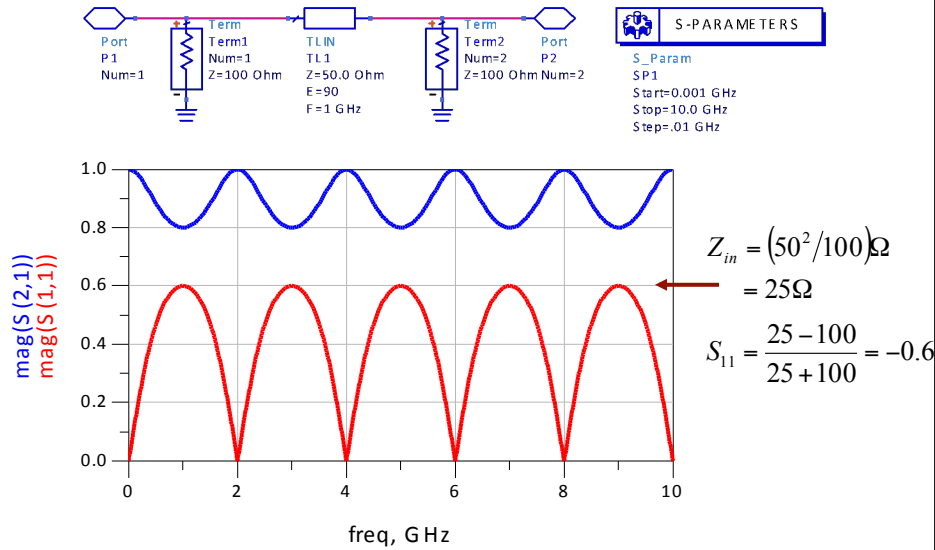

Properties of S-Parameters

Reciprocal networks:

$$S_{ij} = S_{ji} \quad \text{or} \quad [S] = [S]^T \quad \text{Matrix symmetry!}$$

Symmetrical networks:

$$S_{ii} = S_{jj} \quad \text{and} \quad S_{ij} = S_{ji} \quad \text{Electrical Symmetry and Matrix symmetry!}$$

Lossless networks:

For a lossless passive network the scattering matrix [S] is **unitary**:

$$[S]^T [S]^* = [U]$$

transpose
complex-conjugate

Example: two-port network

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad \rightarrow \quad [S]^T [S]^* = ?$$

Properties of S-Parameters

Reciprocal networks:

$$S_{ij} = S_{ji} \quad \text{or} \quad [S] = [S]^T \quad \text{Matrix symmetry!}$$

Symmetrical networks:

$$S_{ii} = S_{jj} \quad \text{and} \quad S_{ij} = S_{ji} \quad \text{Electrical Symmetry and Matrix symmetry!}$$

Lossless networks:

For a lossless network, $[S]$ is unitary.

PHYSICAL SYMMETRY?

Example: two-port network

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad \rightarrow \quad [S]^T [S]^* = ?$$

Lossless Two-Port Networks

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad [S]^T = \begin{bmatrix} S_{11} & S_{21} \\ S_{12} & S_{22} \end{bmatrix} \quad [S]^* = \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix}$$

Then

$$[S]^T [S]^* = \begin{bmatrix} S_{11} & S_{21} \\ S_{12} & S_{22} \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix} = \begin{bmatrix} |S_{11}|^2 + |S_{21}|^2 & S_{11}S_{12}^* + S_{21}S_{22}^* \\ S_{12}S_{11}^* + S_{22}S_{21}^* & |S_{12}|^2 + |S_{22}|^2 \end{bmatrix}$$

From unitary condition follows:

$$\begin{aligned} |S_{11}|^2 + |S_{21}|^2 &= 1 = |S_{12}|^2 + |S_{22}|^2 \\ S_{12}S_{11}^* + S_{22}S_{21}^* &= 0 = S_{11}S_{12}^* + S_{21}S_{22}^* \end{aligned}$$

Example: lossless TL

$$[S] = \begin{bmatrix} 0 & e^{-j\theta} \\ e^{-j\theta} & 0 \end{bmatrix}$$

$$\begin{aligned} |S_{11}|^2 + |S_{21}|^2 &= |0|^2 + |e^{-j\theta}|^2 = 1 \\ S_{12}S_{11}^* + S_{22}S_{21}^* &= e^{-j\theta} \cdot 0 + e^{-j\theta} \cdot 0 = 0 \end{aligned}$$

Lossless Two-Port Networks

$$[S] = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad [S]^T = \begin{bmatrix} S_{11} & S_{21} \\ S_{12} & S_{22} \end{bmatrix} \quad [S]^* = \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix}$$

Then

$$[S]^T [S]^* = \begin{bmatrix} S_{11} & S_{21} \\ S_{12} & S_{22} \end{bmatrix} \begin{bmatrix} S_{11}^* & S_{12}^* \\ S_{21}^* & S_{22}^* \end{bmatrix} = \begin{bmatrix} |S_{11}|^2 + |S_{21}|^2 & S_{11}S_{12}^* + S_{21}S_{22}^* \\ S_{12}S_{11}^* + S_{22}S_{21}^* & |S_{12}|^2 + |S_{22}|^2 \end{bmatrix}$$


for passive (lossy) networks

$$|S_{11}|^2 + |S_{21}|^2 \leq 1 \geq |S_{12}|^2 + |S_{22}|^2$$

$$S_{12}S_{11}^* + S_{22}S_{21}^* = 0 = S_{11}S_{12}^* + S_{21}S_{22}^*$$

Applications

Terminated Port:

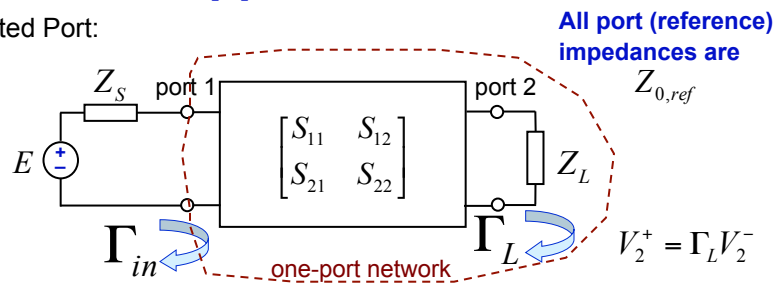

$$V_1^- = S_{11}V_1^+ + S_{12}V_2^+ \quad V_2^+ = \Gamma_L S_{21}V_1^+ + \Gamma_L S_{22}V_2^+ \quad V_2^+ = \frac{\Gamma_L S_{21}}{1 - \Gamma_L S_{22}} V_1^+$$

$$V_2^- = S_{21}V_1^+ + S_{22}V_2^+$$


$$\Gamma_{in} = S_{11} + \frac{\Gamma_L S_{12} S_{21}}{1 - \Gamma_L S_{22}}$$

$(Z_s = Z_{0,ref})$

special case: $Z_L=0 \rightarrow \Gamma_L = -1$

$$\Gamma_{in} = S_{11} - \frac{S_{12} S_{21}}{1 + S_{22}}$$

Shift in Reference Plane

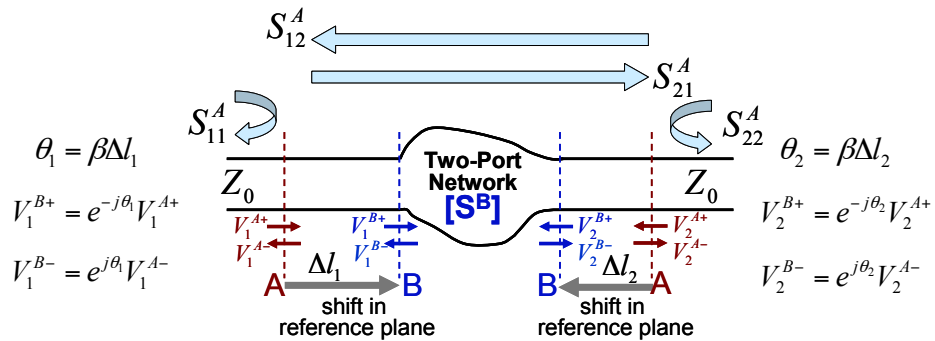

$$\begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{bmatrix} \begin{bmatrix} V_1^{B-} \\ V_2^{B-} \end{bmatrix} = \begin{bmatrix} S_{11}^A & S_{12}^A \\ S_{21}^A & S_{22}^A \end{bmatrix} \begin{bmatrix} e^{j\theta_1} & 0 \\ 0 & e^{j\theta_2} \end{bmatrix} \begin{bmatrix} V_1^{B+} \\ V_2^{B+} \end{bmatrix}$$

$$\begin{bmatrix} S_{11}^B & S_{12}^B \\ S_{21}^B & S_{22}^B \end{bmatrix} = \begin{bmatrix} e^{j\theta_1} & 0 \\ 0 & e^{j\theta_2} \end{bmatrix} \begin{bmatrix} S_{11}^A & S_{12}^A \\ S_{21}^A & S_{22}^A \end{bmatrix} \begin{bmatrix} e^{j\theta_1} & 0 \\ 0 & e^{j\theta_2} \end{bmatrix}$$

S-Matrix Renormalization

$$\mathbf{S} = (\mathbf{Z}_n + \mathbf{U})^{-1}(\mathbf{Z}_n - \mathbf{U}) = (\mathbf{Z}_n - \mathbf{U})(\mathbf{Z}_n + \mathbf{U})^{-1}$$

$$\mathbf{Z}_n = (\mathbf{U} + \mathbf{S})(\mathbf{U} - \mathbf{S})^{-1}$$


$$\mathbf{Z}_n^{\text{new}} = \mathbf{R}_{0,\text{new}}^{-1/2} \mathbf{Z} \mathbf{R}_{0,\text{new}}^{-1/2} = \mathbf{F} \mathbf{Z}_n^{\text{old}} \mathbf{F}$$

($\mathbf{Z}_0 = \mathbf{R}_0 = \text{real}$)



Renormalization matrix

$$\mathbf{F} = \begin{bmatrix} \sqrt{R_{0,1}^{\text{old}}/R_{0,1}^{\text{new}}} & 0 & 0 \\ 0 & \ddots & 0 \\ 0 & 0 & \sqrt{R_{0,N}^{\text{old}}/R_{0,N}^{\text{new}}} \end{bmatrix}$$

Example

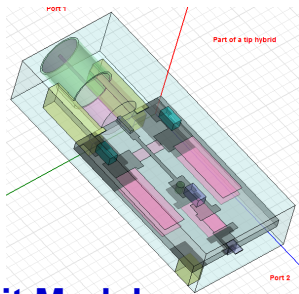



Circuit Model

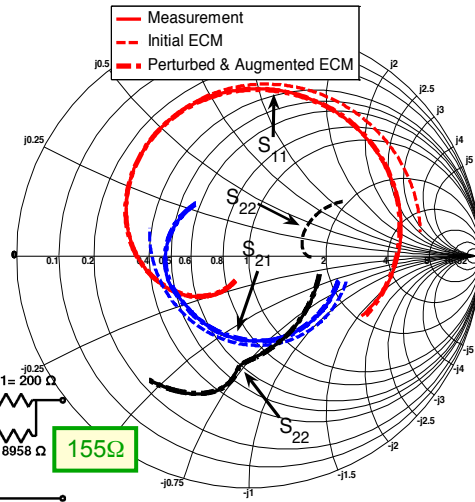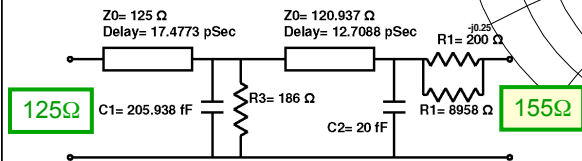


Comparison of Different Port Normalizations

$$Z_{0,1} = 125\Omega \quad Z_{0,2} = 155\Omega$$

$$Z_{0,1} = Z_{0,2} = 50\Omega$$

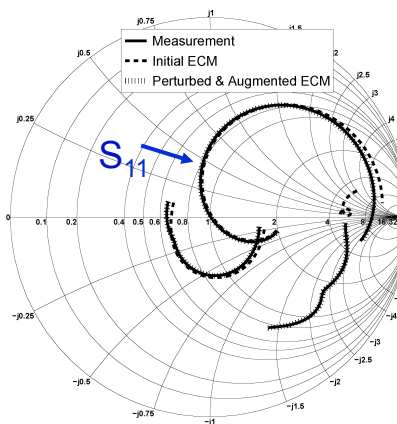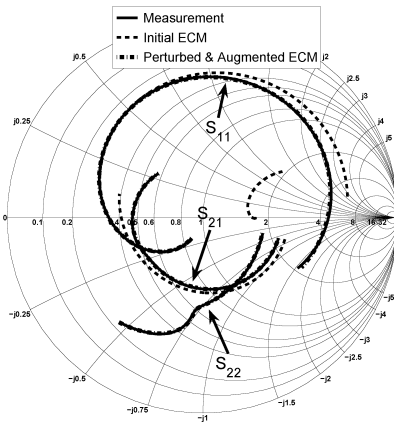

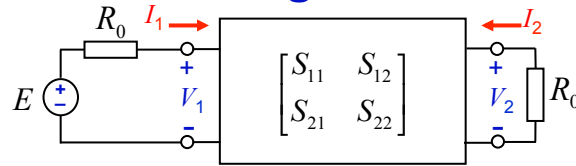Voltage Transfer Function from Scattering Parameters



$$V_1^+ = \frac{1}{2}(V_1 + Z_0 I_1) \quad V_2^- = \frac{1}{2}(V_2 - Z_0 I_2)$$


$$Z_{in} = R_0 \frac{1 + S_{11}}{1 - S_{11}} \quad I_1 = \frac{V_1}{Z_{in}} = \frac{V_1}{R_0} \frac{1 - S_{11}}{1 + S_{11}}$$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{V_2 - R_0 I_2}{V_1 + R_0 I_1} = \frac{2V_2}{V_1 \left(1 + \frac{1 - S_{11}}{1 + S_{11}}\right)} = \dots = \frac{V_2}{V_1} (1 + S_{11})$$

$$\Rightarrow \frac{V_2}{V_1} = \frac{S_{21}}{1 + S_{11}}$$

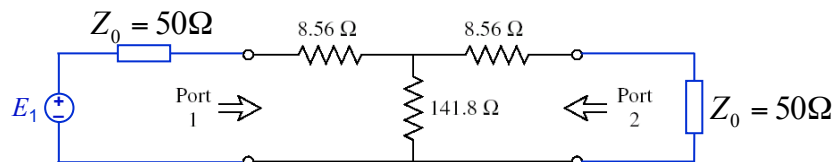Example

Matched 3dB attenuator ($Z_0 = 50 \Omega$) (Ref: Pozar pp. 175/6)




$$V_1 = E_1 \frac{Z_{in,1}}{Z_{in,1} + Z_0} = \frac{1}{2} E_1 \quad Z_{in,1} = 41.444 \Omega + 8.56 \Omega \approx 50 \Omega$$

$$V_2 = V_1 \left(\frac{41.444}{41.444 + 8.56} \right) \left(\frac{50}{50 + 8.56} \right) = 0.7077 V_1$$

$$S_{11} = S_{22} = 0 \quad S_{12} = S_{21} = 0.7077 \quad IL = -20 \log_{10} |S_{21}| = 3 \text{ dB}$$

Example using Z-Matrix

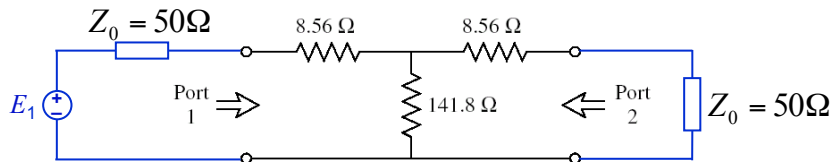

$$\mathbf{Z} = \begin{bmatrix} 150.36 & 141.80 \\ 141.80 & 150.36 \end{bmatrix} \Omega$$

$$Z_{0,1} = Z_{0,2} = 50 \Omega$$

$$\mathbf{Z}_n = \mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} = \begin{bmatrix} 3.0072 & 2.8360 \\ 2.8360 & 3.0072 \end{bmatrix} \quad \mathbf{S} = \begin{bmatrix} 0 & 0.7077 \\ 0.7077 & 0 \end{bmatrix}$$

$$Z_{0,1} = 50 \Omega \quad Z_{0,2} = 100 \Omega$$

$$\mathbf{Z}_n = \mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} = \begin{bmatrix} 3.0072 & 2.0054 \\ 2.0054 & 1.5036 \end{bmatrix} \quad \mathbf{S} = \begin{bmatrix} 0.1670 & 0.6672 \\ 0.6672 & -0.3333 \end{bmatrix}$$

Attenuator terminated in $Z_L=100\Omega$ and
S-Parameters wrt $Z_{0,1}=Z_{0,2}=50\Omega$

$$\Gamma_L = \frac{Z_L - Z_{0,2}}{Z_L + Z_{0,2}} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$$\Gamma_{in} = S_{11} + \frac{\Gamma_L S_{12} S_{21}}{1 - \Gamma_L S_{22}} = \Gamma_L S_{12} S_{21} = \frac{1}{3} \frac{1}{\sqrt{2}} \frac{1}{\sqrt{2}} = 0.167$$

50Ω

Attenuator terminated in $Z_L=100\Omega$ and
S-Parameters wrt $Z_{0,1}=50\Omega \quad Z_{0,2}=100\Omega$

$$\Gamma_L = \frac{Z_L - Z_{0,2}}{Z_L + Z_{0,2}} = 0$$

$$\Gamma_{in} = S_{11} + \frac{\Gamma_L S_{12} S_{21}}{1 - \Gamma_L S_{22}} = S_{11} = 0.167$$

$$Z_{0,1} = Z_{0,2} = 50 \Omega$$

$$\mathbf{Z}_n = \mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} = \begin{bmatrix} 3.0072 & 2.8360 \\ 2.8360 & 3.0072 \end{bmatrix} \quad \mathbf{S} = \begin{bmatrix} 0 & 0.7077 \\ 0.7077 & 0 \end{bmatrix}$$

$$Z_{0,1} = 50 \Omega \quad Z_{0,2} = 100 \Omega$$

$$\mathbf{Z}_n = \mathbf{R}_0^{-1/2} \mathbf{Z} \mathbf{R}_0^{-1/2} = \begin{bmatrix} 3.0072 & 2.0054 \\ 2.0054 & 1.5036 \end{bmatrix} \quad \mathbf{S} = \begin{bmatrix} 0.1670 & 0.6672 \\ 0.6672 & -0.3333 \end{bmatrix}$$

Conversion between Network Parameters

	S	Z	Y	ABCD
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 + S_{22}) - S_{12}S_{21}}$	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
Y_{11}	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 - S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{11}}$	A
B	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	B
C	$\frac{1 - (1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	C
D	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	D

$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}$; $|Y| = Y_{11}Y_{22} - Y_{12}Y_{21}$; $\Delta Y = (Y_0 + Y_0)(Y_0 + Y_0) - Y_{12}Y_{21}$; $\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$; $Y_0 = 1/Z_0$

Properties of Network Parameters

▪ Symmetric Two-Port Network

$$Z_{11} = Z_{22} \quad Y_{11} = Y_{22} \quad S_{11} = S_{22} \quad A = D$$

↑
assuming the same port impedances

▪ Reciprocal Network

$$Z_{ij} = Z_{ji} \quad Y_{ij} = Y_{ji} \quad S_{ij} = S_{ji} \quad AD - BC = 1$$

▪ Lossless Network

$$\operatorname{Re}\{Z_{ij}\} = 0 \quad \operatorname{Re}\{Y_{ij}\} = 0 \quad \mathbf{S}^T \mathbf{S}^* = \mathbf{I} \quad \begin{cases} \operatorname{Re}\{B, C\} = 0 \\ \operatorname{Im}\{A, D\} = 0 \end{cases}$$

e.g. $|S_{11}|^2 + |S_{21}|^2 = 1$