

## HW2 Solution

1. Assume  $V_{out} = 1V$ ,


$$I_{L3} = (sC_4 + \frac{1}{R_2}) \cdot V_{out} = sC_4 + \frac{1}{R_2}$$

$$V_1 = V_{out} + I_{L3} \cdot sL_3 = 1 + (sC_4 + \frac{1}{R_2}) \cdot sL_3$$

$$I_{C2} = sC_2 \cdot V_1 = sC_2 [1 + (sC_4 + \frac{1}{R_2}) \cdot sL_3]$$

$$I_s = I_{L3} + I_{C2} = (sC_4 + \frac{1}{R_2}) + sC_2 [1 + (sC_4 + \frac{1}{R_2}) \cdot sL_3]$$
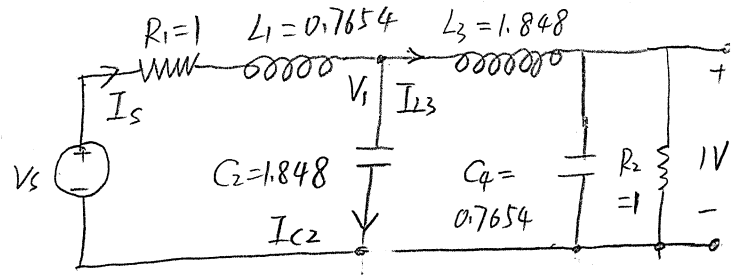
$$V_s = I_s (R_1 + sL_1) + V_1 = [(sC_4 + \frac{1}{R_2}) + sC_2 [1 + (sC_4 + \frac{1}{R_2}) \cdot sL_3]] (R_1 + sL_1) + 1 + (sC_4 + \frac{1}{R_2}) \cdot sL_3$$




$$H(s) = \frac{V_{out}}{V_s} = \frac{1}{V_s} = \frac{1}{2(s^4 + 2.6135s^3 + 3.4149s^2 + 2.6135s + 1)}$$

$$H(j\omega) = \frac{1}{2(\omega^4 - 2.6135j\omega^3 - 3.4149\omega^2 + 2.6135j\omega + 1)}$$

2.  $Y_{11} = \frac{I_1}{V_1} |_{V_2=0}$        $Y_{12} = \frac{I_1}{V_2} |_{V_1=0}$

$Y_{21} = \frac{I_2}{V_1} |_{V_2=0}$        $Y_{22} = \frac{I_2}{V_2} |_{V_1=0}$

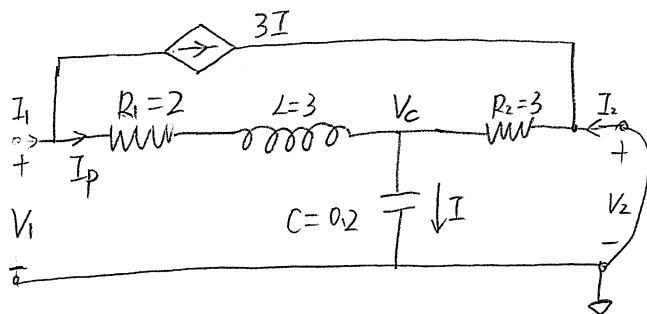$Y_{11}$  and  $Y_{21}$ , the network becomes :



$$V_c = I \cdot \frac{1}{sC} \quad I_p = I + \frac{V_c}{R_2} = I \left( 1 + \frac{1}{sCR_2} \right)$$

$$V_1 = I_p (R_1 + sL) + V_c$$

$$I_1 = I_p + 3I$$


$$Y_{11} = \frac{I_1}{V_1} = \frac{1 + 4sR_2C}{(sR_2C + 1)(R_1 + sL) + R_2} = \frac{1 + 24[s]}{1.8[s^2] + 4.2[s] + 5}$$

$$Y_{21} = \frac{I_2}{V_1}, \quad V_1 = I_p (R_1 + sL) + V_c$$

$$I_2 = -3I - \frac{V_c}{R_2}$$

$$\Rightarrow Y_{21} = - \frac{1 + 3sR_2C}{(sR_2C + 1)(R_1 + sL) + R_2} = \frac{-1.8[s] - 1}{1.8[s^2] + 4.2[s] + 5}$$

to calculate  $Y_{12}$  and  $Y_{22}$

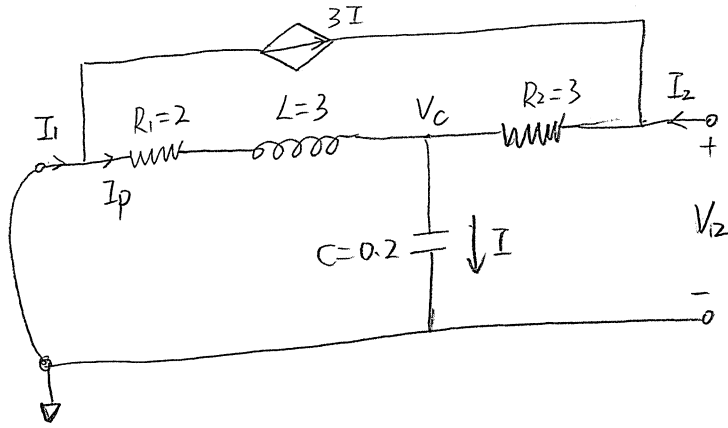

$$V_C = I \cdot \frac{1}{sC}$$

$$I_p = -\frac{V_C}{R_1 + sL}$$

$$I_1 = I_p + 3I$$

$$V_2 = (I - I_p) \cdot R_2 + V_C$$

$$\Rightarrow Y_{12} = \frac{I_1}{V_2} = \frac{3sC(R_1 + sL) - 1}{R_2 + sCR_2(R_1 + sL) + R_1 + sL}$$

$$= \frac{1.8[s^2] + 1.2[s] - 1}{1.8[s^2] + 4.2[s] + 5}$$

$$Y_{22}: \quad V_2 = (I - I_p) \cdot R_2 + V_C$$

$$I_2 = I - I_p - 3I = -2I - I_p$$

$$\Rightarrow Y_{22} = \frac{I_2}{V_2} = \frac{-2sC(R_1 + sL) + 1}{R_2 + sCR_2(R_1 + sL) + R_1 + sL}$$

$$= \frac{-1.2[s^2] - 0.8[s] + 1}{1.8[s^2] + 4.2[s] + 5}$$

$$Y_{11} = \frac{2.4 \boxed{S} + 1}{1.8 \boxed{S^2} + 4.2 \boxed{S} + 5}$$

$$Y_{21} = \frac{-1.8 \boxed{S} - 1}{1.8 \boxed{S^2} + 4.2 \boxed{S} + 5}$$

$$Y_{12} = \frac{1.8 \boxed{S^2} + 1.2 \boxed{S} - 1}{1.8 \boxed{S^2} + 4.2 \boxed{S} + 5}$$

$$Y_{22} = \frac{-1.2 \boxed{S^2} - 0.8 \boxed{S} + 1}{1.8 \boxed{S^2} + 4.2 \boxed{S} + 5}$$