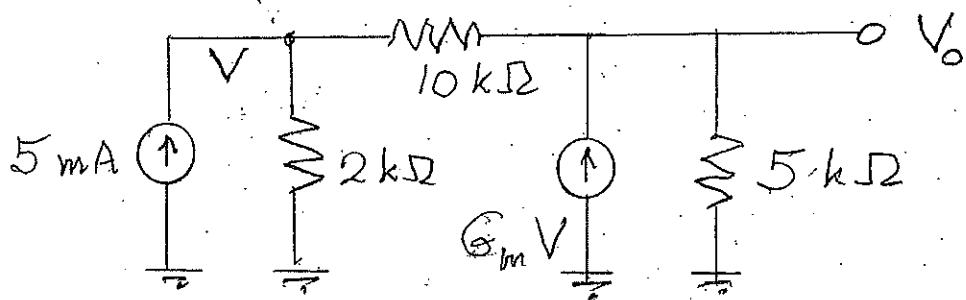


ECE 580 HOMEWORK 3

Due Nov. 19, 2018

1. Using the adjoint network, find the sensitivities of V_o to changes of the transconductance G_m . The nominal value is $G_m = 3 \text{ mA/V}$.



2. Prove that the phase shift of a lumped linear two-port is an odd function of the frequency, so that $\beta(-\omega) = -\beta(\omega)$.