

$$1. G_1(\overset{\vee}{V}_{in} - \overset{\vee}{V}) + sC_2(\overset{\vee}{V}_0 - \overset{\vee}{V}) = (G_4 + sC_3)\overset{\vee}{V}$$

$$(G_1 + sC_2 + G_4 + sC_3)\overset{\vee}{V} = G_1\overset{\vee}{V}_{in} + sC_2\overset{\vee}{V}_0$$

$$\overset{\vee}{V} = \frac{G_1\overset{\vee}{V}_{in} + sC_2\overset{\vee}{V}_0}{()}$$

$$G_5\overset{\vee}{V}_0 = -sC_3\overset{\vee}{V}$$

$$() G_5\overset{\vee}{V}_0 = -sC_3 G_1 \overset{\vee}{V}_{in} - s^2 C_2 C_3 \overset{\vee}{V}_0$$

$$\begin{aligned} \overset{\vee}{V}_0 &= -sC_3 G_1 \overset{\vee}{V}_{in} \bigg/ \left[s^2 C_2 C_3 + G_5(G_1 + G_4 + s(C_2 + C_3)) \right] \\ &= \frac{-sG_1 C_3 \overset{\vee}{V}_{in}}{s^2 C_2 C_3 + sG_5(C_2 + C_3) + (G_1 + G_4)G_5} \end{aligned}$$

$$a. \omega_p^2 = \frac{G_1 + G_4}{C_2 C_3} G_5$$

$$\omega_p / Q_p = G_5 (1/C_2 + 1/C_3)$$

$$Q_p = \frac{\sqrt{G_5(G_1 + G_4)} C_2 C_3}{\sqrt{C_2 C_3} \sqrt{G_5(C_2 + C_3)}}$$

$$y = 1/Q_p = \frac{\sqrt{G_5}}{\sqrt{G_1 + G_4}} \left[\sqrt{\frac{C_2}{C_3}} + \sqrt{\frac{C_3}{C_2}} \right] = k(x + 1/x)$$

$$b. \frac{\partial y}{\partial x} = 1 - 1/x^2 \rightarrow x_{opt} = \pm 1, C_2 = C_3$$

$$c. Q_{pmax} = \frac{1}{2} \sqrt{\frac{G_1 + G_4}{G_5}}$$

$$2. (V_{in} - V_b) sC_1 - G_{m1} V_{out} = 0$$

$$sC_1 V_b = sC_1 V_{in} - G_{m1} V_{out}$$

$$V_b = V_{in} - \frac{G_{m1}}{sC_1} V_{out}$$

$$V_{out} = \frac{1}{sC_2} [G_{m2} V_b - G_{m3} V_{out}]$$

$$\left[1 + \frac{G_{m3}}{sC_2} \right] V_{out} = \frac{G_{m2}}{sC_2} \left[V_{in} - \frac{G_{m1}}{sC_1} V_{out} \right]$$

$$\left[\frac{G_{m1} G_{m3}}{s^2 C_1 C_2} + \frac{G_{m3}}{sC_2} + 1 \right] V_{out} = \frac{G_{m2}}{sC_2} V_{in}$$

$$a. H(s) = \frac{(G_{m2}/C_2) s}{s^2 + (G_{m3}/C_2) s + (G_{m1} G_{m2}/C_1 C_2)}$$

$$b. \omega_p^2 = \frac{C_2}{C_1} \frac{G_{m1} G_{m2}}{G_{m3}} \quad \omega_p^2$$

$$c. \text{Midband gain } |H(\omega_p)| = G_{m2}/G_{m3}$$


$$3. V = G_{m1} V_{in} Z_L$$

$$I = G_{m2} V = G_{m2} G_{m1} V_{in} Z_L$$

$$a. Z_{in} = \frac{V_{in}}{I} = \frac{1}{G_{m1} G_{m2} Z_L}$$

b. Floating inductor.

c. Ideally, impossible

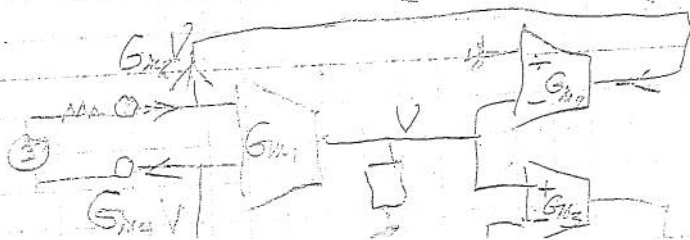

Gaussian surface forces $G_{m1} V = G_{m2} V$. So circuit stops working. Try