


ECE 627

Midterm Examination


May 9, 2014

Open book

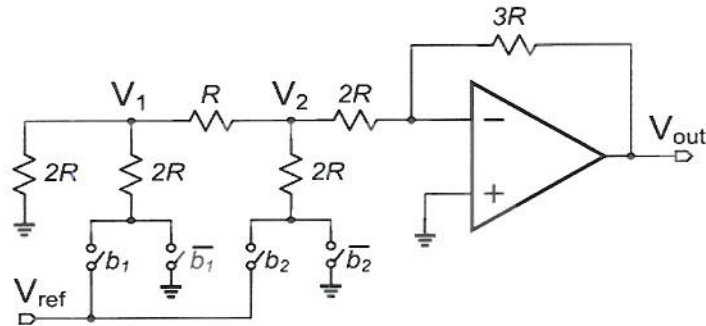
1. In the DAC shown, the opamp is ideal, and $V_{ref} = 2$ V.
 - a. Find the input-output relation of the DAC.
 - b. What are the LSB voltage steps in V_{out} ?
 - c. Is the DAC monotonic?
 - d. What will be the values of the voltages V_1 and V_2 if the input word is 11?
 - e. Find V_{out} if the opamp has a gain of 60 dB. (Difficult, for extra credit only!!)



2. a. Find the STF and NTF of the $\Delta\Sigma$ ADC shown. Use $H(z) = z^{-1}/(1-z^{-1})$.
 - b. What is the value of $|NTF|$ at dc, and at $f_s/2$?

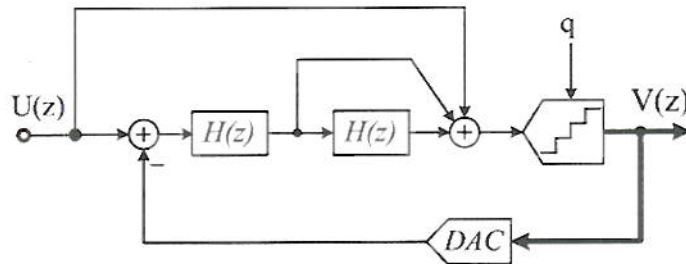

1.

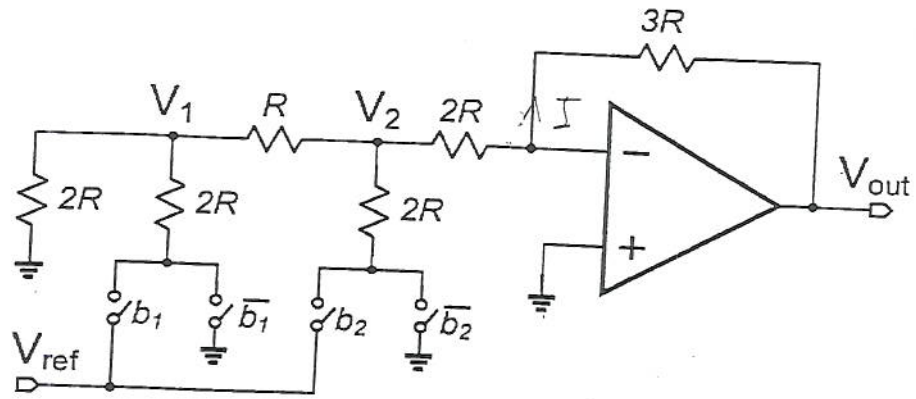

a. For $b_2 = 1, b_1 = 0$

$$I = V_{ref} / 6R, \quad V_{out} = -V_{ref} / 2$$

For $b_1 = 1, b_2 = 0$

$$I = V_{ref} / 12R, \quad V_{out} = -V_{ref} / 4$$

By superposition


$$V_{out} = -(V_{ref} / 4) (b_1 + 2b_2) = -\frac{b_1}{2} - b_2 \quad (V)$$

b. $V_{LSB} = V_{ref} / 4 = 0.5V$

c. Yes, under practical conditions.

d. By symmetry, for $b_1 = b_2 = 1, V_1 = V_2$.
No current through R , so $V_1 = V_2 = V_{ref} / 2 = 1V$

Thévenin eq. of R-2R input branch

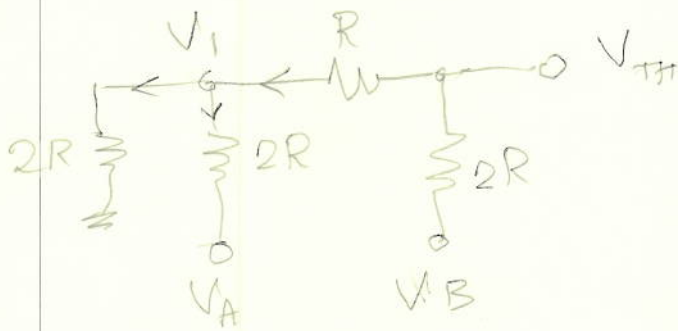

$$\frac{V_1}{2R} + \frac{V_1 - V_A}{2R} = \frac{V_B - V_1}{3R}$$

$$V_1 \left(\frac{G}{2} + \frac{G}{2} + \frac{G}{3} \right) = V_A \frac{G}{2} + V_B \frac{G}{3}$$

4/3


$$V_1 = \frac{3}{8} V_A + \frac{1}{4} V_B$$

$$V_A = b_1 V_{ref}$$

$$V_B = b_2 V_{ref}$$

$$V_{TH} = V_B - \frac{2}{3} (V_B - V_1) = V_A/4 + V_B/2$$

$$= b_1/2 + b_2$$

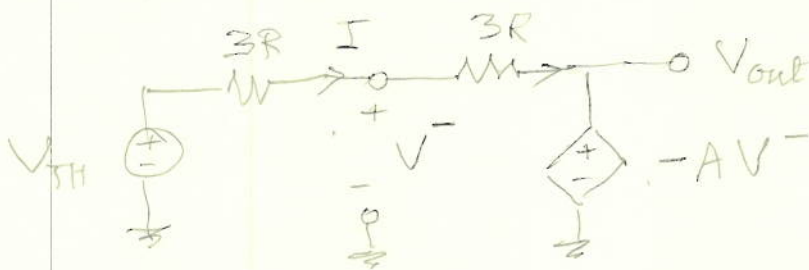


$$I = \frac{V_{TH} - V_{out}}{6R} = \frac{1}{3R} \left(-\frac{1}{A} - 1 \right) V_{out} = -\frac{\mu+1}{3R} V_{out}$$

$$V_{TH} = (1 - 2(\mu+1)) V_{out} = -(1 + 2\mu) V_{out}$$

$$V_{out} = -\frac{V_{TH}}{1 + 2\mu} = -(1 + 2/A) V_{ref} (b_1/4 + b_2/2)$$

$$\approx -0.998 (b_1/2 + b_2)$$

2.

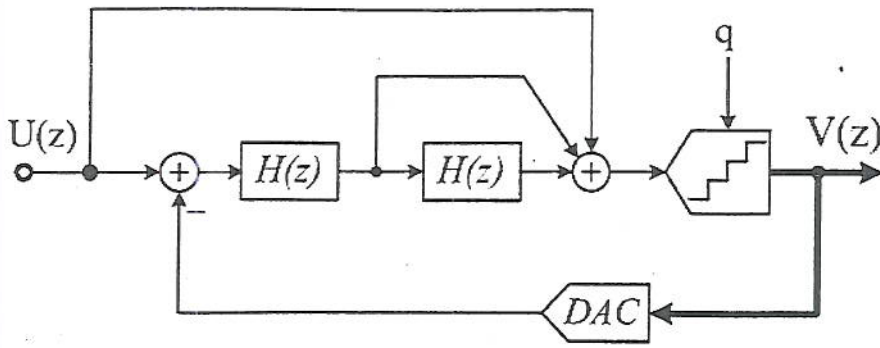

$$2. a. V = Q + U + H(H+1)(U-V)$$

$$V(1+H+H^2) = Q + U(1+H+H^2)$$

$$STF \equiv 1$$

$$NTF = (1+H+H^2)^{-1} = \frac{(1-z^{-1})^2}{(1-z^{-1})^2 + z^{-1}(1-z^{-1}) + z^{-2}}$$

$$= (1-z^{-1})^2 / (1 - \cancel{z^{-1}} + \cancel{z^{-2}} + \cancel{z^{-1}} - \cancel{z^{-2}} + z^{-2})$$

$$= \frac{(1-z^{-1})^2}{1-z^{-1}+z^{-2}}$$

b. dc: $z=1$, $|NTF| \sim (\omega T)^2 \sim 0$

$\frac{\omega_s}{2}$: $z=-1$, $|NTF| = 4/3$