
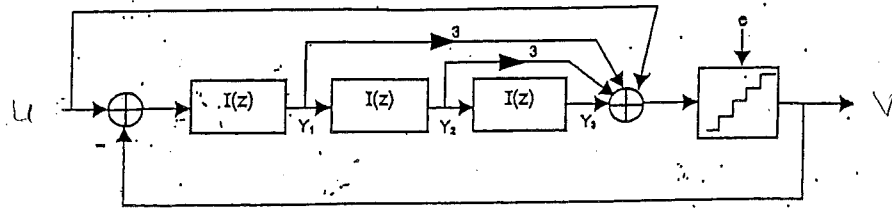


June 6, 2015, 9:30 – 11:20 am


1. In the circuit shown,  $I(z) = 1/(z - 1)$ . Find the integrator outputs in the time domain. Assuming that the quantizer is not overloaded, so  $|e| < V_{LSB}/2$ , what are the largest values of  $y_1, y_2$  and  $y_3$ ?

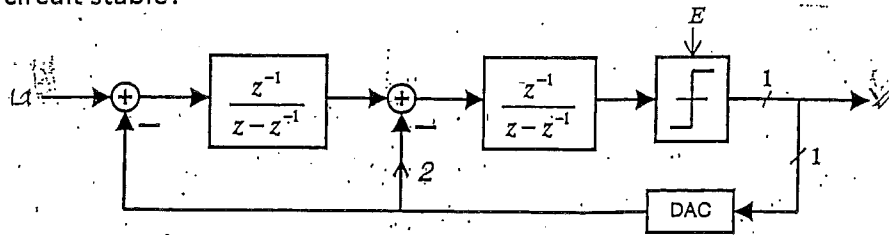

2. a. Find the transfer functions  $STF(z)$  and  $NTF(z)$  of the  $\Delta\Sigma$  ADC shown. Use  $I(z) = 1/(z^2-1)$ . (Note the unusual functions!)
- b. Where are the zeros and poles of  $STF(z)$  and  $NTF(z)$ ?
- c. Draw  $|NTF|$  as a function of frequency for  $0 < f < f_s/2$ .
- d. Is the circuit stable?



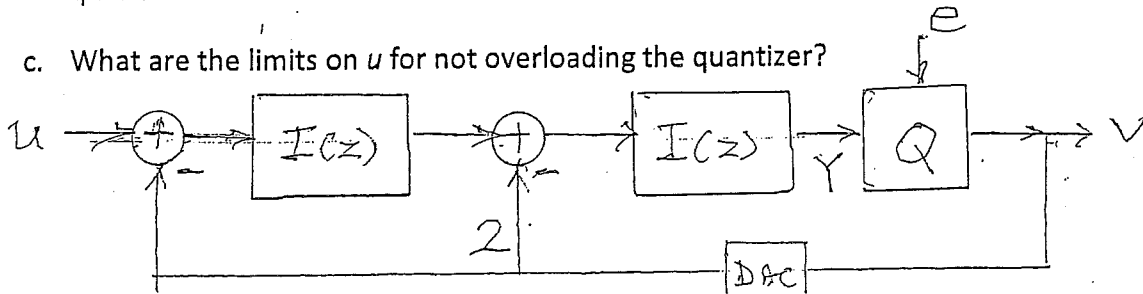3. In the  $\Delta\Sigma$  ADC shown,  $I(z) = 1/(z - 1)$ . Two-bit quantization is used, and  $V_{ref} = 3$  V.
  - a. Find the  $NTF$  and  $STF$ .
  - b. Find the largest and smallest values of  $y(n)$  for a given dc input  $u$ , assuming that the quantizer is not overloaded.
  - c. What are the limits on  $u$  for not overloading the quantizer?



$$1. \quad V = E + U + (U - V)(3I + 3I^2 + I^3)$$

$$V(1+I)^3 = U(1+I)^3 + E$$

$$\text{STF} \equiv 1, \quad \text{NTF} = (1+I)^{-3} = (1-z^{-1})^3$$

$$Y_1 = I(U - V) = -I(1-z^{-1})^3 E = -z^{-1}(1-z^{-1})^2 E$$

$$y_1 = -e(n-1) + 2e(n-2) - e(n-3)$$

$$|y_1| \leq 4|e|_{\max} = 2V_{\text{LSB}}$$

$$Y_2 = -I^2(1-z^{-1})^3 E = -z^{-2}(1-z^{-1}) E$$

$$y_2 = -e(n-2) + e(n-3)$$

$$|y_2| \leq 2|e|_{\max} = V_{\text{LSB}}$$

$$Y_3 = -I^3(1-z^{-1})^3 E = -z^{-3} E$$

$$y_3 = -e(n-3)$$

$$|y_3| \leq |e|_{\max} = V_{\text{LSB}}/2$$

$$2) a \quad V = E + I [-2V + I(u - V)]$$

$$V(1 + 2I + I^2) = E + I^2 u$$


$$(1 + I)^2 = \left[ 1 + \frac{1}{z^2 - 1} \right]^2 = \left[ \frac{z^2}{z^2 - 1} \right]^2$$

$$NTF = \frac{(z^2 - 1)^2}{z^4} \quad \text{zeros at } z = \pm 1 \text{ (double)}$$

4 poles at  $z = 0$

$$STF = z^{-4}; \quad 4 \text{ poles at } z = 0$$

b.

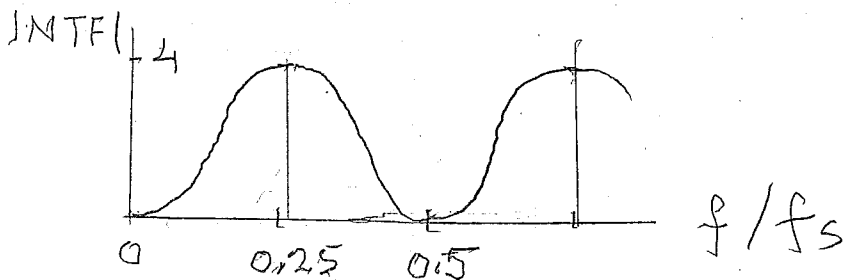

c. The NTF is that of MOD2, with  $z$  replaced by  $z^2$ , same for STF. So both frequency responses are compressed by 2, and the time responses stretched by 2. Since MOD2 is stable, so is this system, for a range of inputs.

$$3. a. \quad V = E + I[-2V + I(U - V)]$$

$$V(1 + 2I + I^2) = E + I^2 U$$

$$(I+1)^2 = \frac{z^2}{(z-1)^2}$$

$$NTF = (1 - z^{-1})^2$$

$$STF = z^{-2}$$

$$b. \quad Y = V - E = z^{-2}U + [(1 - z^{-1})^2 - 1]E$$

$$y(n) = u(n-2) - 2e(n-1) + e(n-2)$$

For the quantizer not over-loaded,  $|e| \leq V_{LSB}/2 = 3/8 \text{ V}$

Hence,

$$u - 9/8 \leq y \leq u + 9/8$$

c. To avoid overloading the quantizer,  $-V_{LSB}/2 \leq y \leq V_{ref} + V_{LSB}/2$  must hold. Hence

$$u_{min} - 9/8 \geq -V_{LSB}/2 \rightarrow u_{min} \geq 0.75 \text{ V}$$

$$u_{max} + 9/8 \leq 3 - 3/8 \rightarrow u_{max} \leq 1.5 \text{ V}$$