

ECE 627

Midterm Examination

May 8, 2015


Open book

1. (10 %) In a flash ADC, each comparator has a dc offset error V_{os} . Assuming 8-bit resolution and $V_{ref} = 5\text{ V}$, what are the limits on these offsets, if

- a. the condition $|DNL| < \frac{1}{2}\text{ LSB}$ must hold?
- b. there must not be any missing code in the output?

2. (15 %) A 10-bit DAC is shown below. $R = 50\ \Omega$. The currents are ideally $I_k = 2^k\ \mu\text{A}$, but each current may have a relative error e_k .

- a. Find the magnitude of the largest permissible relative error $|e_{max}|$ for all currents, if $|DNL| < \frac{1}{2}\text{ LSB}$.
- b. What is the maximum INL for this error?
- c. (5 % extra credit) What is the effect of the finite output impedances of the current sources? Assume $R_k = 10^6 \cdot 2^{-k} \cdot R$.

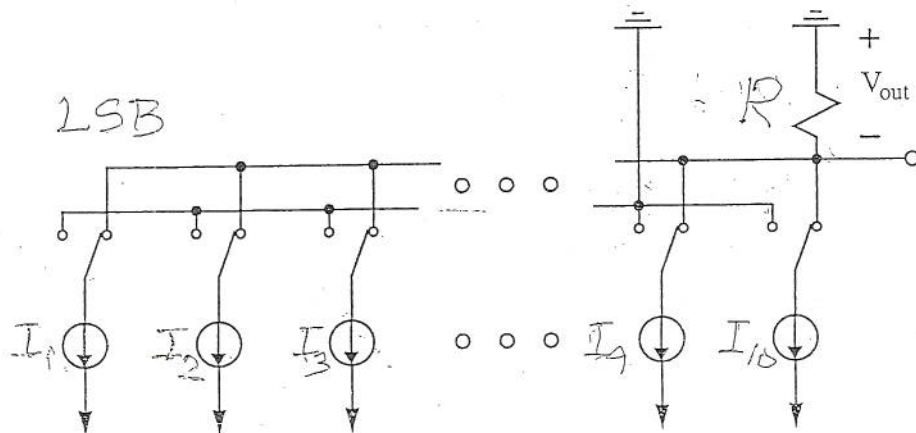


1. a. The input to the k^{th} comparator is $V_k = V_{\text{ref},k} \pm V_{\text{os},k} - V_{\text{in}}$. Hence, the

$\text{DNL}_k = V_{\text{os},k} - V_{\text{os},k-1}$. For $|\text{DNL}_k| < (1/2) V_{\text{LSB}} = V_{\text{ref}} / 2^{N+1}$, must have

$$|V_{\text{os},k}| + |V_{\text{os},k-1}| = 2|V_{\text{os},\text{max}}| < 2^{-N-1} V_{\text{ref}}$$

$$|V_{\text{os},\text{max}}| < V_{\text{ref}} / 2^{N+2} = \frac{5}{2^{10}} \approx 4.9 \text{ mV}$$

b. Missing code occurs if $V_k < V_{k-1}$ which may occur if $2|V_{\text{os},\text{max}}| > V_{\text{LSB}}$. Hence, to avoid it, $|V_{\text{os},\text{max}}| < 9.8 \text{ mV}$

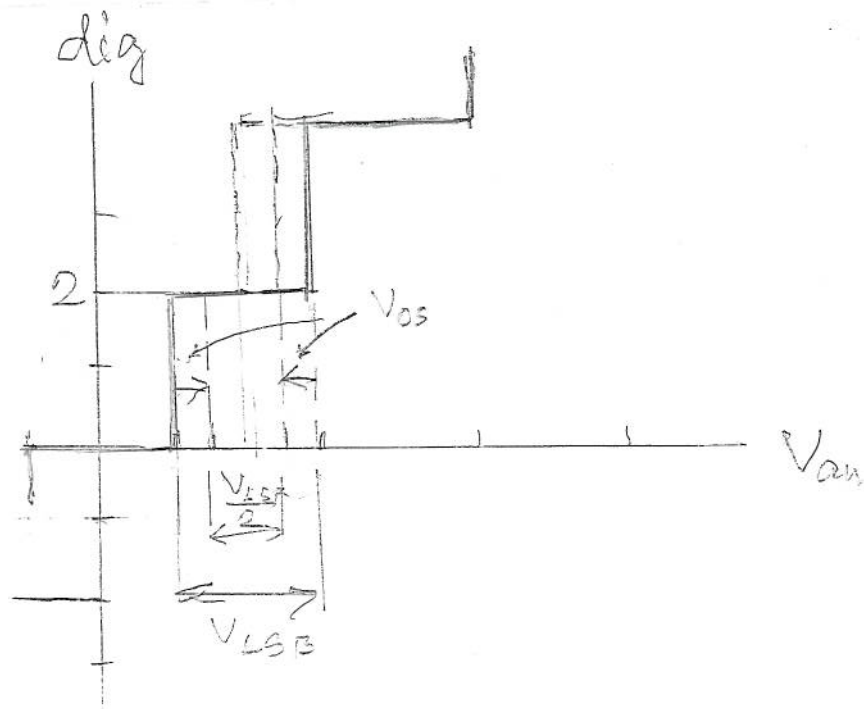

2.a Ideally, $V_{out} = R \sum_{k=1}^{10} b_k I_k$. With errors,

$$V_{out} = R \sum_{k=1}^{10} b_k 2^k \cdot 10^{-6} (1 + e_k), \text{ DNL}_{max}$$

can occur for the major carry transitions $011\dots 1 \leftrightarrow 100\dots 0$. Then, the

$$\text{DNL} = R \cdot 10^{-6} \sum_{k=1}^{10} 2^k e_k, \text{ and}$$

$$\text{DNL}_{max} = R \cdot 10^{-6} |e_{max}| \sum_{k=1}^{10} 2^k = \text{Hence,}$$

$\text{DNL}_{max} = V_{FS} |e_{max}|$, where V_{FS} is the full-scale output voltage:

$$V_{FS} = R (2^{11} - 1) 10^{-6} \approx 0.102 \text{ V. Also,}$$

$$V_{LSB} \approx 0.1 \text{ mV, Hence, we have}$$

$$|e_{max}| < V_{LSB} / (2 V_{FS}) \approx 5 \cdot 10^{-4} \text{ Not realizable!}$$



Absolute INL occurs for $e_k = e_{max}$,

$$\forall k: \text{INL}_{max} = \text{DNL}_{max} = 0.5 V_{LSB},$$

End-point INL occurs for $100\dots 00$.


Half of currents too large, half too
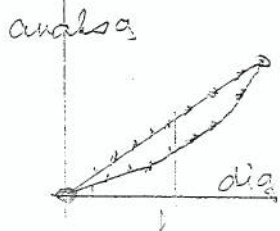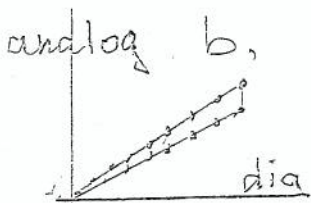
$$\text{small, so } \text{INL}_{max ep} = 0.25 V_{LSB},$$



2. c

3

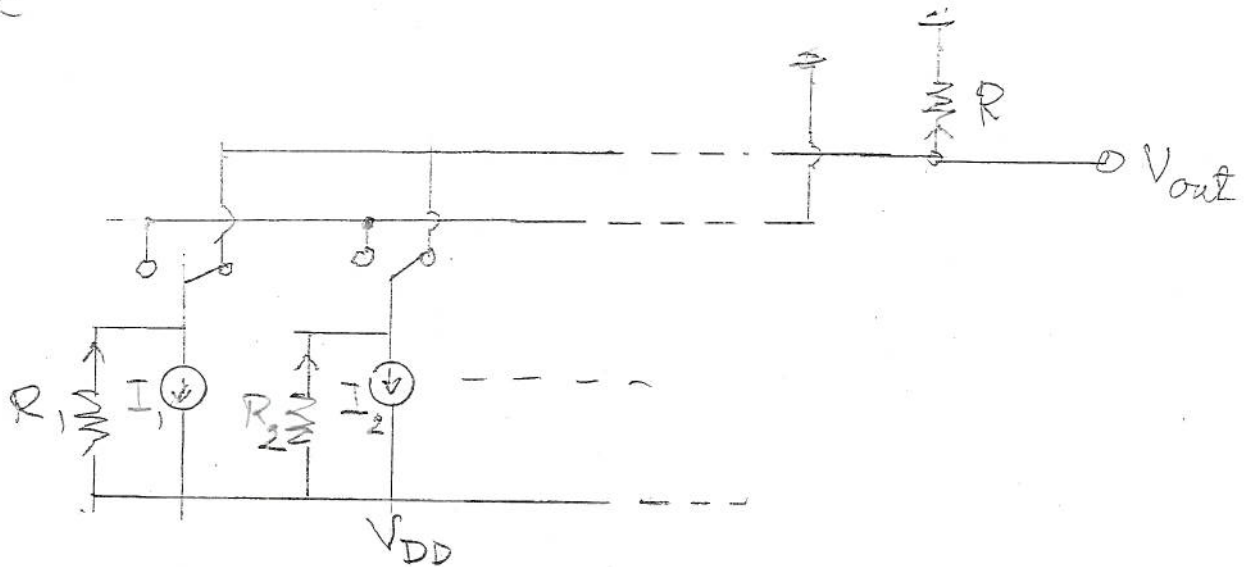

KCL at \$V_{out}\$:

$$GV_{out} + \sum_k b_k I_k = \sum_k b_k G_k (V_{DD} - V_{out})$$

$$\left[G + \sum_k b_k G_k \right] V_{out} = \sum_k b_k (G_k V_{DD} - I_k)$$

$$V_{out} = \frac{\sum_k b_k (G \cdot 2^k \cdot 10^{-6} \cdot V_{DD} - 2^k \times 10^{-6})}{G + \sum_k b_k G \cdot 2^k \times 10^{-6}}$$

$$= \frac{\sum_k b_k (G V_{DD} - 1)}{2^k \cdot 10^{-6} \cdot G + G \sum_k b_k}$$

$V_{out} \propto \sum_k b_k 2^k$, nonlinear operation!