

Brian L. Young, Oregon State University, 5/18/2009

ECE 627 PROJECT DESIGN STRATEGY

OUTLINE

- ✖ Software Tools
- ✖ Preliminary Calculations
- ✖ Mathematical Design Script, MATLAB
- ✖ Simulink Modeling
- ✖ Circuit Implementation
- ✖ Simulink Results
- ✖ Suggestions

SOFTWARE TOOLS

- ✖ MATLAB/Simulink
- ✖ Delta Sigma Toolbox (MATLAB)
 - + <http://www.mathworks.com/matlabcentral/fileexchange/19>
- ✖ SD Toolbox 2 (Simulink)
 - + <http://www.mathworks.com/matlabcentral/fileexchange/7589>
- ✖ Cadence/Spectre
- ✖ SWITCAP (“sw2” on SunOS machine)


WHERE TO BEGIN

- ✖ *Panic* for 5 seconds...
- ✖ Now, Stop *Panicking*
- ✖ Examine Requirements
 - + ENOB, F_{BW} , F_S , etc.
- ✖ Determine Target Technology
 - + Same as ECE 626?
- ✖ Explore DStoolbox Demos
 - + dsdemo[1-3,5].m



TRADEOFFS IN $\Delta\Sigma$ PARAMETERS



 
- ✖ Calculate SQNR
- ✖ Modulator Order, OSR,
Quantizer Levels
- ✖ Power efficient
designs → thermal
noise limited,
~~quantization noise~~
~~limited~~



EMPERICAL SQNR LIMITS


- Compare Modulator Order vs. OSR vs. Quantizer Resolution

[Schreier and Temes, 2005]

   

EXAMINE ARCHITECTURE

 - ✖ Consider $\Delta\Sigma$ Topologies
 - + Single Loop vs. MASH; CIFB, CIFF, CRFB, CRFF, etc.






- ✖ Write MATLAB script to optimize coefficients
 - + Order, OSR, Bits, $\|H\|_\infty$, etc.
 - + DStoolbox → dsdemo[1-3].m

MATLAB SCRIPT OUTPUT

- ✖ Modulator Coefficients
- ✖ NTF and STF
 - + Magnitude
 - + Poles and Zeros
- ✖ Time-domain Simulation Results

MODULATOR COEFFICIENTS

a_1	2.885522268923101
a_2	2.795275751639167
a_3	0.858455887399655
b_1	1
b_4	1
c_1	1
c_2	1
c_3	1
g_1	0.022954073145617

   


DYNAMIC RANGE SCALING

- ✖ Refer to dsdemo3.m
- ✖ `scaleABCD(, , , [x1, ..., xL], , ,)`
- ✖ $x\text{lim} = [x_1, \dots, x_L]$
- ✖ Iteratively adjust values of $x\text{lim}$ to change
[a, b, c, g] coefficients
- ✖ Examine [a, b, c, g] coefficients for integer ratio
quantization → *Eases switched-capacitor
integrator ratios, and matching*

D.R. SCALING RESULTS

 DYNAMIC RANGE SCALED MODULATOR COEFFICIENTS





	Full Precision	Quantized
a_1	1.587037247907706	17/11
a_2	0.854112035223079	9/11
a_3	0.196729474195754	2/11
b_1	0.363636363636364	8/22
b_4	0.2	2.2/11
c_1	0.909090909090909	20/22
c_2	1.8	9/5
c_3	1.333333333333333	4/3
g_1	0.017215554859213	1/60


- ✖ Maximize State Amplitude to minimize distortion
- ✖ Leave some margin

FILTER DESIGN

  - ✖ MATLAB fdatool
 - + Multirate filter (CIC Decimator)
 - + Design Post Filter
 - + Quantize Coeff.
 - ✖ Fixed-point Math
- ✖ Export to Script or Simulink



SD TOOLBOX 2 BLOCKS

 

SD Toolbox 2.0
Copyright 2004
University of Pavia, Italy

This library is free software; you can redistribute it and/or modify it under the terms of the GNU Lesser General Public License as published by the Free Software Foundation; either version 2.1 of the License, or (at your option) any later version. This library is distributed in the hope that it will be useful, but WITHOUT ANY WARRANTY; without even the implied warranty of MERCHANTABILITY or FITNESS FOR A PARTICULAR PURPOSE.


See the [GNU Lesser General Public License](#) for more details.

You should have received a copy of the GNU Lesser General Public License along with this library; if not, write to the Free Software Foundation, Inc., 59 Temple Place, Suite 330, Boston, MA 02111-1307 USA.)

- ✖ Use as starting point
- ✖ Noise Sources
 - + kT/C Noise
 - + White Noise

- ✖ Real Integrator
 - + Finite Gain
 - + Gain Bandwidth
 - + Slew Rate


SIMULINK MODEL – 3RD ORDER CIFF

 




- ✖ Finite Gain & BW, SR
- ✖ DAC & Cap Mismatch
- ✖ Analog Noise
- ✖ Digital Round-off Errors
- ✖ Create MATLAB script to control Simulink model

SIMULINK BLOCK & SIMULATION PARAMS

 - ✖ Initialize variables in MATLAB script
- ✖ Choose “Accelerator” to speedup simulation
 - + Must have C/C++
- ✖ Configuration Parameters → Solver options → variable step, discrete (no continuous states)




SWITCHED-CAPACITOR IMPLEMENTATION

   


FINITE GAIN – SIMULINK

 - ✖ Folding of quantization error
- ✖ Shifts NTF zero locations




SLEW RATE – SIMULINK

 - ✖ Based on max integrator step size
- ✖ Abrupt impact on integrator settling
- ✖ Interdependence with GBW




GAIN BANDWIDTH – SIMULINK

 - ✖ Can cause increased in-band quantization noise
- ✖ GBW of the order of F_S
- ✖ Interdependence with Slew Rate




DAC MISMATCH AND DWA – SIMULINK

 - ✖ Examine dsdemo5.m
- ✖ Mismatch causes distortion
- ✖ DWA high-pass filters mismatch




DIGITAL ROUND-OFF ERROR – SIMULINK

 - ✖ MATLAB fdatool
- ✖ Quantize Coeff.
- ✖ Internal Precision
- ✖ Output Fraction Bits
- ✖ Code into MATLAB
→ Easier Testing



MODULATOR SPECTRUM

 - ✖ Includes non-ideal effects
- ✖ DWA active (8-bit matching)
- ✖ Average of 32 runs, 2^{16} points
 - + Initialize Integrator States Randomly




ADC SPECTRUM

- ✖ PSD of Decimated and Filtered Output
- ✖ $F_{BW} = 20 \text{ MHz}$

DESIGN SPECIFICATIONS

Signal Bandwidth	0 – 20 MHz
Clock Frequency	$\leq 640 \text{ MHz}$
Min Unit Cap	25 fF
Total Capacitance	6.71 pF
Amplifier DC Gain	100 V/V
Amplifier SR	5.2 V/ns
Amplifier GBW	1.0 GHz
DAC 1- σ	0.39%
Total Word Length	21 bits
Fraction Length	8 bits
ENOB @ 156.25 kHz	11.69 bits
ENOB @ 20 MHz	11.36 bits
Power Supply	1V
Input Signal Range	$\pm 1V_{diff}$

 

PROJECT SUGGESTIONS

- ✖ *Start Early!*
- ✖ Understand DStoolbox dsdemo's
- ✖ Write DStoolbox Script
 - + Fully test before starting Simulink and Cadence!!!
- ✖ Build Transistor-based Switches in Cadence
 - + Helps mitigate convergence issues
- ✖ Understand SD Toolbox 2 (Simulink) and adapt to your system