

ECE 580

HOMEWORK 1

Due Oct. 15, 2014

1. Show that $Z(s) = (2s + 3)/(s + 1)$ is a positive real function. Find a circuit which realizes it.

2. Find a simple model in terms of impedances and controlled sources for the hybrid parameters h_{11} , h_{12} , h_{21} and h_{22} .