

MIDTERM EXAMINATION

Open Book


October 27, 2014

Prof. G. Temes

- Find a T network equivalent of the physical transformer. What are the element values of the new circuit in terms of L_1 , L_2 and M ?
- Find the ABCD matrix of the circuit.
- What is y_{11} of the transformer if it is closely coupled?

$$V_1 = sL_1 I_1 + sMI_2$$

$$V_2 = sMI_1 + sL_2 I_2$$

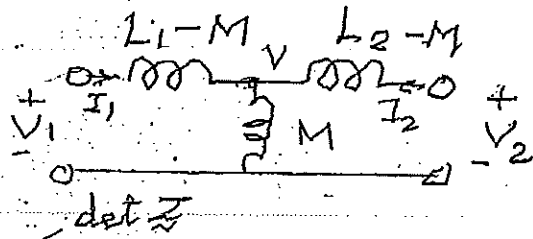


$$\underline{T} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} z_{11}/z_{21} & z_{12}/z_{21} \\ 1/z_{21} & z_{22}/z_{21} \end{bmatrix} = \begin{bmatrix} L_1/M & \frac{s}{M}(L_1 L_2 - M^2) \\ 1/sM & L_2/M \end{bmatrix}$$

$$\text{check: } \det \underline{T} = L_1 L_2 / M^2 - (L_1 L_2 - M^2) / M^2 = 1$$


$$y_{11} = 1/z_{11} = sL_2 / [s^2(L_1 L_2 - M^2)] = 1/[sL_1(1-k^2)]$$

$k^2 = M^2/L_1 L_2$

For $k \rightarrow 1$, $1/y_{11} \rightarrow 0$. All $y_{ij} \rightarrow \infty$.

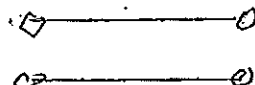The two-port becomes 

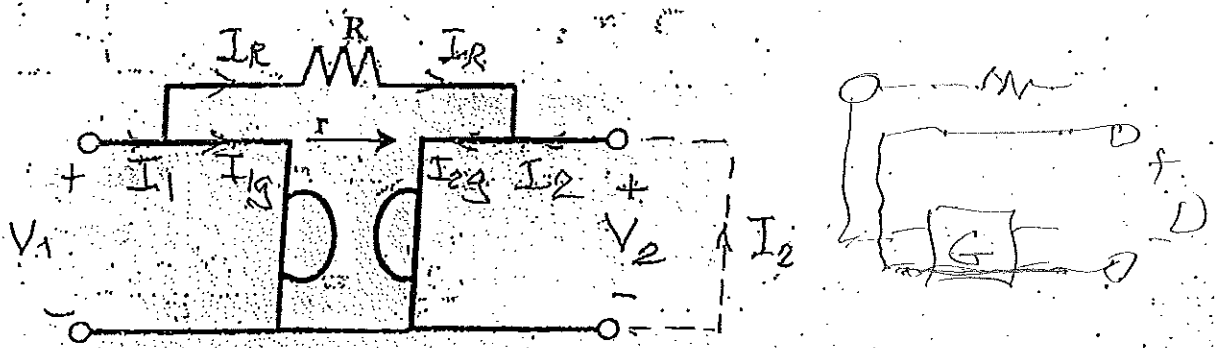2. Find the admittance matrix \underline{Y} of the two-port shown below.



$$V_1 = -r I_{2g}$$

$$V_2 = r I_{1g}$$

$$\underline{Y}_{11} = \left(\frac{I_1}{V_1} \right)_{\substack{V_2=0 \\ I_{2g}=0}} = \left(\frac{I_R}{V_1} \right) = 1/R = \underline{Y}_{22}$$

$$\underline{Y}_{21} = \left(\frac{I_2}{V_1} \right)_{V_2=0} = I_{2g} - I_R = -1/r - 1/R$$

$$\underline{Y}_{12} = (\underline{Y}_{21}) r \rightarrow -r = 1/r - 1/R$$

$$\underline{Y} = \begin{bmatrix} 1/R & 1/r - 1/R \\ -1/r - 1/R & 1/R \end{bmatrix}$$

Can also break the two-port into the parallel combination of \underline{Y}_R & \underline{Y}_G

$$\underline{Y}_R = \begin{bmatrix} G & -G \\ -G & G \end{bmatrix}, \quad \underline{Y}_G = \begin{bmatrix} 0 & g \\ -g & 0 \end{bmatrix} \quad g = 1/r, \quad G = 1/R$$

$$\underline{Y} = \underline{Y}_R + \underline{Y}_G$$