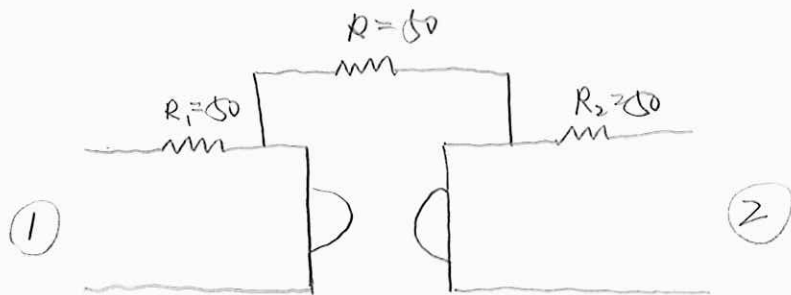


Solutions:

1. Terminated Gyration:



a. Scattering Matrix

For the two port Gyrator without Termination

$$Y = \begin{bmatrix} \frac{1}{R} & \frac{1}{R} - \frac{1}{R} \\ -\frac{1}{R} - \frac{1}{R} & \frac{1}{R} \end{bmatrix}$$

$$z = R \begin{bmatrix} \frac{1}{R} & 0 \\ -\frac{2}{R} & \frac{1}{R} \end{bmatrix} \Rightarrow Z = Y^{-1} = \frac{1}{\det Y} \begin{bmatrix} \frac{1}{R} & 0 \\ \frac{2}{R} & \frac{1}{R} \end{bmatrix} = \begin{bmatrix} R & 0 \\ 2R & R \end{bmatrix}$$

After Terminated by R_1 & R_2 ,

the Argument Z matrix becomes:

$$Z_a = Z + \begin{bmatrix} R_1 & 0 \\ 0 & R_2 \end{bmatrix} = \begin{bmatrix} R+R_1 & 0 \\ 2R & R+R_2 \end{bmatrix} = \begin{bmatrix} 2R & 0 \\ 2R & 2R \end{bmatrix}$$

$$Z_{an} = \begin{bmatrix} 2 & 0 \\ 2 & 2 \end{bmatrix}$$

$$\text{Thus } Y_{an} = \frac{1}{\det Z_{an}} \begin{bmatrix} 2 & 0 \\ -2 & 2 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & 0 \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$


$$\Rightarrow S = I - 2Y_{an} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$

b. $S_{21} = 1 \Rightarrow$ No Power loss inbetween the two ports.

$S_{11} = S_{22} = 0 \Rightarrow$ No termination reflections

$S_{12} = 0 \Rightarrow$ Ideal reverse isolation from 2 to 1

(2)

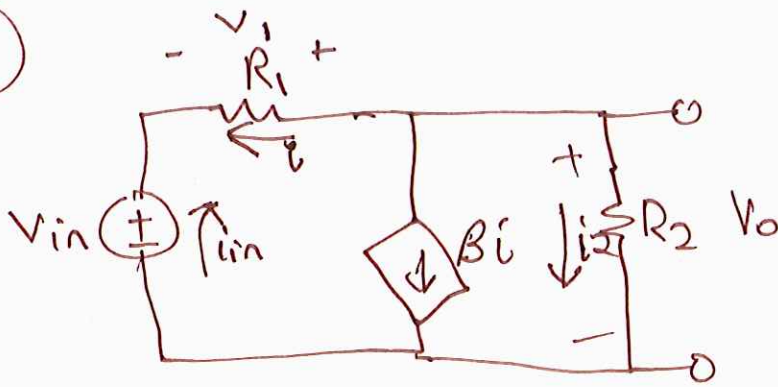

$$V_{in} = 5V$$

$$R_1 = 2K$$

$$R_2 = 4K$$

$$\beta = 4$$

* Normal Circuit Parameters by KCL

$$V_o = R_2 i_2 \quad i_2 = -(\beta + 1)i_1 \quad i_1 = \frac{V_o - V_{in}}{R_1}$$

$$V_o = -\frac{R_2(\beta + 1)(V_o - V_{in})}{R_1} \Rightarrow V_o \left(1 + \frac{R_2(\beta + 1)}{R_1} \right) = \frac{V_{in} R_2(\beta + 1)}{R_1}$$

$$\left\{ V_o = \frac{V_{in} R_2(\beta + 1)}{R_1 \left(1 + \frac{R_2(\beta + 1)}{R_1} \right)} = \frac{V_{in} R_2(\beta + 1)}{R_1 + (\beta + 1)R_2} \right\} \quad \text{* similar to voltage divider}$$

$$R_{in} = \frac{V_{in}}{i_{in}} \quad i_{in} = -i_1 = \frac{V_{in} - V_o}{R_1} = \frac{V_{in}}{R_1} - \frac{V_{in} R_2(\beta + 1)}{R_1 + R_2(\beta + 1)}$$

$$i_{in} = V_{in} \left[\frac{R_1 + R_2(\beta + 1) - R_2(\beta + 1)}{R_1(R_1 + R_2(\beta + 1))} \right] = V_{in} \left[\frac{1}{R_1 + R_2(\beta + 1)} \right]$$

$$\left[\frac{V_{in} [R_1 + R_2(\beta + 1)]}{V_{in}} \right] R_{in} = R_1 + R_2(\beta + 1)$$

Sensitivity for R_{in} due to R_1, R_2, β is very straight Bruar derivative

$$\left[\frac{\partial R_{in}}{\partial R_1} = 1 \frac{\Omega}{\Omega} \quad \frac{\partial R_{in}}{\partial R_2} = \beta + 1 = 5 \frac{\Omega}{\Omega} \quad \frac{\partial R_{in}}{\partial \beta} = R_2 = 4K \frac{\Omega}{\text{unit}} \right]$$

For first order Taylor series approximation $\frac{\partial V_o}{\partial R_1}$, $\frac{\partial V_o}{\partial R_2}$, $\frac{\partial V_o}{\partial \beta}$ are still relatively easy to compute with Quotient rule


$$\frac{\partial V_o}{\partial R_1} = \frac{0 - V_{in}(\beta+1)R_2 \cdot 1}{[R_1 + R_2(\beta+1)]^2} = -\frac{V_{in}(\beta+1)R_2}{[R_1 + R_2(\beta+1)]^2} \approx -\frac{206.6 \mu V}{\Omega}$$

$$\frac{\partial V_o}{\partial R_2} = \frac{V_{in}(\beta+1)(R_1 + R_2(\beta+1)) - V_{in}R_2(\beta+1)(\beta+1)}{[R_1 + R_2(\beta+1)]^2} = \frac{V_{in}R_1(\beta+1)}{[R_1 + R_2(\beta+1)]^2} = \frac{103.3 \mu V}{\Omega}$$

$$\frac{\partial V_o}{\partial \beta} = \frac{V_{in}R_2[R_1 + R_2(\beta+1)] - V_{in}R_2(\beta+1)R_2}{[R_1 + R_2(\beta+1)]^2} = \frac{V_{in}R_2R_1}{[R_1 + R_2(\beta+1)]^2} \approx \frac{0.826 V}{\text{unit}}$$

Can also be solved using adjoint network

Adjoint Network

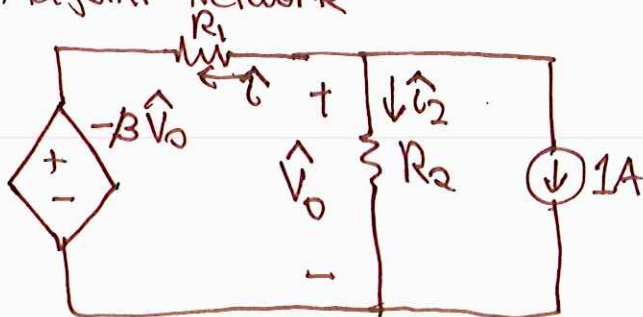

By Tellegen's

$$\frac{\partial V_o}{\partial R_1} = S_{R_1} = -\hat{U} \hat{i}$$

$$\frac{\partial V_o}{\partial R_2} = S_{R_2} = -\hat{U}_2 \hat{i}_2$$

$$\frac{\partial V_o}{\partial \beta} = S_{\beta} = \hat{V}_o \cdot \hat{i}$$

From physical network

$$\hat{i}_2 = \frac{\hat{V}_o}{R_2} = \frac{50}{11.4e^3} = 1.14 \mu A$$

$$\hat{i} = \frac{\hat{V}_o - V_{in}}{R_1} = \left(\frac{50}{11} - 5 \right) \frac{1}{2e^3} \approx -227 \mu A$$

$$\hat{V}_o = -\left[\frac{\hat{V}_o(\beta+1)}{R_1} + 1 \right] R_2 \Rightarrow \hat{V}_o \left(1 + \frac{(\beta+1)R_2}{R_1} \right) = -R_2 \Rightarrow \hat{V}_o = \frac{-R_2}{1 + \frac{(\beta+1)R_2}{R_1}}$$

Solving Adjoint

$$\hat{V}_o = \hat{U}_2 \cdot R_2 \quad \boxed{\hat{U}_2 = -(\hat{U} + 1)}$$

$$\hat{U} = \frac{\hat{V}_o + \beta \hat{V}_o}{R_1} = \frac{\hat{V}_o(\beta+1)}{R_1} = \hat{U}$$

$$\hat{V}_0 = -363.7_{11} \text{ V} \quad \hat{I}_1 = -.909 \text{ A} \quad \hat{I}_2 = -.0909 \text{ A}$$

$$S_{R1} = -\hat{V}_1 i = -(-.909 \text{ A})(-227 \mu\text{A}) = \boxed{-206 \mu\text{W} = S_{R1}}$$

$$S_{R2} = -\hat{V}_2 i_2 = -(-.0909 \text{ A})(1.14 \text{ mA}) = \boxed{103.6 \mu\text{W} = S_{R2}}$$

~~S_{R3}~~

$$S_B = \hat{V}_0 \cdot i = (-363.7_{11} \text{ V})(-227 \mu\text{A}) = \boxed{.0825 = S_B [\text{V}\cdot\text{unit}]}$$

A Results between two methods are closely matched