

# ECE 580

## HOMEWORK 1


Due Oct. 15, 2015

1. Find the admittance and impedance parameters of a gyrator with gyration resistance  $R$ .

$$Y_g = \begin{bmatrix} 0 & 1/r \\ -1/r & 0 \end{bmatrix}$$

$$Z_g = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix}$$

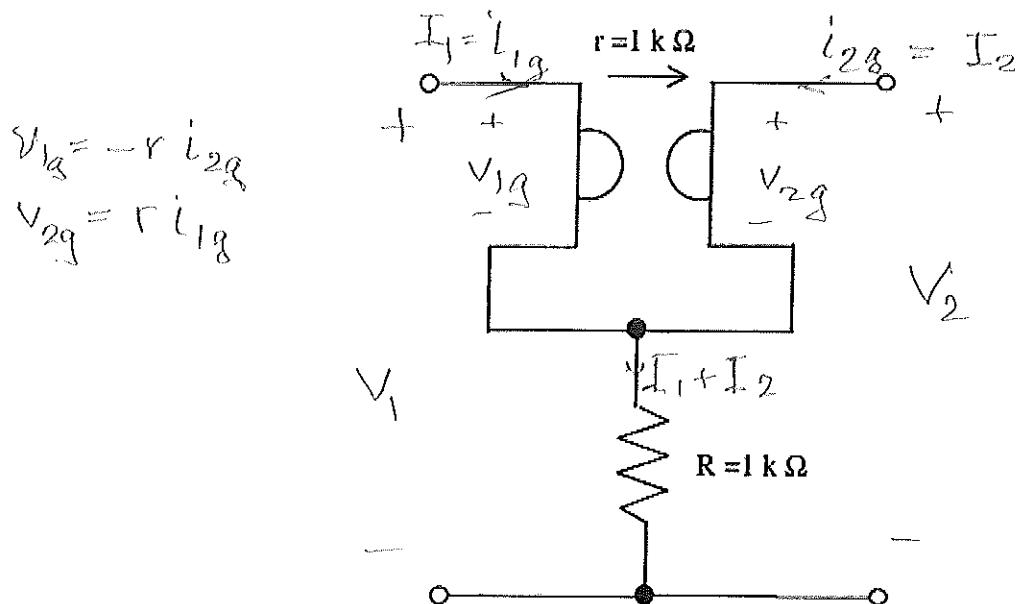2. Find the impedance parameters of the circuit shown below.



$$V_1 = -r I_2 + R(I_1 + I_2) = RI_1 + (R-r)I_2$$

$$V_2 = r I_1 + R(I_1 + I_2) = (R+r)I_1 + RI_2$$