
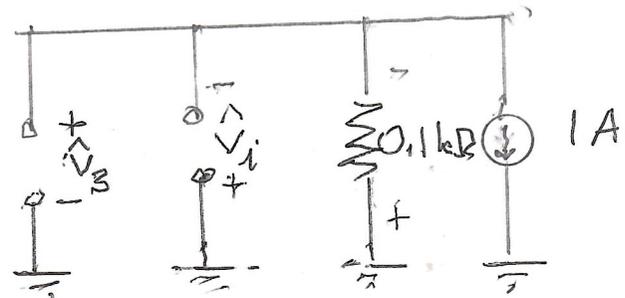
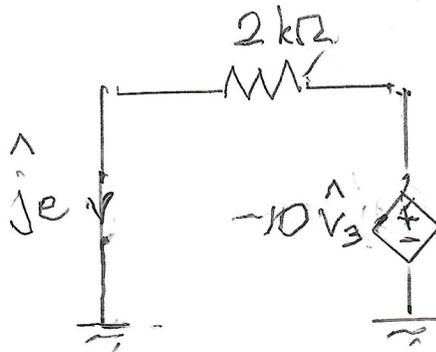
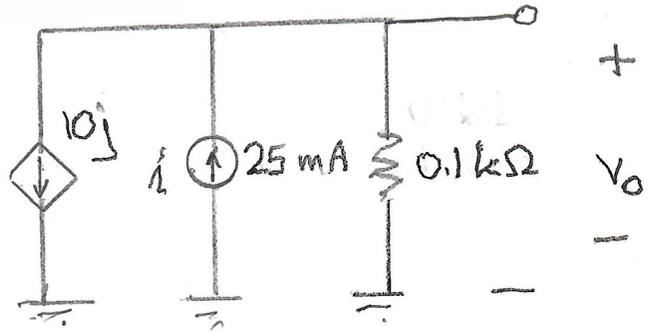


580 HW 3

1.


N:

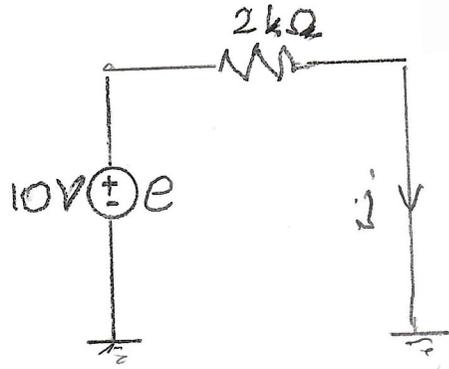

$$V_0 = -\hat{j}e \cdot e + \hat{V}_i \cdot i = -5 + 2.5 = -2.5 \text{ V} = V_{TH}$$

$$\hat{V}_i = 100 = -\hat{V}_3, \quad \hat{j}e = +0.5$$
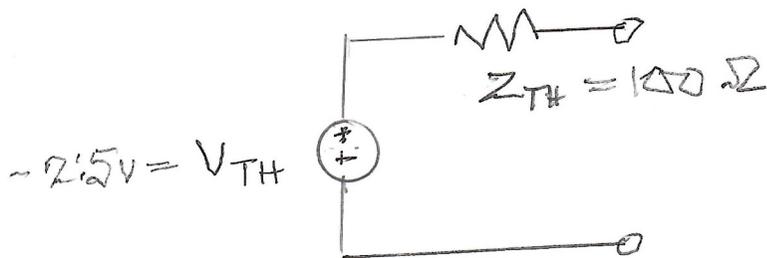
$$\hat{V}_0 = \hat{V}_3 = -100 \text{ V} = Z_{TH}$$




Check: in N

$$i = 5 \text{ mA}, \quad V_0 = 100 (0.025 - 0.05) = -2.5 \text{ V}$$


$$\text{Short circuit current} = -0.025 \text{ A}$$

$$Z_{TH} = 100 \Omega$$

2.

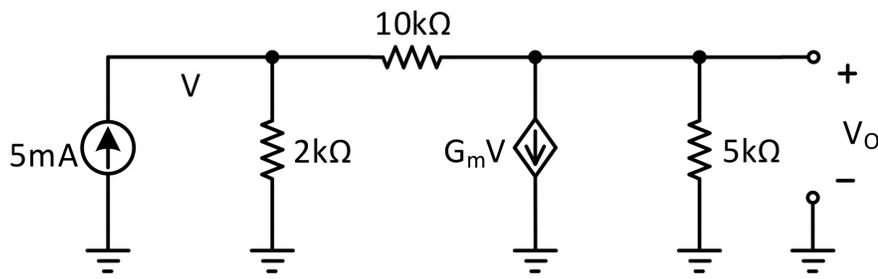

Adjoint:

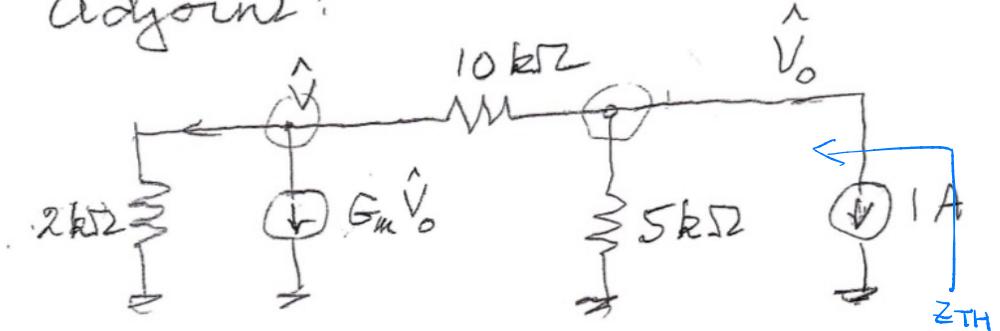

$$0.5\hat{V} + 3\hat{V}_0 + 0.1(\hat{V} - \hat{V}_0) = 0 \quad (1)$$

$$2.9\hat{V}_0 = -0.6\hat{V},$$

$$0.1(\hat{V} - \hat{V}_0) = 10^3 + 0.2\hat{V}_0 \quad (2)$$

$$0.1\hat{V} = 10^3 + 0.3\hat{V}_0$$

$$0.1 \cdot \frac{2.9}{-0.6} \hat{V}_0 = 10^3 + 0.3\hat{V}_0$$


$$-\left(\frac{2.9}{6} + 0.3\right)\hat{V}_0 = 10^3$$

$$-\frac{4.7}{6}\hat{V}_0 = 10^3, \quad \hat{V}_0 = -\frac{6000}{4.7} \approx -1276.6 \text{ V}$$

$$\hat{V} = -\frac{2.9}{0.6}\hat{V}_0 = \frac{29000}{4.7} \text{ V}$$


$$V_0 = -i \cdot \hat{V} = -5 \text{ mA} \cdot \frac{29000}{4.7} \text{ V/A} \approx -30.85 \text{ V} = V_{TH}$$
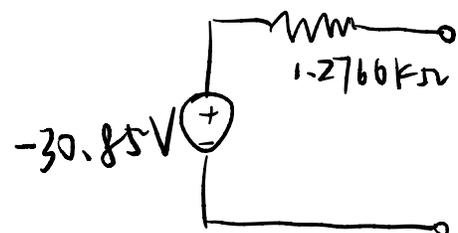
$$Z_{TH} = \frac{\hat{V}_0}{-1 \text{ A}} = 1.2766 \text{ k}\Omega$$




$Z'$

(OR, if you are using this network)

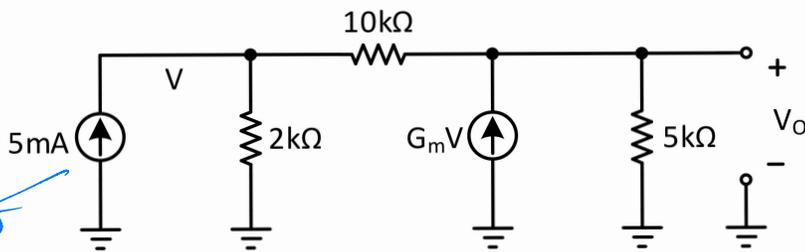

Adjoint:

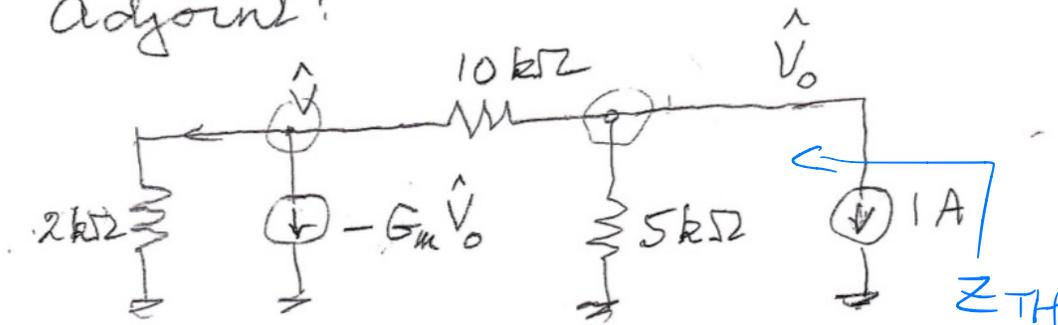

$$-\frac{\hat{V}}{2} + 3\hat{V}_0 + 0.1(\hat{V}_0 - \hat{V}) = 0$$

$$3.1\hat{V}_0 = 0.6\hat{V}$$

$$0.1(\hat{V} - \hat{V}_0) = 10^3 + 0.2\hat{V}_0$$

$$0.1\hat{V} = 10^3 + 0.3\hat{V}_0$$

$$0.1 \frac{3.1}{0.6} \hat{V}_0 = 10^3 + 0.3\hat{V}_0$$

$$\left(\frac{3.1}{6} - 0.3\right)\hat{V}_0 = 10^3$$


$$\frac{1.3}{6}\hat{V}_0 = 10^3, \quad \hat{V}_0 = \frac{6000}{1.3} \approx 4615.4 \text{ V}$$

$$\hat{V} = \frac{31}{6}\hat{V}_0 = \frac{310000}{13} \text{ V}$$


$$V_0 = -i \cdot \hat{V} = -5 \text{ mA} \cdot \frac{310000}{13} \text{ V/A} \approx -119.23 \text{ V} = V_{TH}$$

$$Z_{TH} = \frac{\hat{V}_0}{-1 \text{ A}} = -4.6154 \text{ k}\Omega$$

$$-119.23 \text{ V} = V_{TH}$$

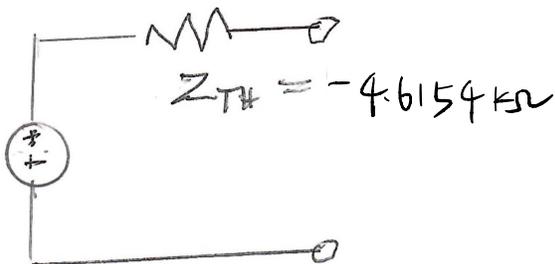

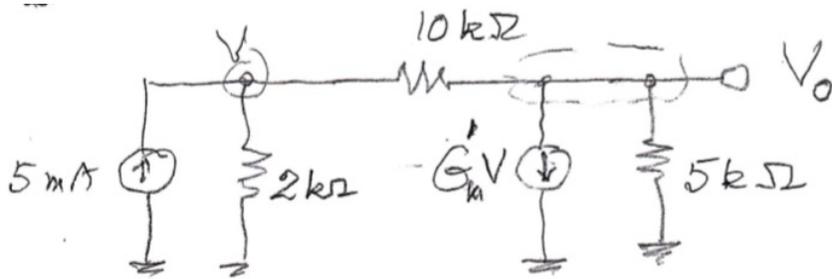2' Another approach for obtaining  $V_0$ : solving the original circuit directly



$$G_{kk} = 3 \text{ mS}, \quad G_m' = -G_m$$

$$\frac{\partial V_0}{\partial G_m} = ? \quad (5.325 \times 10^4 \text{ V/S})$$

$$5 + 0.1(V_0 - V) = 0.5 \text{ V}$$

$$0.1(V - V_0) + G_m V = 0.2 V_0$$

$$V_0 = 10 [0.6 \text{ V} - 5] = 6 \text{ V} - 50$$

$$V_0 = \frac{1}{0.3} [0.1 \text{ V} + G_m V] = (1 + 10G_m) V / 3$$

$$6 \text{ V} - 50 = \frac{31}{3} \text{ V}$$

$$V = \frac{50}{-13/3} = -\frac{150}{13} \approx -11.538 \text{ V}$$

$$V_0 = -\frac{900}{13} - 50 \approx -119.23 \text{ V}$$

Extra derivation on sensitivity of  $V_0$  to  $dG_m$ .

$$\frac{\partial V_0}{\partial G_m'} = V \hat{V}_0 = -\frac{150}{13} \times \frac{6 \times 10^4}{13} = -\frac{9 \times 10^6}{169} \approx -53.25 \times 10^3 \frac{\text{V}}{\text{S}}$$

$$\frac{\partial V_0}{\partial G_m} = +53.25 \text{ V/μS}$$