

FINAL EXAMINATION

December 8, 2010, 2 – 3:30 pm


Prof. G.C. Temes

Open book

1. A Butterworth filter has been designed for a passband ripple of 0.15 dB and a minimum stopband attenuation of 45 dB. Now it needs to be redesigned for a new ^{pass} stopband ripple of 0.10 dB, with the same order and selectivity. What will be the new value of the minimum stopband loss?

2. a. Find the adjoint network of a gyrator with resistance R . Express the sensitivity to a change in R in terms of the gyrator currents in the physical and adjoint networks.


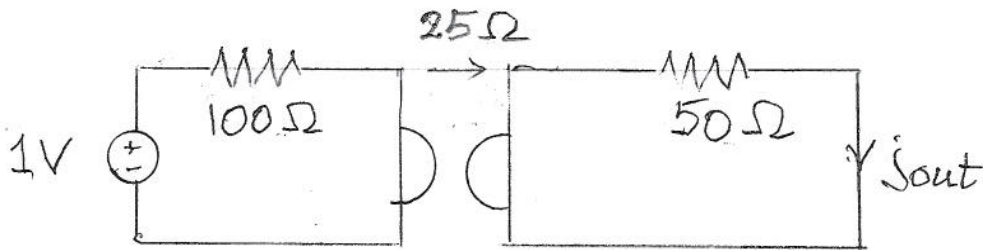
b. Find the sensitivities of the output current j_{out} to variations of the terminations and the gyration resistance R in the circuit shown.



3. The two-ports shown below are equivalent. Find

a. the impedances Z_a , Z_b , and Z_c ;

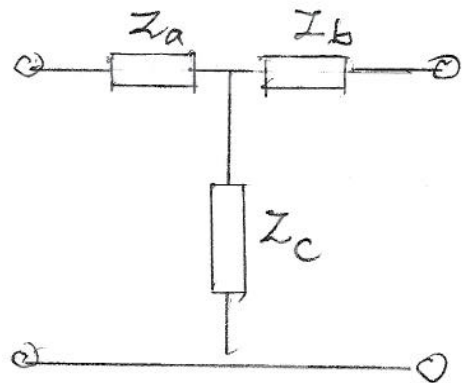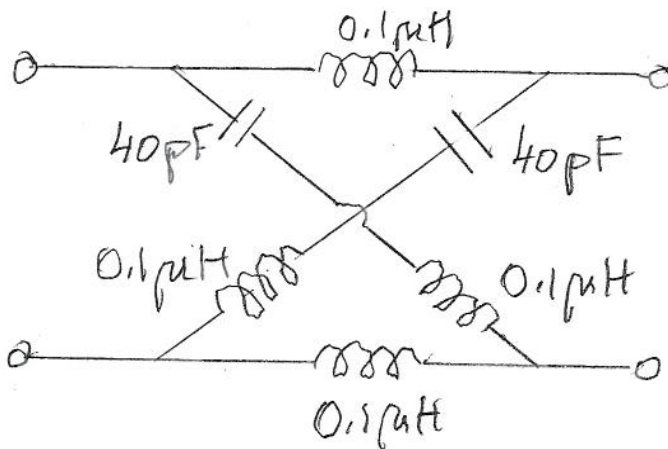b. the scattering matrix at $\omega_1 = 500 \text{ Mrad/s}$, when the circuit is terminated by two 50 ohm resistors.



FINAL EXAMINATION

December 8, 2010, 2 – 3:30 pm

Prof. G.C. Temes

Open book

pass

1. A Butterworth filter has been designed for a passband ripple of 0.15 dB and a minimum stopband attenuation of 45 dB. Now it needs to be redesigned for a new ~~stopband~~ ripple of 0.10 dB, *with the same order and selectivity*. What will be the new value of the minimum stopband loss?

1. k_1^2 must remain unchanged, so

$$k_1^2 = \frac{10^{\alpha_p/10} - 1}{10^{\alpha_{s1}/10} - 1} = \frac{10^{0.015} - 1}{10^{4.5} - 1} = \frac{10^{0.01} - 1}{10^{\alpha_{s2}/10} - 1}$$

$$10^{\alpha_{s2}/10} = X + \frac{10^{0.01} - 1}{10^{0.015} - 1} (10^{4.5} - X)$$


$$\alpha_{s2} \approx 45 - 1.77 = 43.23 \text{ dB}$$

CAMRAD




2. a. Find the adjoint network of a gyrator with resistance R . Express the sensitivity to a change in R in terms of the gyrator currents in the physical and adjoint networks.

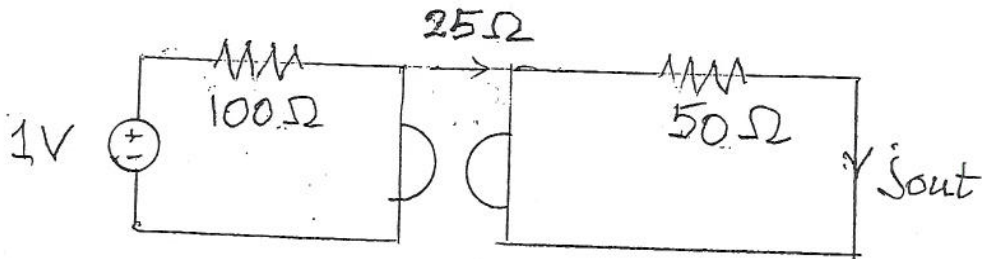
b. Find the sensitivities of the output current j_{out} to variations of the terminations and the gyration resistance R in the circuit shown.



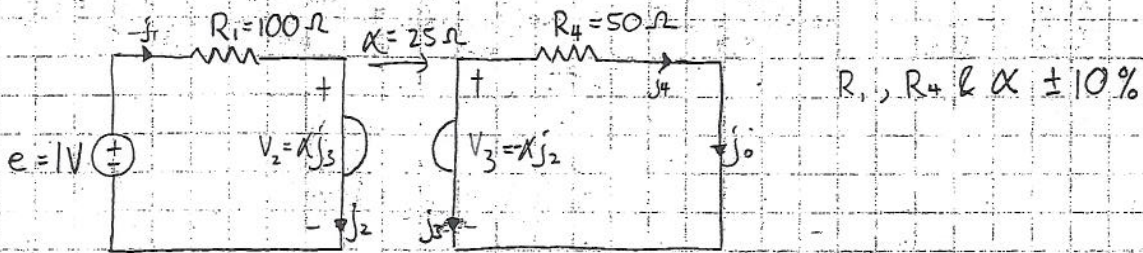~~$j_o = 15 \text{ mA}$ when $0.10 \text{ mA} = j_o = 15 \text{ mA}$~~



And the corresponding adjoint network

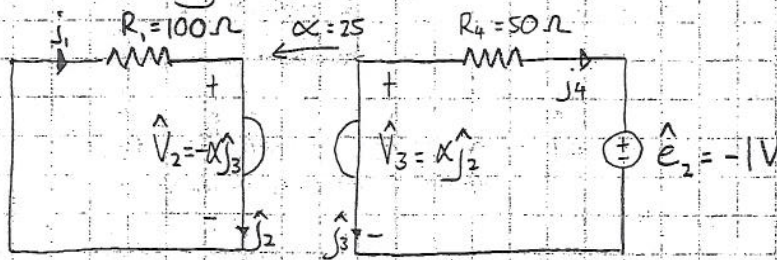

From the circuit,

$$j_1 = j_2 = \frac{e - V_2}{R_1} = \frac{1 - 25j_3}{100} = \frac{1}{100} - \frac{j_3}{4} \quad (1)$$

$$j_3 = -j_4 = \frac{-V_3}{R_4} = \frac{-25j_2}{50} = \frac{-j_2}{2} \quad (2)$$

$$j_3 = \frac{j_2}{2} = \frac{1}{2} \left(\frac{1}{100} - \frac{j_3}{4} \right)$$

$$2j_3 = \frac{1}{100} - \frac{j_3}{4}$$

$$j_3 = \frac{1}{225} \text{ A}$$

$$\Rightarrow j_4 = -j_3 = -\frac{1}{225} \text{ A}$$

$$j_2 = 2j_3 = \frac{2}{225} \text{ A} = j_1$$

From the adjoint network,

$$\hat{j}_1 = \hat{j}_2 = \frac{-\hat{V}_2}{R_1} = \frac{\alpha \hat{j}_3}{R_1} = \frac{25 \hat{j}_3}{100} = \frac{1}{4} \hat{j}_3$$

$$\hat{j}_3 = -\hat{j}_4 = \frac{\hat{e}_2 - \hat{V}_3}{R_4} = \frac{\hat{e}_2 - \alpha \hat{j}_2}{R_4} = \frac{-1 - 25 \hat{j}_2}{50} = -\frac{1}{50} - \frac{1}{2} \hat{j}_2$$

$$\Rightarrow j_2 = \frac{1}{4} \left(-\frac{1}{50} - \frac{1}{2} \hat{j}_2 \right)$$

$$4.5 j_2 = -\frac{1}{50}$$

$$j_2 = -\frac{1}{225} \text{ A} = \hat{j}_1$$

$$j_3 = 4 j_2 = -\frac{4}{225} \text{ A} = \hat{j}_4$$

To find the sensitivities,

$$\frac{\delta j_0}{\delta R_1} = -\hat{j}_1 j_1 = -\left(-\frac{1}{225} \right) \left(\frac{2}{225} \right) = \frac{2}{50625} \text{ A}/\Omega$$

$$\frac{\delta j_0}{\delta R_4} = -\hat{j}_4 j_4 = -\left(-\frac{4}{225} \right) \left(-\frac{1}{225} \right) = \frac{4}{50625} \text{ A}/\Omega$$

$$\frac{\partial j_o}{\partial \alpha} = + \hat{j}_3 \hat{j}_2 - \hat{j}_2 \hat{j}_3 = + \left(-\frac{4}{225}\right) \left(\frac{2}{225}\right) - \left(-\frac{1}{225}\right) \left(\frac{1}{225}\right)$$

↑
change in direction of α

$$= \frac{7}{50625} \text{ A}/\Omega$$

Also,

$$\Delta R_{1\max} = 100 \times 0.1 = 10 \Omega$$

$$\Delta R_{4\max} = 50 \times 0.1 = 5 \Omega$$

$$\Delta \alpha_{\max} = 25 \times 0.1 = 2.5 \Omega$$

$$\Rightarrow |\Delta j_o|_{\max} = \left| \frac{\partial j_o}{\partial R_1} \Delta R_{1\max} \right| + \left| \frac{\partial j_o}{\partial R_4} \Delta R_{4\max} \right| + \left| \frac{\partial j_o}{\partial \alpha} \Delta \alpha_{\max} \right|$$

$$= \left(\frac{2}{50625} \cdot 10 \right) + \left(\frac{4}{50625} \cdot 5 \right) + \left(\frac{7}{50625} \cdot 2.5 \right)$$

$$= 1.1358 \times 10^{-3} \text{ A}$$

$$\approx 1.136 \text{ mA}$$

\therefore The range of j_o is $\pm 1.1358 \text{ mA}$

$$j_o = -\frac{1}{225} \text{ A} = -4.44 \text{ mA}$$

$$j_o = -4.444 \pm 1.136 \text{ (mA)}$$



\Rightarrow The range of j_o is

$$\textcircled{+} 5.58 \text{ mA} \leq j_o \leq \textcircled{+} 3.31 \text{ mA}$$



3. The two-ports shown below are equivalent. Find

a. the impedances Z_a , Z_b , and Z_c ;

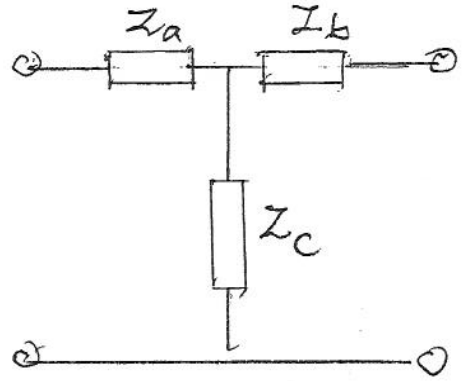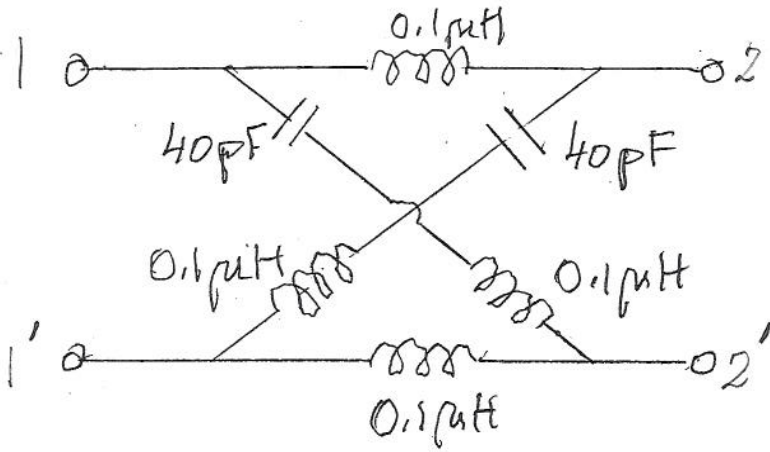b. the scattering matrix at $\omega_1 = 500 \text{ Mrad/s}$, when the circuit is terminated by two 50 ohm resistors.



3.

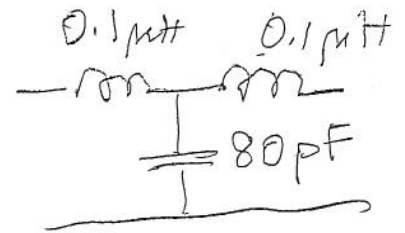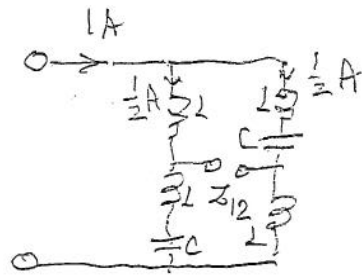

$$Z_{12} = \frac{1}{2} (sL + 1/sC - sL) = 1/s2C = Z_c$$


$$Z_{11} = \frac{1}{2} (s2L + 1/sC) = sL + \frac{1}{s2C} = Z_a + Z_c$$

$$Z_a = sL = Z_b$$

At $500 \text{ Mrad/s} = \omega_1$, $j\omega_1 L = j50 \Omega$

$$\frac{1}{j\omega_1 C} = -j / (5 \times 10^8 \times 4 \times 10^{-11}) = -j50 \Omega$$

So the lattice becomes

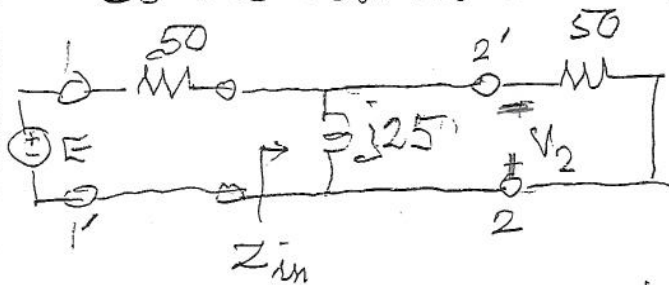


$$Z_{in} = \frac{j25 \times 50}{j25 + 50} = \frac{j50}{2 + j}$$

$$S_{11} = S_{22} = \frac{j50 - 50(2+j)}{j50 + 50(2+j)} = \frac{-100}{100 + 100j} = \frac{-1}{1+j} = \frac{-1+j}{2}$$

$$S_{21} = S_{12} = \frac{-2Z_{in}}{50 + Z_{in}} = \frac{-j100}{50(2+j) + j50} = \frac{-j}{1+j} = \frac{-1+j}{2}$$

Or

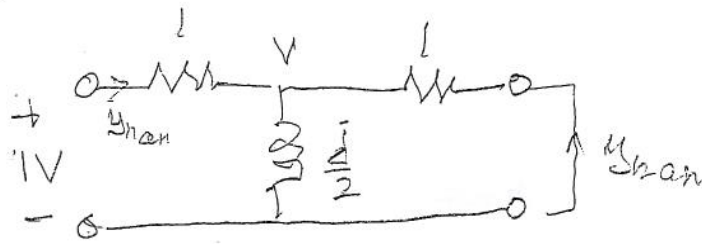


$$Y_{11,an} = Y_{22,an} = \frac{1}{1 + \frac{j/2}{1 + j/2}} = \frac{1 + j/2}{1 + j}$$

$$Y_{12,an} = Y_{21,an} = +V = +Y_{11,an} \frac{j/2}{1 + j/2} = + \frac{j/2}{1 + j}$$

$$S_{11} = S_{22} = 1 - 2Y_{11,an} = 1 - \frac{2 + j}{1 + j} = \frac{-1}{1 + j} = \frac{-1 + j}{2}$$

$$S_{12} = S_{21} = +2Y_{12,an} = \frac{-j}{1 + j} = \frac{1 + j}{2}$$

Note: lattice becomes

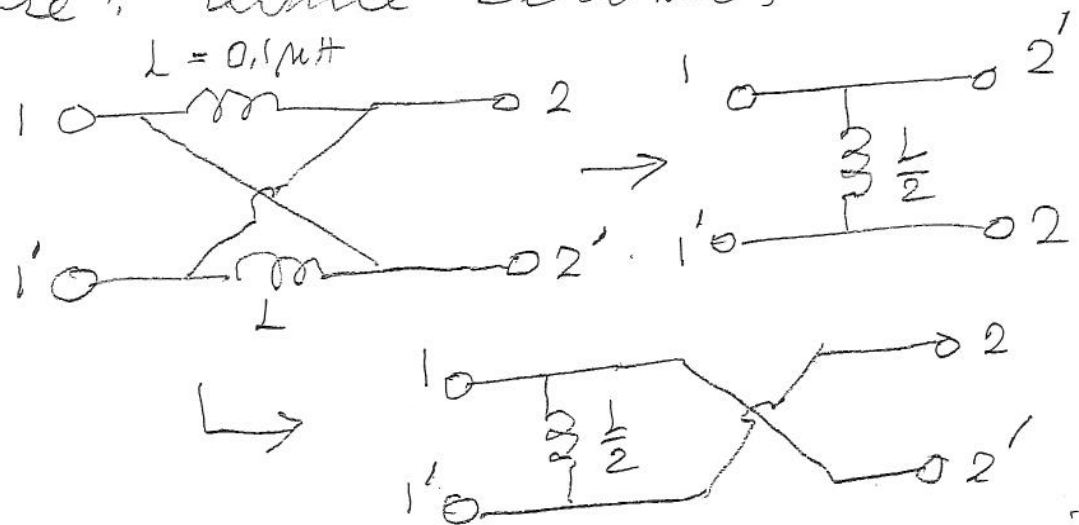

Causing $S_{12} \neq S_{21}$ to change sign!