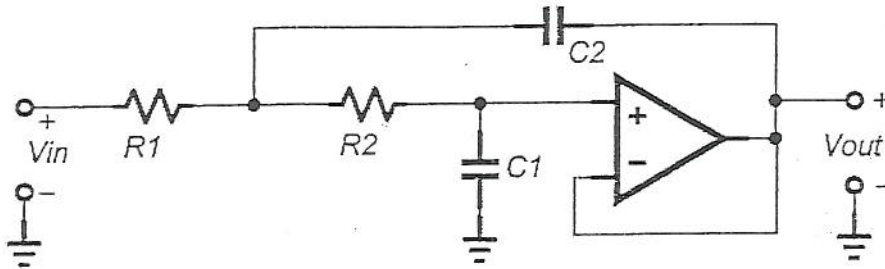



FINAL EXAMINATION
ECE 580

Dec.8, 2011
Open Book

1. In the Sallen-Key filter shown, $R_1 = 25 \text{ kohms}$ and $C_2 = 50 \text{ pF}$. Choose R_2 to maximize the pole Q , and C_1 to achieve $Q_{\text{max}} = 4$.



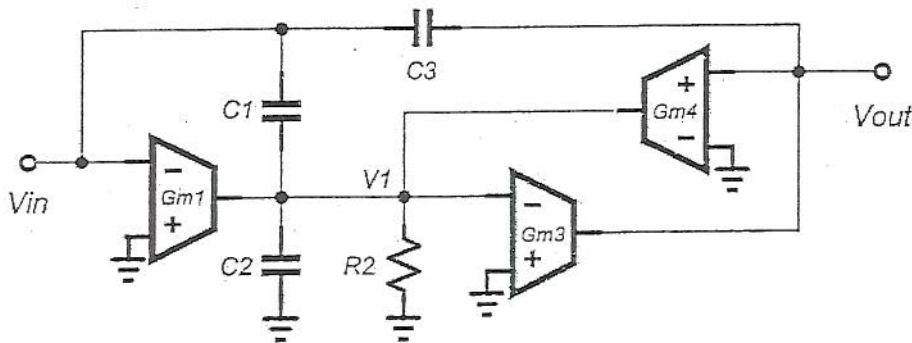2. For the G_m - C filter shown, find
 a. the condition for zeros located on the imaginary axis in the s plane;
 b. the pole frequency and pole Q .



3. Find all transfer functions V_{out}/I_k , $k = 1, 2, 3, 4$ for the circuit shown. All impedances are equal to Z .
 (Hint: use interreciprocity, and analyze the adjoint network from the left!)

