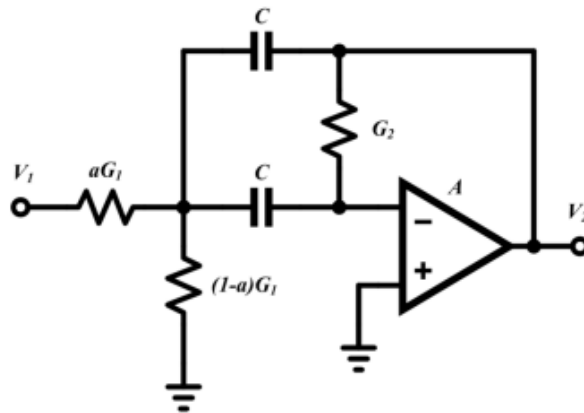


FINAL EXAMINATION

ECE 580

December 7, 2021

1. Design a Delyiannis-Friend filter for a peak frequency of $f_o = 12.5$ kHz, a midband voltage gain of 20, and a pole $Q = 10$. Set $C = 5$ pF.



2. (a) Find the admittance matrix Y of the two-port shown below.
- (b) Find its scattering matrix when it operates between two $1\text{ k}\Omega$ resistors. What are the power transmission properties of the terminated two-port?
- (c) Find the sensitivities of the output voltage V_o to variations of R and r if instead of the $1\text{ k}\Omega$ terminations the two-port is driven by a 1 V voltage source, and its output is open circuited.

