

# ECE 580

## Homework 3

Due November 3, 2021

1. Using inter-reciprocity, find the Thevenin equivalents of the two circuits shown below. Use  $G_m = 3\text{mA/V}$  in (b).

