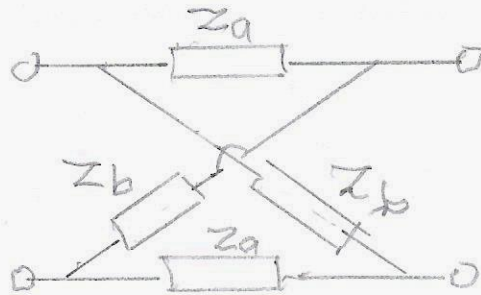


# HOMWORK 1

ECE 580, 2022

1. Find the ABCD parameters of the symmetrical lattice shown.



2. The two two-ports shown below are equivalent. Find the element values of the ladder circuit.

