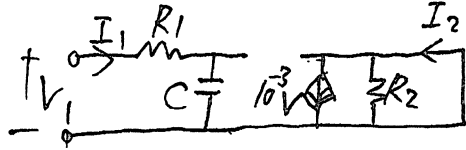


## Midterm Solution

1.

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$



$$Y_{11} = \frac{1}{R_1 + \frac{1}{sC}} = \frac{sC}{sR_1C + 1} = \frac{j\omega C}{j\omega R_1C + 1} = 3 \times 10^{-4} + 2.43 \times 10^{-4} j$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

Since \$R\_2\$ is shorted, \$I\_2 = 10^{-3} V\$

$$= 10^{-3} \cdot V_1 \cdot \frac{1}{R_1 + \frac{1}{sC}}$$

$$\therefore Y_{21} = \frac{I_2}{V_1} = 10^{-3} \frac{1}{R_1 + \frac{1}{sC}}$$

$$= 10^{-3} \frac{1}{sR_1C + 1}$$


$$= 10^{-3} \cdot \frac{1}{j\omega R_1C + 1}$$

$$= 10^{-3} \frac{1}{j 2\pi \times 10^8 \times 2 \times 10^{-3} \times 10^{-12} + 1}$$

$$= \frac{10^{-3}}{j 0.4\pi + 1}$$

$$\doteq 3.8 \times 10^{-4} - 4.8 \times 10^{-4} j$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

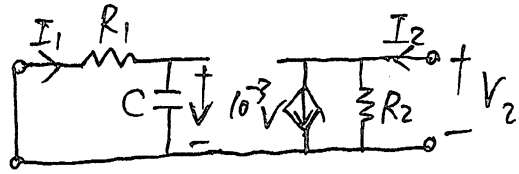

$$\therefore V_1=0 \quad \therefore V=0$$

$$\therefore \frac{I_2}{V_2} = \frac{1}{R_2} = \frac{1}{1 \times 10^3} = 10^{-3}$$

$$\therefore Y_{22} = 10^{-3}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$


$$\therefore V_1=0 \quad \therefore I_1=0$$

$$\therefore Y_{12} = 0$$


$$\therefore Y = \begin{bmatrix} 3 \times 10^{-4} + 2.43 \times 10^{-4} j & 0 \\ 3.8 \times 10^{-4} - 4.8 \times 10^{-4} j & 10^{-3} \end{bmatrix}$$

~~XXXXXXXX~~

2a) We first get

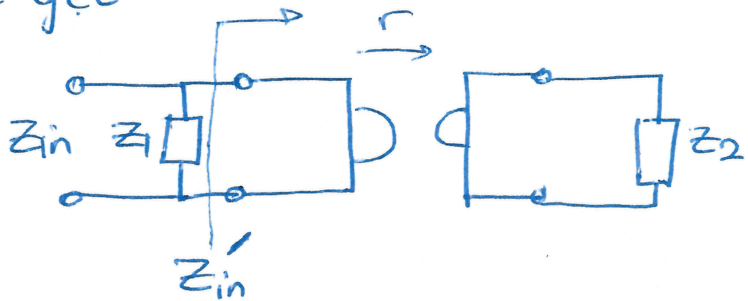

For a gyrator,

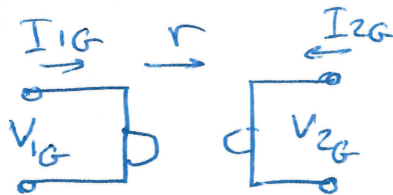

Admittance matrix,

$$Y_G = \begin{bmatrix} 0 & 1/r \\ -1/r & 0 \end{bmatrix}$$

Adding output impedance  $Z_2$ :


~~Y~~  
Solving

$$I_{1G} = \frac{1}{r} V_{2G} \quad (1)$$

$$I_{2G} = -\frac{1}{r} V_{1G} \quad (2) \quad \& \quad I_{2G} = -\frac{V_{2G}}{Z_2} \quad (3)$$

$$\Rightarrow -V_{2G} Y_2 = -\frac{1}{r} V_{1G}$$

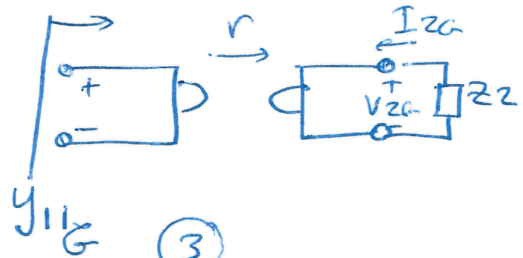
$$V_{2G} = \frac{1}{r Y_2} V_{1G} \quad (4)$$



$$4' \text{ in } \textcircled{1} : I_{IG} = \frac{1}{r} \cdot \frac{1}{rY_2} V_{IG}$$

$$y_{11G} = \frac{I_{IG}}{V_{IG}} = \frac{1}{r^2 Y_2}$$

$\therefore$  For complete network

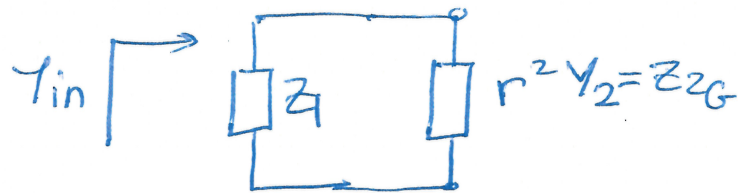

$$Y_{in} = Y_1 + \frac{1}{r^2 Y_2}$$

where  $Y_1 = \frac{1}{R} + sC_1$ ;  ~~$Z$~~   $Y_2 = \frac{1}{R} + sC_2$

$$Y_{in} = \frac{1}{R} + sC_1 + \frac{1}{r^2 \cdot \left[ \frac{1}{R} + sC_2 \right]}$$

$$Z_{in} = Y_{in}^{-1}$$

b)



To find passive realization,

Note that

$$Z_2 = r^2 Y_2$$


$$= r^2 \left( \frac{1}{R} + sC_2 \right)$$

This is equivalent to


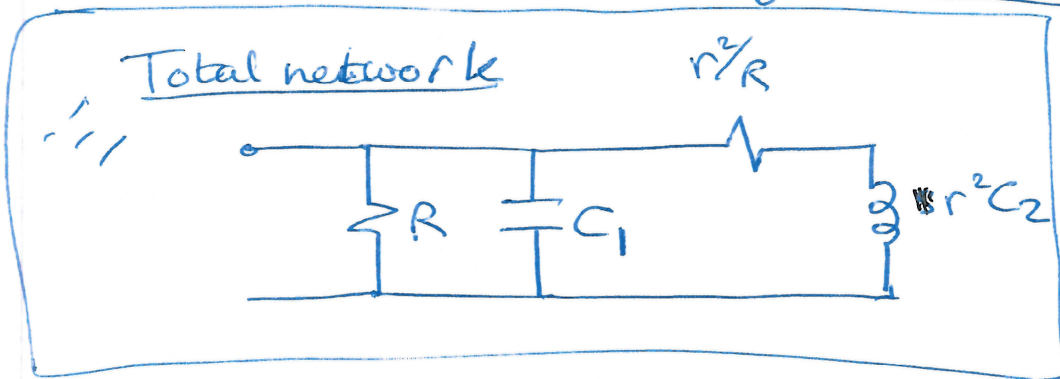
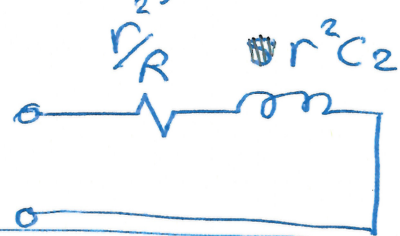


3

a)

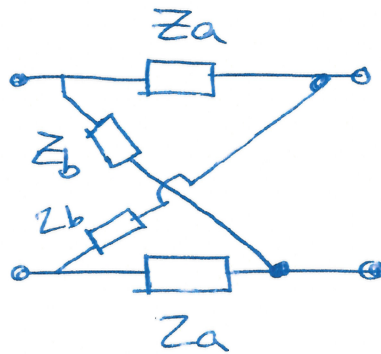

To split the lattice, we can re-draw as

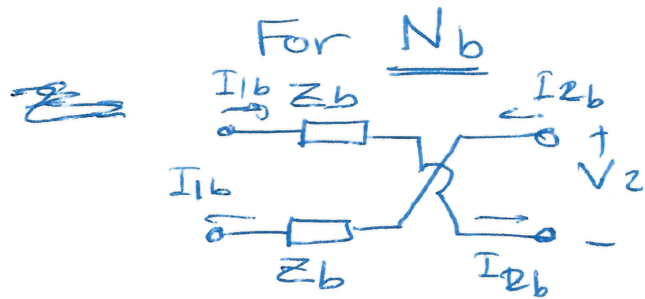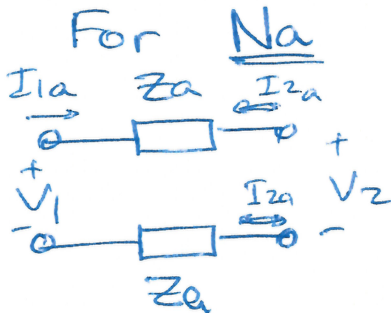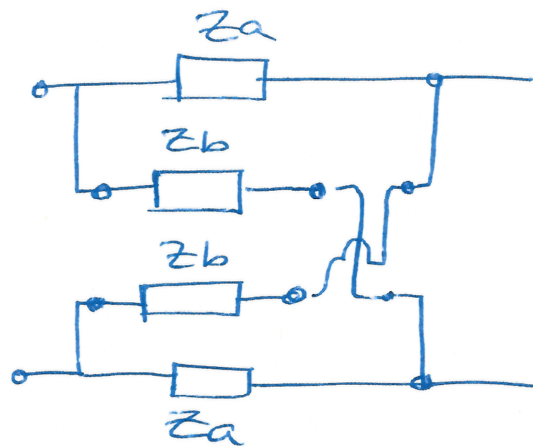

Since output are open-circuit, we can only find admittance parameters

$$\begin{aligned}
 \underline{Na} \quad y_{11a} &= \frac{1}{2Za} & y_{21a} &= -\frac{1}{2Za} \\
 y_{22a} &= \frac{1}{2Za} & y_{12a} &= -\frac{1}{2Za}
 \end{aligned}$$

$$\underline{N_b} \quad y_{11b} = \frac{1}{2Z_b}$$

$$y_{22b} = \frac{1}{2Z_b}$$

For  $N_b$  due to cross-coupling w/o/p :

$$y_{12b} = +\frac{1}{2Z_b} \quad (\text{positive})$$

$$y_{21b} = \frac{1}{2Z_b}$$

Since they are in parallel

$$Y_T = Y_a + Y_b = \begin{bmatrix} \frac{1}{2Z_a} + \frac{1}{2Z_b} & -\frac{1}{2Z_a} + \frac{1}{2Z_b} \\ -\frac{1}{2Z_a} + \frac{1}{2Z_b} & \frac{1}{2Z_a} + \frac{1}{2Z_b} \end{bmatrix}$$

3. (b) For a lattice

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{11} = \frac{1}{(Z_a \parallel Z_b) + (Z_b \parallel Z_a)}$$

$$= \frac{1}{2 \left( \frac{1}{Z_a} + \frac{1}{Z_b} \right)}$$

$$= \frac{\frac{1}{Z_a} + \frac{1}{Z_b}}{2}$$

$$= \frac{1}{2Z_a} + \frac{1}{2Z_b}$$

$$= Y_{11a} + Y_{11b}$$

$$\therefore Y = Y_a + Y_b$$

