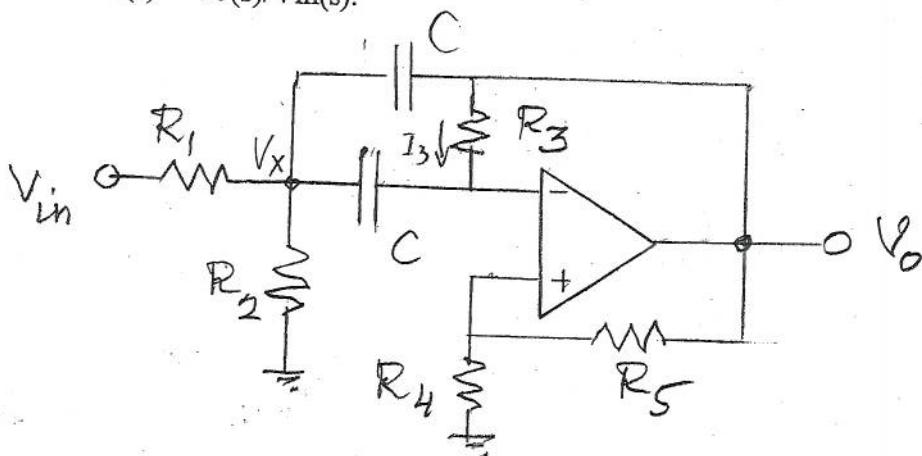


FINAL EXAMINATION
Dec. 8, 2008, 9:30 - 11:20 am


ECE 580

Prof. G. C. Temes

1. Analyze the active filter shown below. Find its transfer function
 $H(s) = V_o(s)/V_{in}(s)$.



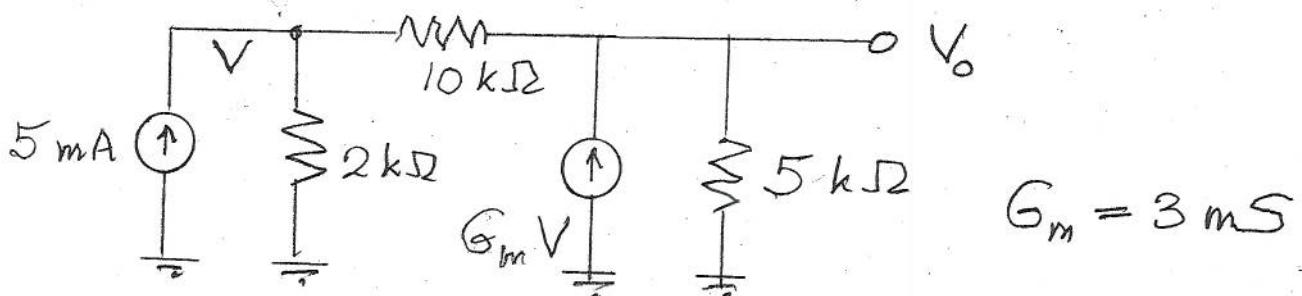2. Find the sensitivity of V_o to variations of the transconductance G_m in the circuit shown, using the adjoint network method.



3. (Easy) Prove that the phase shift of a lumped linear two-port is an odd function of the frequency.
 or

3. (Hard!) What is the asymptotic behavior of the group delay of a lumped linear two-port at very high frequencies? Why?

1' 10"

$$\textcircled{1} \quad I_3 = \left(V_o - V_o \cdot \frac{R_4}{R_4 + R_5} \right) \cdot \frac{1}{R_3} = V_o \cdot \frac{R_5}{(R_4 + R_5)R_3}$$

$$\therefore V_x = V_o - I_3 \cdot (R_3 + \frac{1}{SC})$$

$$= V_o - V_o \cdot \frac{R_5}{(R_4 + R_5)R_3} \cdot (R_3 + \frac{1}{SC}) = V_o \cdot \frac{R_4 R_3 - \frac{R_5}{SC}}{(R_4 + R_5)R_3}$$


Nodal eq. at V_x

$$V_x \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + 2SC \right) - V_{in} \cdot \frac{1}{R_1} - V_o \cdot SC - V_o \cdot \frac{R_4}{R_4 + R_5} SC = 0$$

$$\therefore V_{in} \frac{1}{R_1} = V_o \cdot \left[\frac{R_4 R_3 - \frac{R_5}{SC}}{(R_4 + R_5)R_3} \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + 2SC \right) - SC \cdot \frac{2R_4 + R_5}{R_4 + R_5} \right] = 0$$

$$\begin{aligned} \therefore \frac{V_o(s)}{V_{in}(s)} &= \frac{\frac{1}{R_1}}{\frac{R_4 R_3 - \frac{R_5}{SC}}{(R_4 + R_5)R_3} \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + 2SC \right) - SC \cdot \frac{2R_4 + R_5}{R_4 + R_5}} \\ &= \frac{\frac{1}{R_1}}{\frac{(R_4 R_3 - \frac{R_5}{SC})(\frac{1}{R_1} + \frac{1}{R_2} + 2SC) - SC(2R_4 + R_5)R_3}{(R_4 + R_5)R_3}} \\ &= \frac{(R_4 + R_5)R_3}{R_1 \left[(R_4 R_3 - \frac{R_5}{SC})(\frac{1}{R_1} + \frac{1}{R_2} + 2SC) - SC(2R_4 + R_5)R_3 \right]} \\ &= \frac{a_1 s}{b_2 s^2 + b_1 s + b_0} \\ &= \frac{(R_4 + R_5)R_3 C s}{-R_1 R_3 R_5 C^2 s^2 + R_1 [R_3 R_4 C (\frac{1}{R_1} + \frac{1}{R_2}) - 2R_5 C] s - R_1 R_5 (\frac{1}{R_1} + \frac{1}{R_2})} \end{aligned}$$

(2)

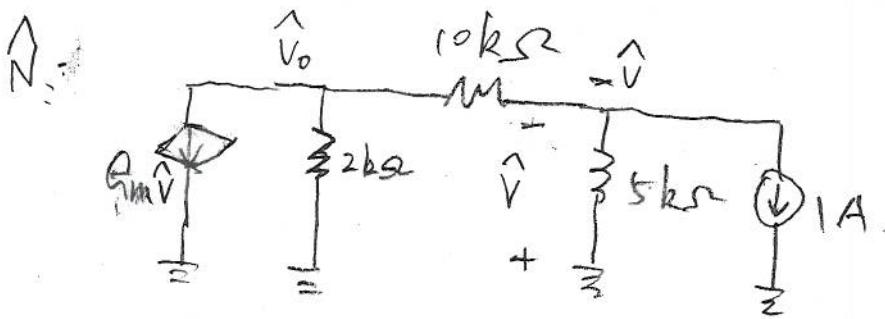Solve V_o :

$$\begin{cases} V \cdot \left(\frac{1}{2} + \frac{1}{10} \right) - V_o \cdot \frac{1}{10} = 5 \\ V_o \cdot \left(\frac{1}{10} + \frac{1}{5} \right) - V \cdot \frac{1}{10} = G_m \cdot V \end{cases} \Rightarrow V = -11.5V$$

Solve V :

$$\begin{cases} -V \cdot \left(\frac{1}{10} + \frac{1}{5} \right) - V_o \cdot \frac{1}{10} = -1000 \\ V_o \cdot \left(\frac{1}{10} + \frac{1}{2} \right) - (-V) \cdot \frac{1}{10} = -G_m V \end{cases} \Rightarrow V = -4615V$$

$$\therefore \frac{\partial V_o}{\partial G_m} = V \cdot V = -53 \text{ V/mS}$$

Si
E
c
f

12-39 3 (easy)

Since $H(s)$ is real rational, it can be written separately in even part and odd part

$$\begin{aligned} H(s) &= H_e(s) + H_o(s) = P_e(s) + s Q_e(s) \\ &= R_1(s^2) + s R_2(s^2) \end{aligned}$$

For $s = j\omega$

$$H(j\omega) = R_1(-\omega^2) + j\omega R_2(-\omega^2)$$

12-41

For

 a_0^n

$$\beta(\omega) = \tan^{-1} \frac{\omega R_2(-\omega^2)}{R_1(-\omega^2)} = \tan^{-1} U(\omega)$$

$$U(\omega) = \frac{\omega R_2(-\omega^2)}{R_1(-\omega^2)} \text{ is an odd function.}$$

 a_0'

Also $\theta(x) = \tan^{-1} x$ is an odd function.

(2n)

$\beta(\omega)$ is obviously an odd function;

$$\text{i.e. } \beta(-\omega) = -\beta(\omega)$$

For

 a

~~10-51~~ 3 (hard)

If we write $H(s)$ as $H(s) = \frac{N(s)}{D(s)}$,

$$F(s) = T_g(\omega) \Big|_{\omega=s/j} = Ev \left[\frac{1}{H(s)} \frac{dH(s)}{ds} \right]$$

$$= Ev \left[\frac{D(s)}{N(s)} \frac{N'(s)D(s) + D'(s)N(s)}{D^2(s)} \right]$$

$$= Ev \left[\frac{N'(s)}{N(s)} + \frac{D'(s)}{D(s)} \right] = \frac{1}{2} \left[\frac{N'(s)}{N(s)} + \frac{N'(-s)}{N(-s)} + \frac{D'(s)}{D(s)} + \frac{D'(-s)}{D(-s)} \right]$$

$$= \frac{1}{2} \left[\frac{N'(s)N(-s) + N'(-s)N(s)}{N(s)N(-s)} + \frac{D'(s)D(-s) + D'(-s)D(s)}{D(s)D(-s)} \right]$$

Considering the numerator of the first term.

$N'(s)N(-s) + N'(-s)N(s)$, the highest-degree terms are cancelled. Therefore the numerator is lower by 2 in degree than the denominator. Same argument goes to second part. Therefore $T_g(\omega) \rightarrow 0$ as const. / ω^2 as $\omega \rightarrow \infty$.

12-53

Norm

Frc

X₁

T1

P

F1

Ik

F