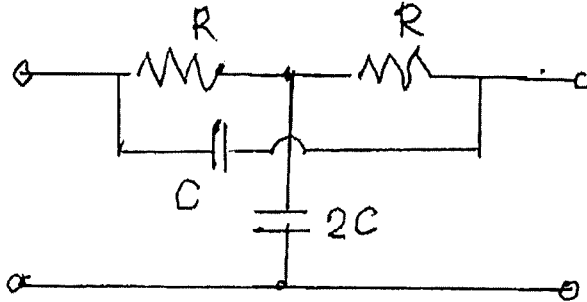


MIDTERM EXAMINATION


October 19, 2022

Open Book


1. Find the short-circuit parameters of the circuit shown below. Assume $R = 5 \text{ k}\Omega$, $C = 10 \text{ pF}$ and $f = 3 \text{ MHz}$.



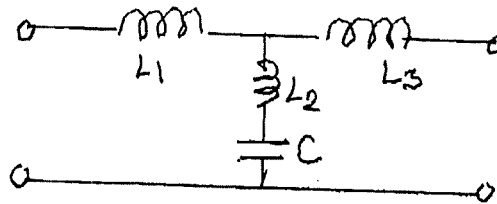2. Two of the short-circuit admittances of the circuit shown are $Y_{11} = Y_{22} = (7s^2 + 1)/(16s^3 + 4s)$. Find all element values.




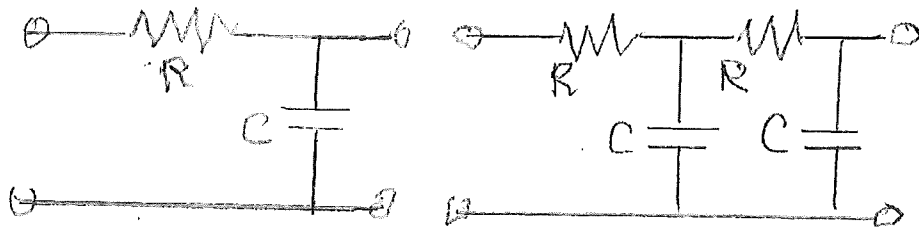3. Find the chain matrices of the two-ports shown below.




Solutions

1. Splitting into parallel two-ports.

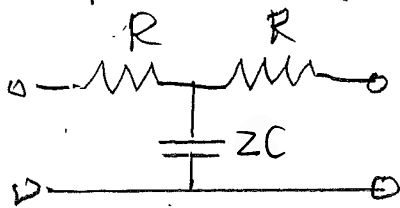

$$Y_{11a} = Y_{22a} = \frac{G}{2} \frac{2sC + G}{sC + G}$$
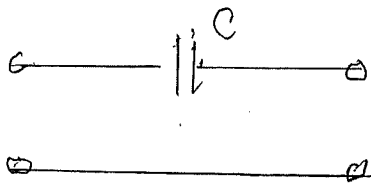
$$Y_{12a} = Y_{21a} = -\frac{G}{2} \frac{G}{sC + G}$$




$$Y_{11b} = Y_{22b} = -Y_{12b} = -Y_{21b} = j\omega C$$

$$\tilde{Y} = \begin{bmatrix} 1.47 + j2.38 & -0.53 - j1.38 \\ \times 0.1 \text{ mS} & \frac{G}{2} \end{bmatrix}$$

2. Next sheet

3. Next sheet

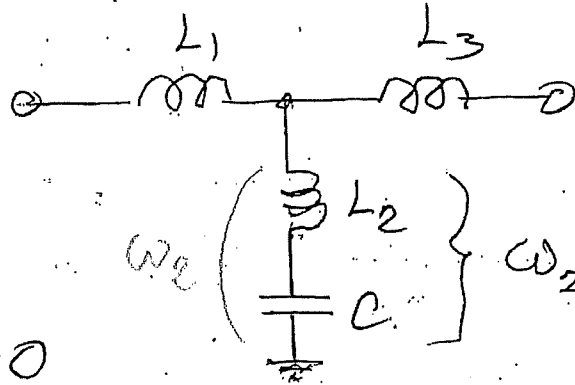3. Find the element values of the two-port shown from $y_{11} = y_{22} = (7s^2 + 1)/(16s^3 + 4s)$.



For $s = 0$

$$y_{11}^{-1} = y_{22}^{-1} = s(L_1 + L_3) \Rightarrow L_1 + L_3 = 4 \text{ H}$$

For $s = j\omega_2$

$$y_{11}^{-1} = y_{22}^{-1} = j\omega_2 L_1 \neq j\omega_2 L_3 \Rightarrow L_1 = L_3 = 2 \text{ H}$$

For $s \rightarrow \infty$


$$y_{11}^{-1} \rightarrow sL_1 + s \frac{L_1 L_2}{L_1 + L_2} = sL_1 \left(1 + \frac{L_2}{L_1 + L_2} \right) = s \frac{6}{7}$$

$$L_1/L_2 = 6, \quad L_2 = 1/3 \text{ H}$$

$$y_{11}^{-1} - sL_1 = \frac{16s^3 + 4s}{7s^2 + 1} - s2 = \frac{2s^3 + 2s}{7s^2 + 1}$$

$$\text{Hence, } \omega_2 = \pm 1, \quad C_2 = 1/L_2 = 3 \text{ F}$$

2

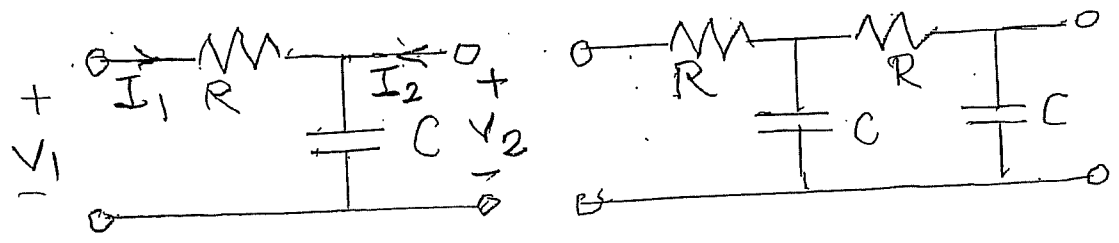

Solutions

1 a. $I_1 = sCV_2 - I_2$

$V_1 = RI_1 + V_2 = R(sCV_2 - I_2) + V_2$

$$\vec{I} = \begin{bmatrix} sRC + 1 & +R \\ sC & +1 \end{bmatrix}$$

b. Find $T^2 = \begin{bmatrix} (sRC+1)^2 + sRC & R(sRC+1) + R \\ sC(sRC+1) + sC & sRC+1 \end{bmatrix}$

CE-11-13-13