


# First-Order Filters

Secton 14.4

# First-order Switched-capacitor Filter


## Active RC Prototype

Fig. 14.17

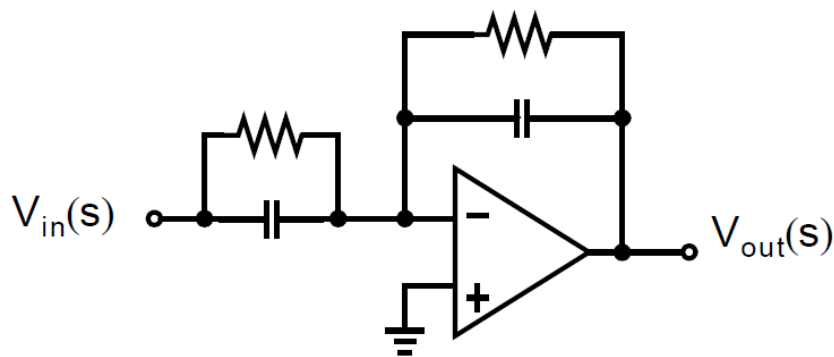

## Switched-capacitor Equivalent

Fig. 14.18(a)

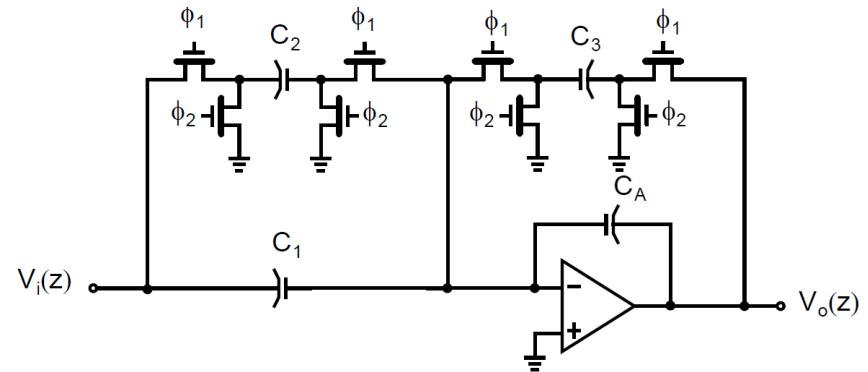


Beginning with conventional continuous-time active RC filters, and replacing each resistor with a switched-capacitor results in a discrete-time filter whose frequency response closely approximates that of the original continuous-time filter at frequencies far below the sampling frequency

# First-order Switched-capacitor Filter


## Signal Flow Graph

Fig. 14.18(b)

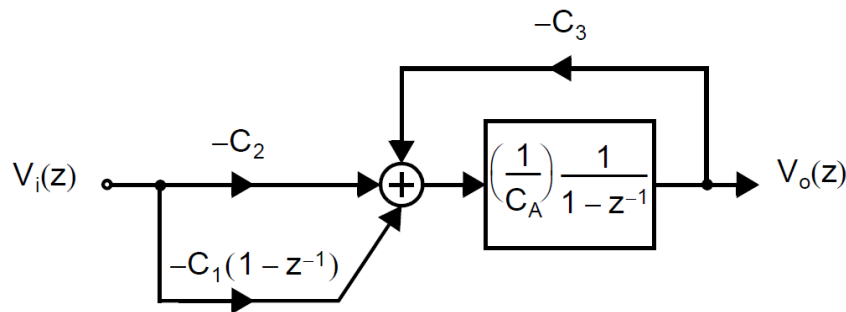

## Switched-capacitor Filter

Fig. 14.18(a)

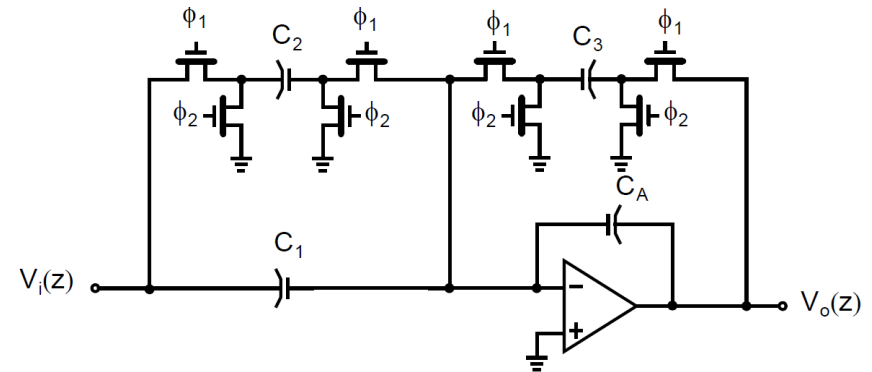


$$C_A(1 - z^{-1})V_o(z) = -C_3V_o(z) - C_2V_i(z) - C_1(1 - z^{-1})V_i(z)$$

Once a filter structure is obtained, its precise frequency response is determined through the use of discrete-time analysis

# First-order Switched-capacitor Filter

$$C_A(1 - z^{-1})V_o(z) = -C_3V_o(z) - C_2V_i(z) - C_1(1 - z^{-1})V_i(z)$$

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = -\frac{\left(\frac{C_1}{C_A}\right)(1 - z^{-1}) + \left(\frac{C_2}{C_A}\right)}{1 - z^{-1} + \frac{C_3}{C_A}}$$
$$= -\frac{\left(\frac{C_1 + C_2}{C_A}\right)z - \frac{C_1}{C_A}}{\left(1 + \frac{C_3}{C_A}\right)z - 1}$$


$$z_p = \frac{C_A}{C_A + C_3} \quad z_z = \frac{C_1}{C_1 + C_2}$$

$$H(1) = \frac{-C_2}{C_3}$$

# Frequency response of the first-order filter

$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = -\frac{\left(\frac{C_1}{C_A}\right)(1-z^{-1}) + \left(\frac{C_2}{C_A}\right)}{1-z^{-1} + \frac{C_3}{C_A}} = -\frac{\left(\frac{C_1}{C_A}\right)(z^{1/2}-z^{-1/2}) + \left(\frac{C_2}{C_A}\right)z^{1/2}}{z^{1/2}-z^{-1/2} + \frac{C_3}{C_A}z^{1/2}}$$

Using:  $z^{1/2} = \cos\left(\frac{\omega T}{2}\right) + j \sin\left(\frac{\omega T}{2}\right)$  &  $z^{-1/2} = \cos\left(\frac{\omega T}{2}\right) - j \sin\left(\frac{\omega T}{2}\right)$

$$H(e^{j\omega T}) \equiv \frac{V_o(e^{j\omega T})}{V_i(e^{j\omega T})} = -\frac{j\frac{2C_1+C_2}{C_A}\sin\left(\frac{\omega T}{2}\right) + \frac{C_2}{C_A}\cos\left(\frac{\omega T}{2}\right)}{j\left(2 + \frac{C_3}{C_A}\right)\sin\left(\frac{\omega T}{2}\right) + \frac{C_3}{C_A}\cos\left(\frac{\omega T}{2}\right)}$$

$$\omega T \ll 1 \Rightarrow \omega \ll 1/T: \quad = -\frac{j\left(\frac{C_1+C_2/2}{C_A}\right)\omega T + \frac{C_2}{C_A}}{j\left(1 + \frac{C_3}{2C_A}\right)\omega T + \frac{C_3}{C_A}}$$

$$\left. \begin{aligned} j\omega_z T &= \frac{-C_2/C_1}{1 + \frac{C_2}{2C_1}} \\ j\omega_p T &= \frac{-C_3/C_A}{1 + \frac{C_3}{2C_A}} \end{aligned} \right\}$$

# Switch Sharing

Fig. 14.18(a)



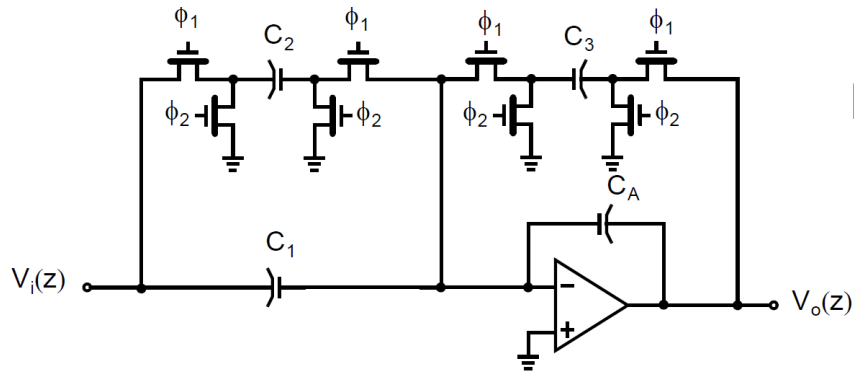
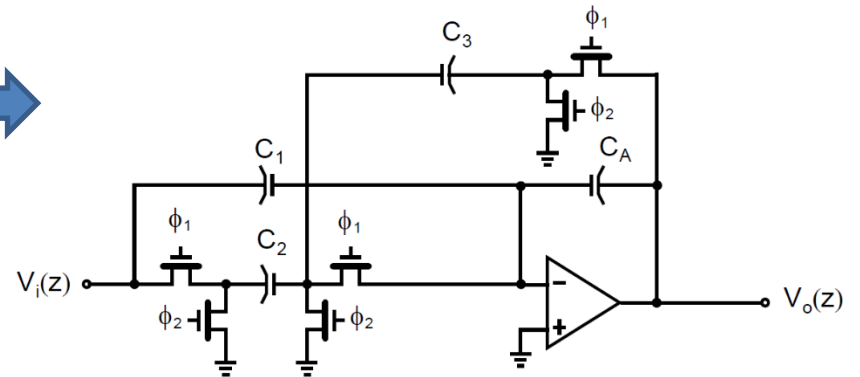


Fig. 14.19

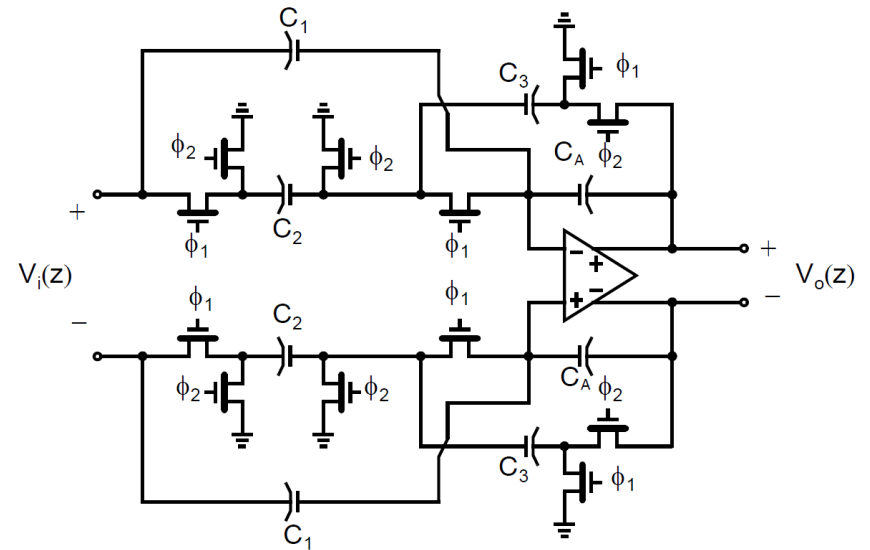

# Fully Differential Implementation

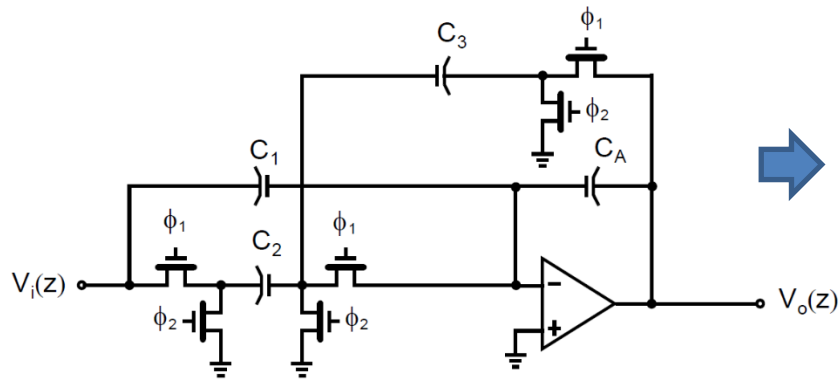

Allows for signal inversion by crossing wires

# Biquad Filters

Secton 14.5




# Discrete-Time Biquad Realizations


- Similar to continuous-time biquads, discrete-time biquads may be realized using two integrators in a negative feedback loop, one of the integrators having loss to provide stability
- Several different discrete-time biquads can be realized by varying the type (i.e., delayed, delay-free) and exact connection of switched-capacitor branches within the two-integrator loop
- The choice of which biquad to use depends upon the specific pole and zero locations sought.

# Biquad #1

## Active RC Prototype

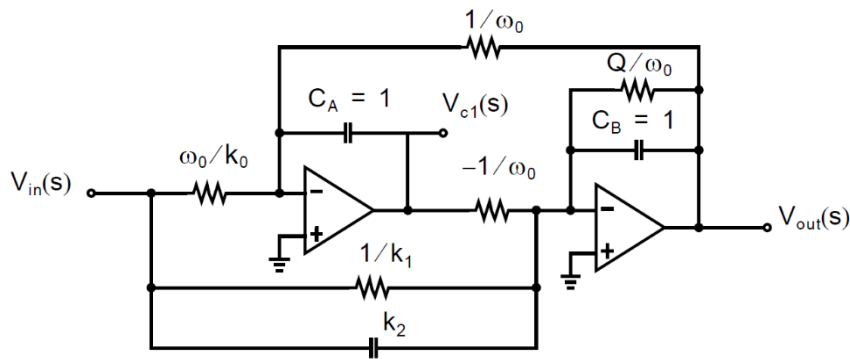


## Switched-capacitor Equivalent

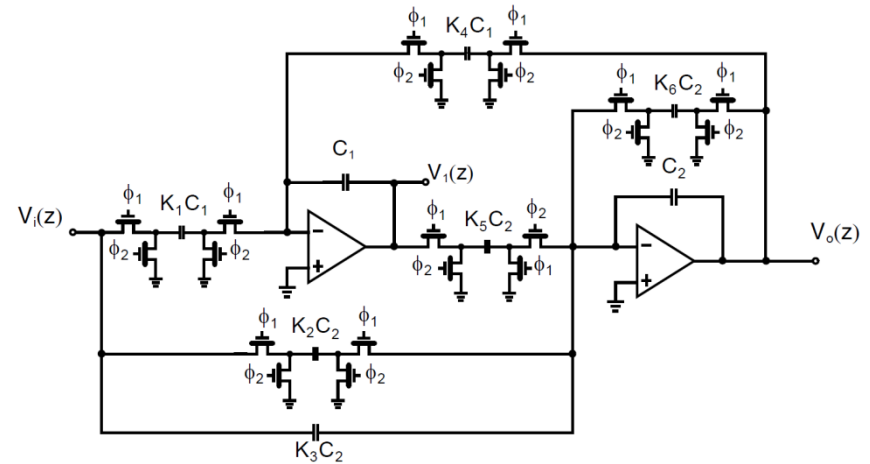


# Biquad #1


## Signal Flow Graph

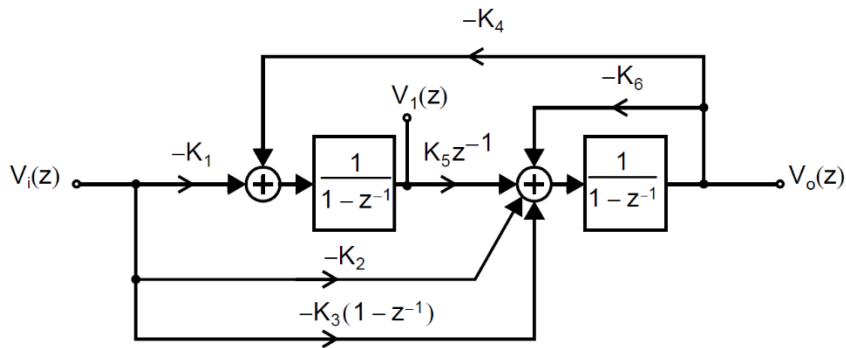

## Switched-capacitor Equivalent

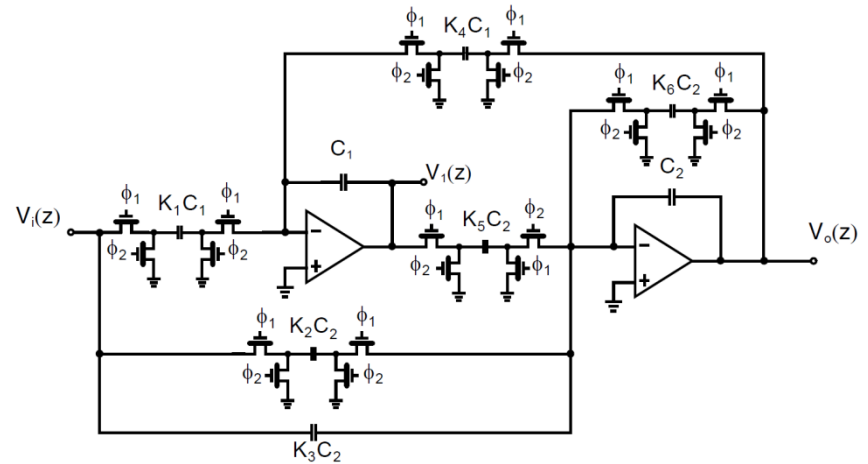

# Biquad #1 Transfer Function

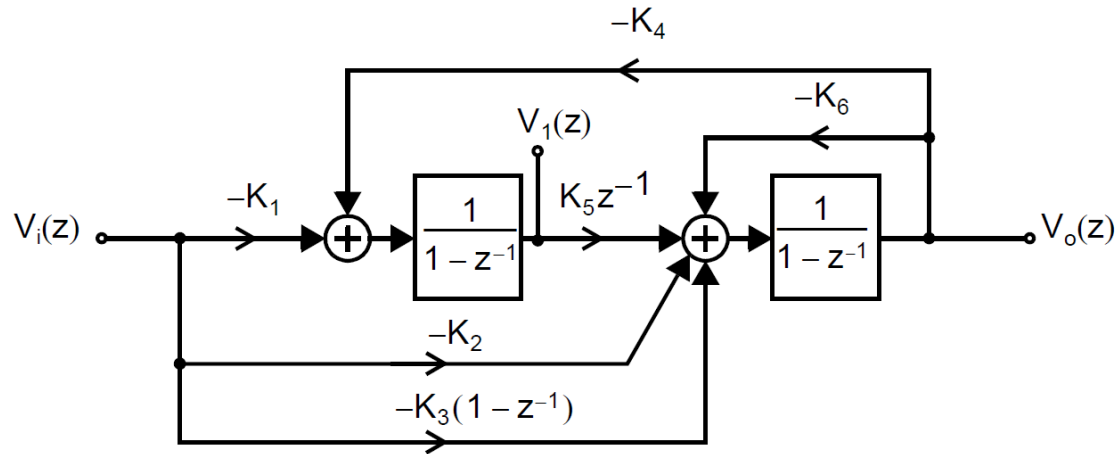


$$H(z) \equiv \frac{V_o(z)}{V_i(z)} = - \frac{(K_2 + K_3)z^2 + (K_1K_5 - K_2 - 2K_3)z + K_3}{(1 + K_6)z^2 + (K_4K_5 - K_6 - 2)z + 1}$$

# Biquad #1 Design Equations

$$H(z) = -\frac{a_2z^2 + a_1z + a_0}{b_2z^2 + b_1z + 1} = -\frac{(K_2 + K_3)z^2 + (K_1K_5 - K_2 - 2K_3)z + K_3}{(1 + K_6)z^2 + (K_4K_5 - K_6 - 2)z + 1}$$

$$K_3 = a_0$$

$$K_2 = a_2 - a_0$$

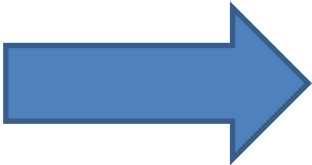
$$K_1K_5 = a_0 + a_1 + a_2$$


$$K_6 = b_2 - 1$$

$$K_4K_5 = b_1 + b_2 + 1$$


Extra degree of freedom in choice of  $K_5$  determines the amplitude of the signal at  $V_1$ .

# Biquad #2

## Active RC Prototype

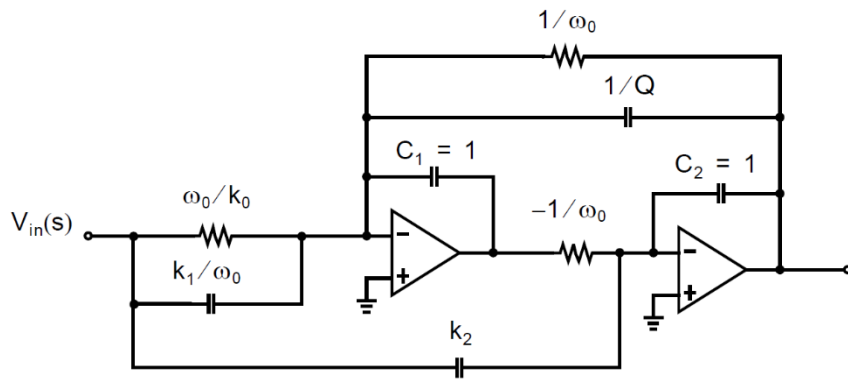

## Switched-capacitor Equivalent

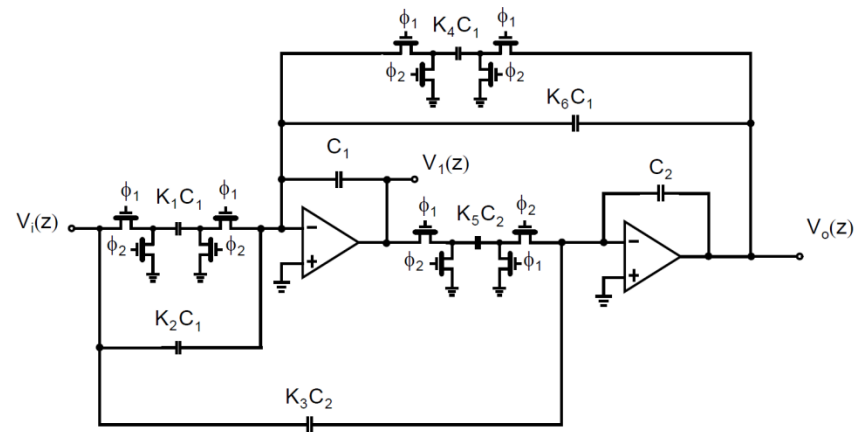

# Biquad #2 Design Equations

$$H(z) = -\frac{a_2 z^2 + a_1 z + a_0}{z^2 + b_1 z + b_0} = -\frac{K_3 z^2 + (K_1 K_5 + K_2 K_5 - 2K_3)z + (K_3 - K_2 K_5)}{z^2 + (K_4 K_5 + K_5 K_6 - 2)z + (1 - K_5 K_6)}$$

$$K_1 K_5 = a_0 + a_1 + a_2$$

$$K_2 K_5 = a_2 - a_0$$

$$K_3 = a_2$$

$$K_4 K_5 = 1 + b_0 + b_1$$

$$K_5 K_6 = 1 - b_0$$

Extra degree of freedom  
in choice of  $K_5$  determines  
the amplitude of the signal  
at  $V_1$ .

