

Back to the chain matrix:

$$V_1 = AV_2 - BI_2 \quad I_1 = CV_2 - DI_2 \quad (5-24)$$

A , B , C , and D are called the *chain parameters*; their matrix

$$\mathbf{T} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad (5-25)$$

$$A = \left(\frac{V_1}{V_2} \right)_{I_2=0} \quad B = \left(\frac{V_1}{-I_2} \right)_{V_2=0} \quad C = \left(\frac{I_1}{V_2} \right)_{I_2=0} \quad D = \left(\frac{I_1}{-I_2} \right)_{V_2=0} \quad (5-27)$$

Hence, \mathbf{T} can be found from the schemes shown in Fig. 5-11.


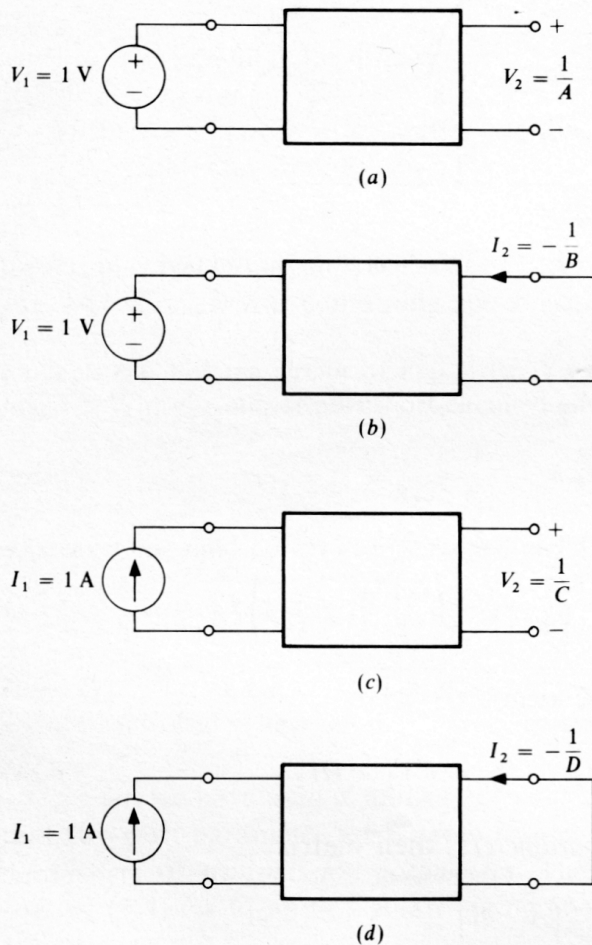


Figure 5-11 Schemes for calculating the chain parameters of a two-port.

Integrator:

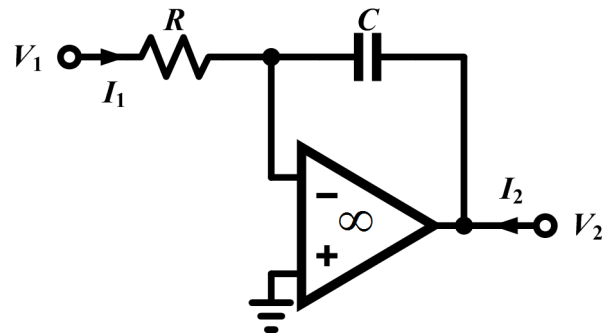

$$V_2 = \frac{-V_1}{sRC} \quad I_1 = \frac{V_1}{R}$$

$$\begin{aligned} V_1 &= -sRCV_2 + 0 \cdot I_2 \\ I_1 &= V_1 / R = -sCV_2 + 0 \cdot I_2 \\ T &= \begin{bmatrix} -sRC & 0 \\ -sC & 0 \end{bmatrix} = sC \begin{bmatrix} R & 0 \\ 1 & 0 \end{bmatrix} \end{aligned}$$

Cascaded integrators:

$$T_1 T_2 = s^2 C_0^2 \begin{bmatrix} R^2 & 0 \\ R & 0 \end{bmatrix} = (-sRC_0)^2 \begin{bmatrix} 1 & 0 \\ 1/R & 0 \end{bmatrix}$$

NOTE: B=D=0 means buffered two-port!

Example 5-3 Find \mathbf{Y} and \mathbf{Z} for the circuit of Fig. 5-7a.

From Fig. 5-7b (where we have chosen for simplicity $V_1 = 1$ V), by inspection

$$y_{11} \triangleq \frac{I_1^1}{V_1} = I_1^1 = sC_1 + \frac{1}{R} \quad y_{21} \triangleq \frac{I_2^1}{V_1} = I_2^1 = -\frac{1}{R}$$

and from Fig. 5-7c, with $V_2 = 1$ V,

$$y_{12} \triangleq \frac{I_1^2}{V_2} = I_1^2 = -\frac{1}{R} \quad y_{22} \triangleq \frac{I_2^2}{V_2} = I_2^2 = sC_2 + \frac{1}{R}$$

Hence

$$\mathbf{Y} = \begin{bmatrix} sC_1 + \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & sC_2 + \frac{1}{R} \end{bmatrix}$$

Therefore

$$\Delta_Y = \left(sC_1 + \frac{1}{R}\right)\left(sC_2 + \frac{1}{R}\right) - \frac{1}{R^2} = s^2C_1C_2 + \frac{s(C_1 + C_2)}{R}$$

and, by (5-17),

$$\mathbf{Z} = \begin{bmatrix} \frac{sC_2 + 1/R}{\Delta_Y} & \frac{1/R}{\Delta_Y} \\ \frac{1/R}{\Delta_Y} & \frac{sC_1 + 1/R}{\Delta_Y} \end{bmatrix}$$

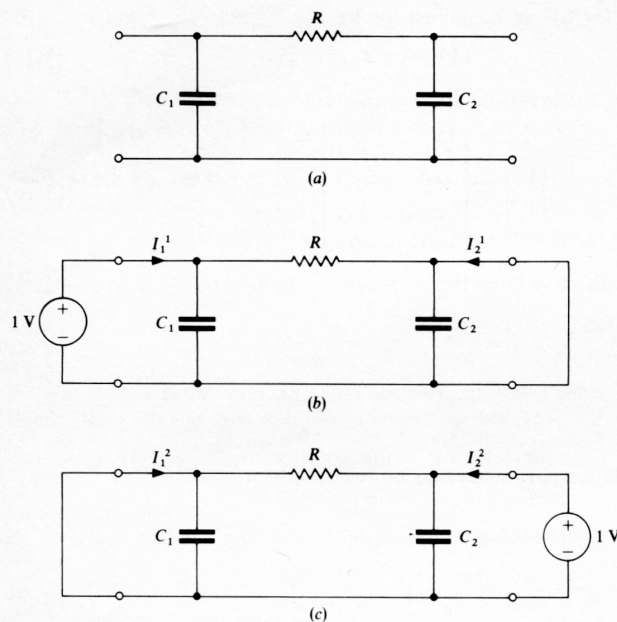


Figure 5-7 Simple RC two-port and the calculation of its admittance parameters.

Of course, \mathbf{Z} can also be obtained directly, using the method illustrated in Fig. 5-4. For our example, this gives

$$z_{11} = \frac{V_1^1}{I_1^1} = \frac{1}{sC_1 + \frac{1}{R + 1/sC_2}}$$

$$z_{11} = \frac{sRC_2 + 1}{s^2RC_1C_2 + s(C_1 + C_2)} = \frac{sC_2 + 1/R}{s^2C_1C_2 + s(C_1 + C_2)/R}$$

Example 5-4 Find \mathbf{Z} and \mathbf{Y} for the two-port shown in Fig. 5-8.

With an input current $I_1 = 1$ A, from (5-2) and Fig. 5-4b,

$$z_{11} = V_1^1 = \frac{sL_1 R_1}{sL_1 + R_1} + \frac{R_2/sC}{R_2 + 1/sC} = \frac{s}{s+1} + \frac{1/s}{1+1/s} = 1$$

and

$$z_{21} = V_2^1 = \frac{R_2/sC}{R_2 + 1/sC} = \frac{1/s}{1+1/s} = \frac{1}{s+1}$$

Similarly, from (5-3) and Fig. 5-4c,

$$z_{12} = V_1^2 = \frac{R_2/sC}{R_2 + 1/sC} = \frac{1}{s+1}$$

and

$$z_{22} = V_2^2 = \frac{sL_2 R_3}{sL_2 + R_3} + \frac{R_2/sC}{R_2 + 1/sC} = 1$$

Hence,

$$\Delta_Z = 1 - \frac{1}{(s+1)^2} = \frac{s^2 + 2s}{s^2 + 2s + 1}$$

and by (5-19)

$$y_{11} = \frac{z_{22}}{\Delta_Z} = \frac{s^2 + 2s + 1}{s^2 + 2s}$$

$$y_{12} = y_{21} = -\frac{z_{12}}{\Delta_Z} = -\frac{s+1}{s^2 + 2s}$$

$$y_{22} = \frac{z_{11}}{\Delta_Z} = \frac{s^2 + 2s + 1}{s^2 + 2s}$$

Again, y_{11} will be checked using the scheme of Fig. 5-5b. For $V_1 = 1$ V,

$$\begin{aligned} y_{11} = I_1^1 &= \frac{1}{\frac{sL_1 R_1}{sL_1 + R_1} + \frac{1}{1/R_2 + sC + 1/R_3 + 1/sL_2}} \\ &= \frac{1}{\frac{s}{s+1} + \frac{1}{2+s+1/s}} = \frac{s^2 + 2s + 1}{s^2 + 2s} \end{aligned}$$

as before.

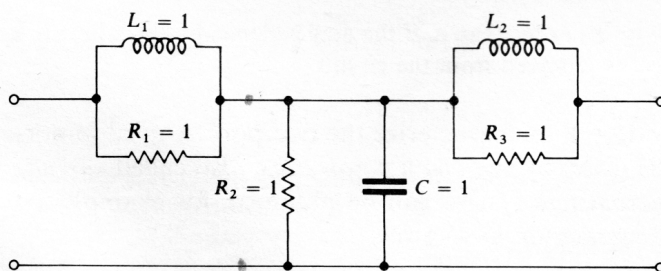


Figure 5-8 RLC two-port example.

Symmetric, reciprocal constant-resistance twoport.

Example 5-5 Find the z_{ij} for the two-port shown in Fig. 5-9.

From Fig. 5-4, we obtain

$$z_{11} = Z_1 + \frac{Z_2(Z_3 + Z_4)}{Z_2 + Z_3 + Z_4}$$

$$z_{12} = z_{21} = \frac{Z_2 Z_4}{Z_2 + Z_3 + Z_4}$$

$$z_{22} = \frac{Z_4(Z_2 + Z_3)}{Z_2 + Z_3 + Z_4}$$

The reader should fill in the details.

Hitherto, all two-port examples contained reciprocal circuits. Hence, by (5-5), $z_{12} = z_{21}$ held, and so did

$$y_{12} = y_{21} \quad (5-21)$$

Equation (5-21) can be obtained either from Eqs. (5-5) and (5-19) or from Fig. 1-6b. For circuits containing active elements, (5-5) and (5-21) need not hold.

Example 5-6 For the circuit of Fig. 5-10a, \mathbf{Y} can readily be found using the scheme of Fig. 5-5. With the output port short-circuited and $V_1 = 1$ V (Fig. 5-10b),

$$y_{11} = I_1^1 = \frac{1}{R_1} + \frac{1}{R_2} \quad y_{21} = I_2^1 = -\frac{G}{R_3} - \frac{1}{R_2}$$

whereas if the input port is short-circuited and $V_2 = 1$ V (Fig. 5-10c),

$$y_{12} = I_1^2 = -\frac{1}{R_2} \quad \text{and} \quad y_{22} = \frac{1}{R_3} + \frac{1}{R_2}$$

Here, $y_{12} \neq y_{21}$, except if $G = 0$ or $R_3 \rightarrow \infty$, that is, if the active element (which here is a voltage-controlled voltage source) is removed from the circuit.

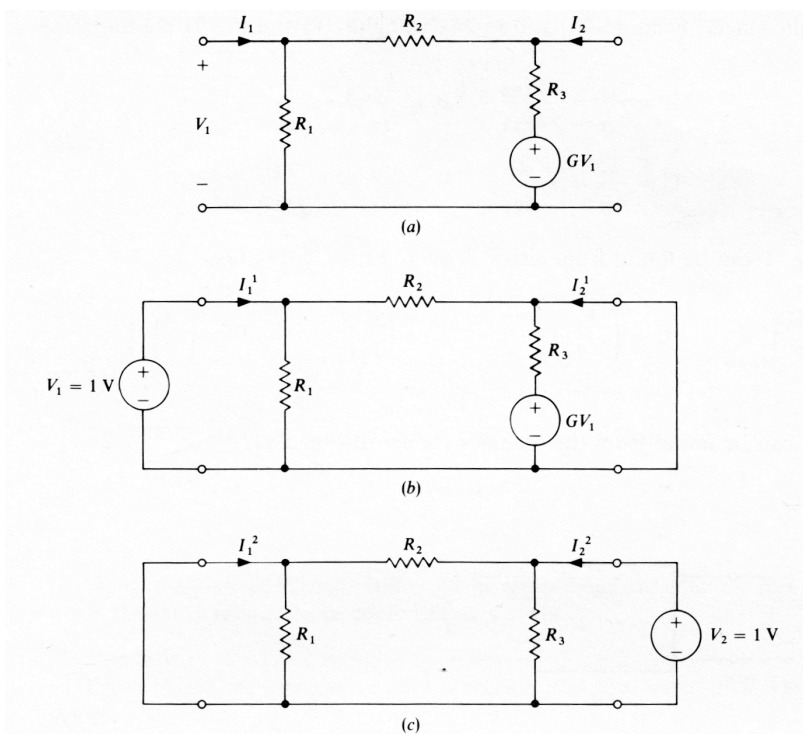


Figure 5-10 (a) Nonreciprocal two-port; (b) and (c) calculation of \mathbf{Y} for the two-port.

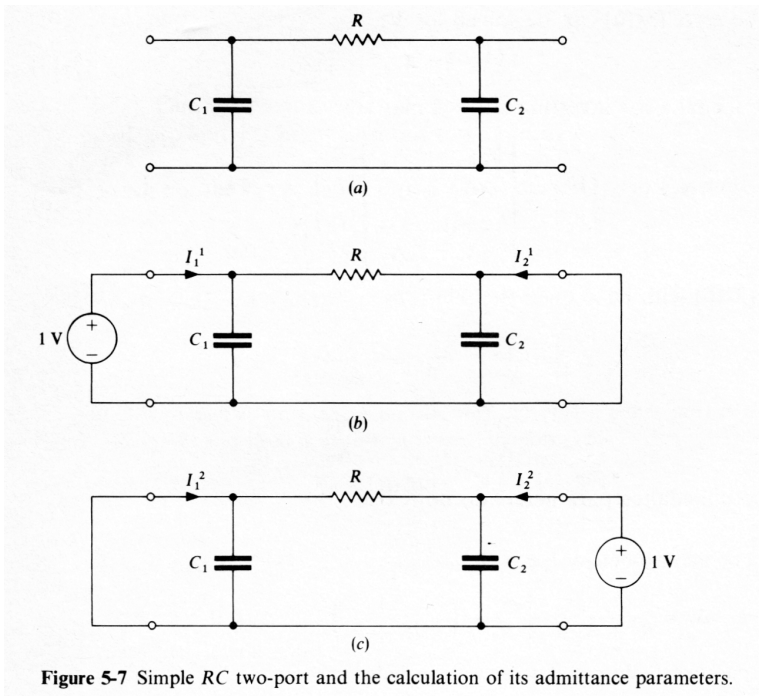


Figure 5-7 Simple RC two-port and the calculation of its admittance parameters.

Example 5-7 For the two-port of Fig. 5-7a, using Fig. 5-11, we find

$$A = \left(\frac{1}{V_2} \right)_{\substack{V_1=1\text{ V} \\ I_2=0}} = \left(\frac{1/sC_2}{R + 1/sC_2} \right)^{-1} = sRC_2 + 1$$

$$B = \left(-\frac{1}{I_2} \right)_{\substack{V_1=1\text{ V} \\ V_2=0}} = R$$

$$C = \left(\frac{1}{V_2} \right)_{\substack{I_1=1\text{ A} \\ I_2=0}} = \left(\frac{1}{V_1 \frac{1/sC_2}{R + 1/sC_2}} \right)_{\substack{I_1=1\text{ A} \\ I_2=0}}$$

$$= \frac{1}{\frac{(1/sC_1)(R + 1/sC_2)}{(1/sC_1 + R + 1/sC_2)} \frac{1/sC_2}{R + 1/sC_2}} = s^2RC_1C_2 + s(C_1 + C_2)$$

and

$$D = \left(-\frac{1}{I_2} \right)_{\substack{I_1=1\text{ A} \\ V_2=0}} = \left(\frac{1/R}{sC_1 + 1/R} \right)^{-1} = sRC_1 + 1$$

When (5-26) is used in conjunction with the values found earlier for the \mathbf{Z} and \mathbf{Y} of this circuit, the above results can be confirmed.

Check:

Example 5-8 For the circuit of Fig. 5-7a,

$$\Delta_T = (sRC_2 + 1)(sRC_1 + 1) - R(s^2RC_1C_2 + sC_1 + sC_2) = 1$$

as expected.

Example 5-9 For the circuit of Fig. 5-10a, the chain parameters can be found from the admittance parameters calculated earlier, for example:

$$A = -\frac{y_{22}}{y_{21}} = -\frac{1/R_3 + 1/R_2}{-G/R_3 - 1/R_2} = \frac{R_2 + R_3}{GR_2 + R_3}$$

$$B = -\frac{1}{y_{21}} = -\frac{1}{-G/R_3 - 1/R_2} = \frac{R_2 R_3}{GR_2 + R_3}$$

$$\begin{aligned} C &= -\frac{y_{11}y_{22} - y_{12}y_{21}}{y_{21}} = -\frac{y_{11}y_{22}}{y_{21}} + y_{12} \\ &= -\frac{(1/R_1 + 1/R_2)(1/R_3 + 1/R_2)}{-G/R_3 - 1/R_2} - \frac{1}{R_2} \\ &= \frac{(R_1 + R_2)(R_2 + R_3)}{(GR_2 + R_3)R_1 R_2} - \frac{1}{R_2} \end{aligned}$$

$$D = -\frac{y_{11}}{y_{21}} = -\frac{1/R_1 + 1/R_2}{-G/R_3 - 1/R_2} = \frac{(R_1 + R_2)R_3}{R_1(GR_2 + R_3)}$$

Hence

$$AD - BC = \frac{\frac{(R_2 + R_3)(R_1 + R_2)R_3}{R_1} - R_2 R_3 \left[\frac{(R_1 + R_2)(R_2 + R_3)}{R_1 R_2} - \frac{GR_2 + R_3}{R_2} \right]}{(GR_2 + R_3)^2}$$

or, after simplifications,

$$AD - BC = \frac{R_3}{GR_2 + R_3}$$

Hence, $AD - BC = 1$ holds only if $R_3 \rightarrow \infty$ or $G \rightarrow 0$, that is, only if the controlled source is removed from the circuit.

Since Eq. (5-4) can be rearranged six different ways with two parameters on the left-hand side and two on the right-hand side, we can define six different sets of two-port parameters. The reader should consult Ref. 1, table 17-1, for a listing of these parameters and for the formulas needed to convert from one set to another.

Transfer Functions for Terminated Twoports

Transfer Function: Possible output/known input (voltage or current. For a two-port, we may have

Voltage ratio, voltage gain: $A_v(s) = V_s(s) / E(s)$

Transfer Admittance: $Y_T(s) = I_2(s) / E(s)$

Transfer Impedance: $Z_T(s) = V_2(s) / I(s)$

Current Ratio, current gain: $A_I(s) = I_2(s) / I(s)$

5-5 TRANSFER FUNCTIONS

When the two-port is excited by a generator and terminated by a load, as illustrated in Fig. 5-1, the signal-transfer properties of the *complete* circuit can be described by an appropriately chosen *transfer function*. We define the transfer function as the ratio of an output variable (voltage or current) to a known input quantity (generator voltage or current).† Since most practical generator and load impedances are essentially resistive, we shall restrict our discussions to resistor-terminated reactance two-ports.

In the simplest (and least useful) situation, both terminations are zero or infinite. Then we have one of the four configurations depicted in Fig. 5-18. These circuits are called *unterminated (unloaded)* two-ports. The proper choice of a transfer function for any of these circuits is obvious and unique. For example, for the circuit of Fig. 5-18a, the output variable must be V_2 since $I_2 \equiv 0$; the known input quantity is the generator voltage E . Hence, we must choose the *voltage ratio* A_V , defined by

$$A_V(s) \triangleq \frac{V_2(s)}{E(s)} \quad (5-84)$$

[The reader should keep in mind the dual interpretation of the variable s . Thus, for $s = j\omega$, $A_V(j\omega)$ may represent the ratio of the steady-state sine-wave voltage phasors at the output and input. In general, however, $A_V(s)$ is the ratio of the Laplace-transformed output signal $v_2(t)$ and generator signal $e(t)$ for a two-port initially free of stored energy.]

Similarly, for the circuit in Fig. 5-18b the transfer function must be the *transfer admittance*

$$Y_T(s) \triangleq \frac{I_2(s)}{E(s)} \quad (5-85)$$

For the circuit of Fig. 5-18c, the transfer function is the *transfer impedance*

$$Z_T(s) \triangleq \frac{V_2(s)}{I(s)} \quad (5-86)$$

† Here all quantities are assumed to be functions of s , not t .

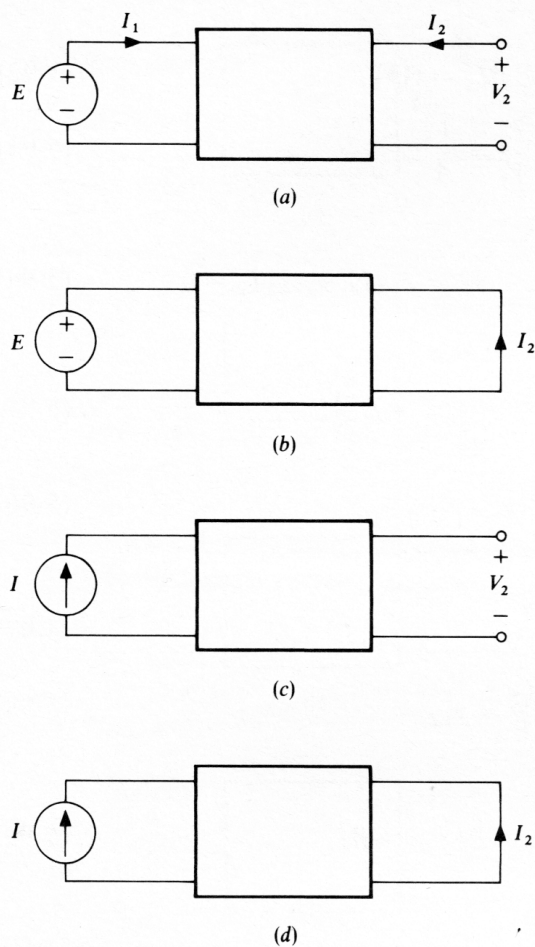


Figure 5-18 Underterminated two-ports.

Finally, for the circuit of Fig. 5-18d, the transfer function is the *current ratio*

$$A_I(s) \triangleq \frac{I_2(s)}{I(s)} \quad (5-87)$$

The transfer functions can readily be calculated from the two-port parameters **Z** or **Y** or **T**. For example, for the circuit of Fig. 5-18a, from (5-9)

$$V_1 = z_{11}I_1 + z_{12}I_2 = z_{11}I_1 \quad V_2 = z_{12}I_1 + z_{22}I_2 = z_{12}I_1 \quad (5-88)$$

Hence

$$A_V = \frac{V_2}{E} = \frac{V_2}{V_1} = \frac{z_{12}}{z_{11}} \quad (5-89)$$

Alternatively, from (5-10)

$$I_2 = y_{12}V_1 + y_{22}V_2 = 0 \quad (5-90)$$

which gives

$$A_V = \frac{V_2}{V_1} = -\frac{y_{12}}{y_{22}} \quad (5-91)$$

Or, from (5-24),

$$V_1 = AV_2 - BI_2 = AV_2 \quad (5-92)$$

so that
$$A_V = \frac{V_2}{V_1} = \frac{1}{A} \quad (5-93)$$

For the circuit of Fig. 5-18b, from (5-9),

$$V_1 = z_{11}I_1 + z_{12}I_2 = E \quad V_2 = z_{12}I_1 + z_{22}I_2 = 0 \quad (5-94)$$

Solving (5-94) for I_2 gives

$$I_2 = -\frac{Ez_{12}}{z_{11}z_{22} - z_{12}^2} = -E\frac{z_{12}}{\Delta_Z} \quad (5-95)$$

so that
$$Y_T \triangleq \frac{I_2}{E} = -\frac{z_{12}}{\Delta_Z} \quad (5-96)$$

Alternatively, from (5-10)

$$I_2 = y_{12}V_1 + y_{22}V_2 = y_{12}E \quad (5-97)$$

so that
$$Y_T = \frac{I_2}{E} = y_{12} \quad (5-98)$$

Or, from (5-24),

$$V_1 = E = AV_2 - BI_2 = -BI_2 \quad (5-99)$$

which gives

$$Y_T = \frac{I_2}{E} = -\frac{1}{B} \quad (5-100)$$

directly.

Exactly analogous manipulations give

$$Z_T = \frac{V_2}{I} \triangleq z_{12} = -\frac{y_{12}}{\Delta_Y} = \frac{1}{C} \quad (5-101)$$

for the circuit of Fig. 5-18c and

$$A_I = -\frac{z_{12}}{z_{22}} = \frac{y_{12}}{y_{11}} = -\frac{1}{D} \quad (5-102)$$

for the circuit of Fig. 5-18d.

If the two-port has a single resistive termination, it is called a *singly terminated* or *singly loaded* two-port. Four possible circuits for such a two-port are illustrated in Fig. 5-19. Notice that two other possible circuits exist which may be obtained by replacing the generator and its internal impedance R by its Norton equivalent in the circuit of Fig. 5-19b or by its Thevenin equivalent in Fig. 5-19d. Their transfer functions differ only by a factor R from those of Fig. 5-19b and d, and hence they do not merit separate treatment.

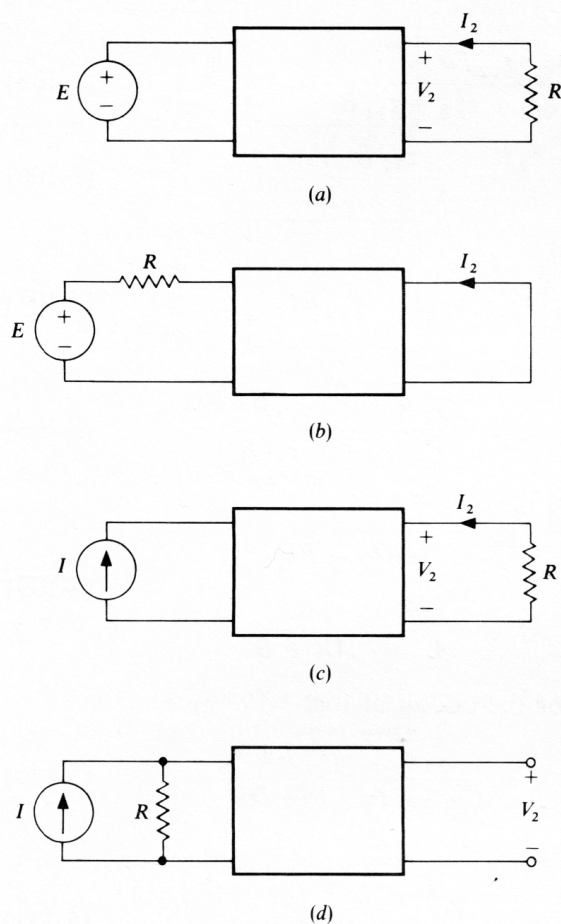


Figure 5-19 Singly terminated two-ports.

For the circuit of Fig. 5-19a, we can choose $A_V = V_2/E$ as the transfer function. (Again, a trivially different choice is to select $Y_T \triangleq I_2/E$; since $I_2 = -V_2/R$, here $Y_T = -A_V/R$.)

For the circuit of Fig. 5-19b, the transfer function may be selected as $Y_T = I_2/E$ [or as $A_I = I_2/I = I_2/(E/R) = RY_T$ if the Norton generator model is substituted].

For the circuit of Fig. 5-19c, we can use $A_I = I_2/I$ or, as trivial variant, $Z_T = V_2/I = -I_2 R/I = -RA_I$. For the circuit of Fig. 5-19d, the transfer function can be $Z_T = V_2/I$ or if the Thevenin equivalent is used for the generator, $A_V = V_2/E = V_2/(IR) = Z_T/R$.

The transfer functions of the singly loaded two-port can also easily be found in terms of the two-port parameters and R , as will be shown next. For the circuit of Fig. 5-19a, combining the branch relations

$$V_1 = E \quad V_2 = -RI_2 \quad (5-103)$$

and the two-port relations (5-9), we get

$$z_{11}I_1 + z_{12}I_2 = E \quad z_{12}I_1 + (z_{22} + R)I_2 = 0 \quad (5-104)$$

which gives

$$I_2 = \frac{z_{12}E}{-z_{11}z_{22} + z_{12}^2 - z_{11}R} \quad (5-105)$$

so that

$$A_V = \frac{V_2}{E} = \frac{-I_2R}{E} = \frac{z_{12}R}{\Delta_Z + z_{11}R} \quad (5-106)$$

Alternatively, from (5-103) and (5-10)

$$I_2 = y_{12}V_1 + y_{22}V_2 = y_{12}E - y_{22}RI_2 \quad (5-107)$$

which gives

$$I_2 = \frac{y_{12}E}{1 + y_{22}R} \quad A_V = \frac{-I_2R}{E} = \frac{-y_{12}R}{1 + y_{22}R} \quad (5-108)$$

Finally, from (5-24), using (5-103), we have

$$\begin{aligned} V_1 = E = AV_2 - BI_2 &= -ARI_2 - BI_2 \\ I_2 = \frac{-E}{AR + B} \quad A_V = \frac{-I_2R}{E} &= \frac{R}{AR + B} \end{aligned} \quad (5-109)$$

Similar calculations performed for the circuit of Fig. 5-19b give

$$Y_T \triangleq \frac{I_2}{E} = \frac{-z_{12}}{\Delta_Z + z_{22}R} = \frac{y_{12}}{1 + y_{11}R} = \frac{-1}{B + DR} \quad (5-110)$$

For the circuit of Fig. 5-19c,

$$A_I \triangleq \frac{I_2}{I} = \frac{-z_{12}}{z_{22} + R} = \frac{y_{12}}{\Delta_Y R + y_{11}} = \frac{-1}{CR + D} \quad (5-111)$$

Finally, for the circuit of Fig. 5-19d,

$$Z_T \triangleq \frac{V_2}{I} = \frac{z_{12}R}{z_{11} + R} = \frac{-y_{22}R}{\Delta_Y R + y_{22}} = \frac{R}{A + RC} \quad (5-112)$$

The most important and most widely used circuit is the doubly terminated (or doubly loaded) reactance two-port, illustrated in Fig. 5-20. Depending on whether Thevenin or Norton model is used for the generator and whether V_2 or I_2 is used as output variable, any one of the four transfer functions A_V , A_I , Z_T , and Y_T can be used to describe the transmission properties of the circuit. If the circuit of Fig. 5-20a is chosen, for example, i.e., a Thevenin generator model, and V_2 as output variable, A_V is the proper transfer function. Now the branch relations are

$$V_1 = E - R_G I_1 \quad V_2 = -I_2 R_L \quad (5-113)$$

They can be combined with the two-port relations (5-9) to give

$$(z_{11} + R_G)I_1 + z_{12}I_2 = E \quad z_{12}I_1 + (z_{22} + R_L)I_2 = 0 \quad (5-114)$$

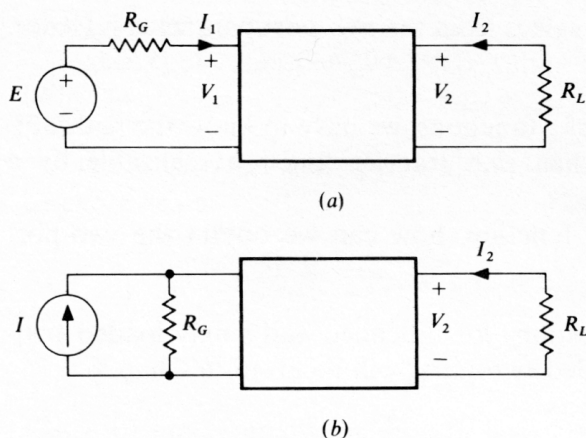


Figure 5-20 Doubly terminated two-ports.

Solving (5-114) for I_2 gives

$$I_2 = \frac{-z_{12}E}{\Delta_Z + z_{11}R_L + z_{22}R_G + R_G R_L} \quad (5-115)$$

Hence
$$A_V = \frac{V_2}{E} = \frac{-I_2 R_L}{E} = \frac{z_{12} R_L}{\Delta_Z + z_{11} R_L + z_{22} R_G + R_G R_L} \quad (5-116)$$

Carrying out the calculations in terms of the y_{ij} , that is, combining and solving (5-113) and (5-10), gives

$$A_V = \frac{-y_{12}R_L}{\Delta_Y R_G R_L + y_{11}R_G + y_{22}R_L + 1} \quad (5-117)$$

Finally, to express A_V in terms of the chain parameters, we combine and solve Eqs. (5-113) and (5-24). This results in


$$A_V = \frac{R_L}{AR_L + B + CR_G R_L + DR_G} \quad (5-118)$$

As will be shown in Chap. 6, the design of a doubly terminated two-port is expediently performed using a different transfer function $H(s)$, which is related to $A_V(s)$ by

$$H(s) \triangleq \frac{1}{2} \sqrt{\frac{R_L}{R_G} \frac{E}{V_2}} = \frac{\sqrt{R_L/R_G}}{2A_V} \quad (5-119)$$

Design of passive two-ports: filter, equalizer (gain or phase).

Delay line

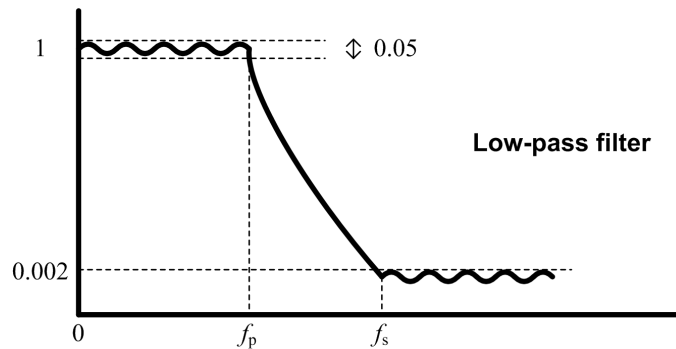

Specs \rightarrow Transfer functions $\rightarrow Z_{oc}, Y_{sc}, T, \dots \rightarrow$ circuit

Example:

Calculate $Z_T = V_2 / I$ for the circuit shown using its z_{ij} parameters.

Solution:

Since $Z_T = z_{12}R / (z_{11} + R)$, we first find

$$z_{11} = (2s^2 + 1) / s(s^2 + 2) \approx 1/2s, s \rightarrow 0$$

$$z_{12} = (V_2 / I_1) \text{ for } I_2 = 0 \rightarrow z_{12} = 1 / (s^3 + 2s), s \rightarrow \infty$$

Substituting gives

$$Z_T = 1 / (s^3 + 2s^2 + 2s + 1)$$

Checks: for $s=0$, $Z_T(s) = 1$; true from circuit diagram. For $s \rightarrow \infty$, $Z_T(s) \rightarrow s^{-3}$, also obvious from circuit.

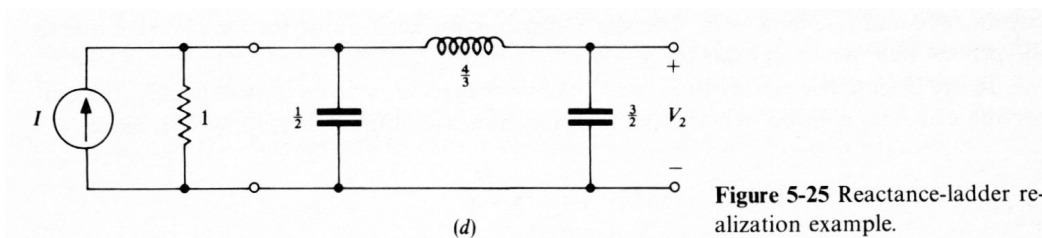



Figure 5-25 Reactance-ladder realization example.

Example:

Find the z_{ij} and AI for the circuit shown. The results are:

$$z_{12} = \frac{3}{s(s^2 + 2)} \quad z_{22} = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$
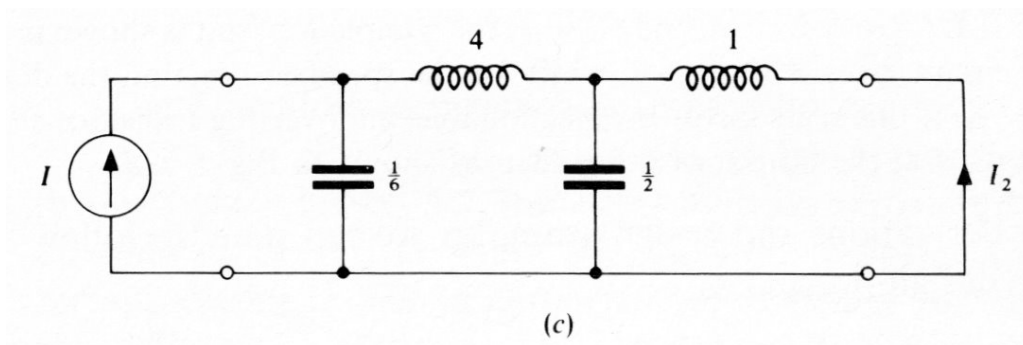
$$A_I \equiv \frac{I_2}{I} = -\frac{z_{12}}{z_{22}} = \frac{-3}{(s^2 + 1)(s^2 + 3)}$$



Again, testing for $z=0$ shows that $z_{22} = -z_{12} = 1/(2s/3)$ and $AI = -1$ are correct, as are $z_{22} \rightarrow$

$$s, z_{12} \rightarrow \frac{3}{s^3} \text{ and } AI \rightarrow \frac{-3}{s^4}$$