

# ECE 580

## HOMEWORK 1

Due Oct. 15, 2015

1. Find the admittance and impedance parameters of a gyrator with gyration resistance  $R$ .
2. Find the impedance parameters of the circuit shown below.

