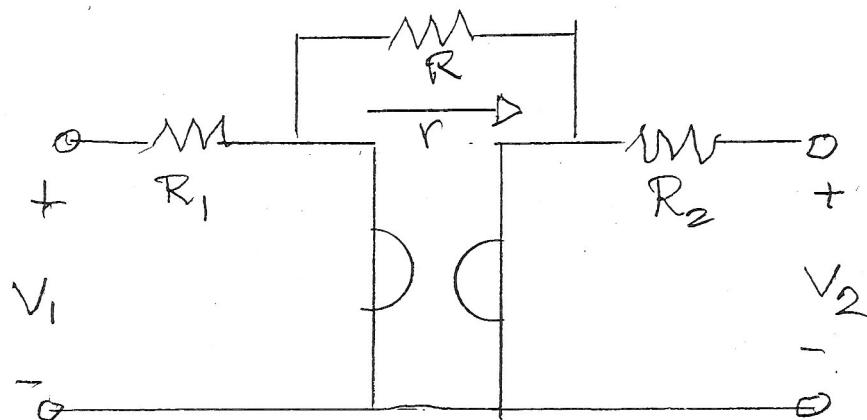


ECE 580


HOMEWORK 3

Due Nov. 11, 2015

1. a. Find the scattering matrix of the circuit shown. Assume that all resistors (including the gyration resistance R) equal 50Ω .
- b. What can you state about the physical properties of the two-port?



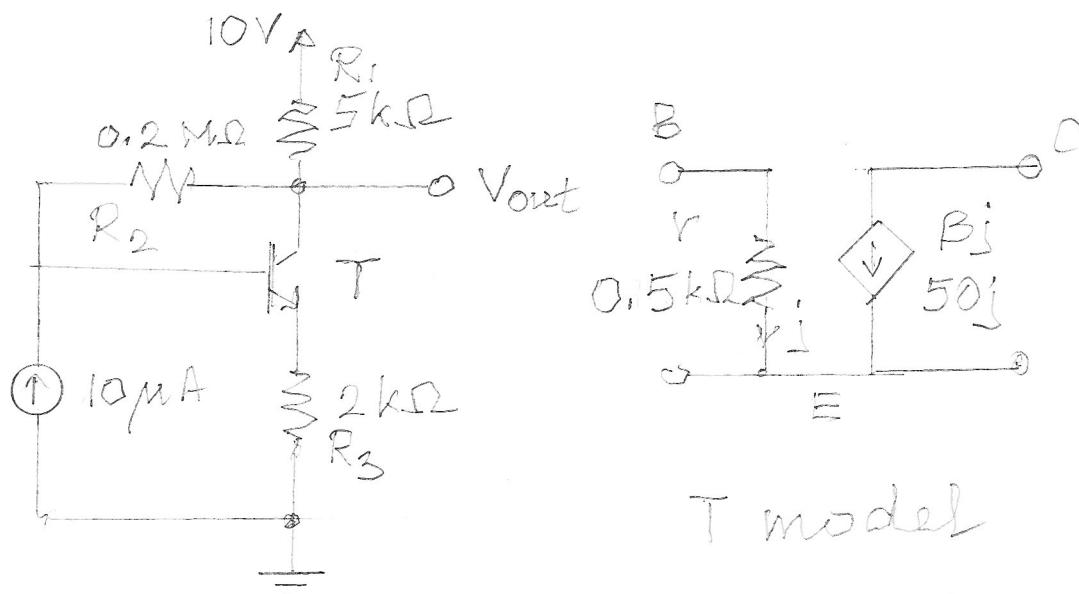2. Find the sensitivities of the output voltage of the amplifier shown to variations of all circuit parameters (including β).



Problem 3: (10 points) For the two-port of Problem 2, assume $r = R = 1\Omega$. Choose as its terminations $R_1 = R_2 = 1\Omega$. Find the scattering matrix, and comment on the transmission properties of the circuit.

For $r = R = 1\Omega, R_1 = R_2$,

$$\tilde{Z} = \begin{bmatrix} 1 & 0 \\ 2 & 1 \end{bmatrix}, \quad \tilde{Z}_{an} = \begin{bmatrix} 2 & 0 \\ 2 & 2 \end{bmatrix} = \tilde{Z}_{an}$$

$$\tilde{Y}_{an} = \frac{1}{4} \begin{bmatrix} 2 & 0 \\ -2 & 2 \end{bmatrix}$$

$$\tilde{S} = \frac{1}{2} - 2 \tilde{Y}_{an} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$

In our case, Z parameter is different by 50 times but S parameter is the same since they are normalized by termination impedance

$S_{11} = S_{22} = 0$; matching at both ports at all frequencies; max. power entering.

$S_{12} = 0$; if excited at port 2, no power at port 1 \rightarrow all power steered to R .

$S_{21} = 1$; if excited at port 1, max. power transfer into R_2 , no power in R ($V_2 = V_1$).

3. Analyze the sensitivities of the small-signal output v_0 to variations of R_1 , R_2 , R_3 , r and β using the given transistor model. What is the possible range of v_0 if all tolerances are 5 percent?

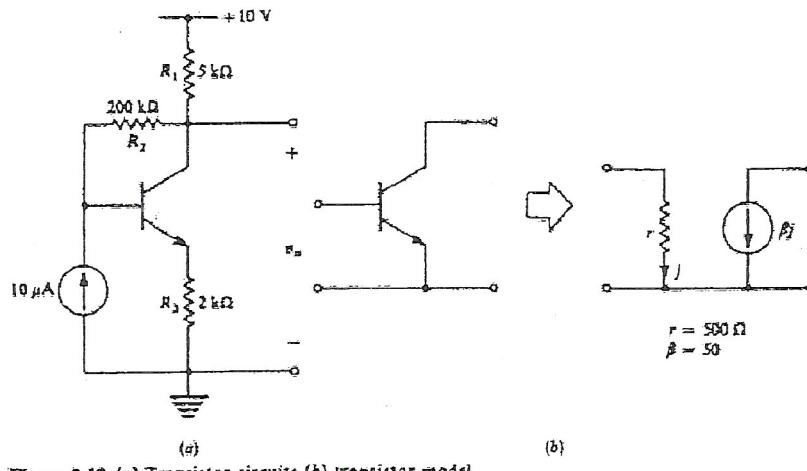


Figure 9-19 (a) Transistor circuit; (b) transistor model.

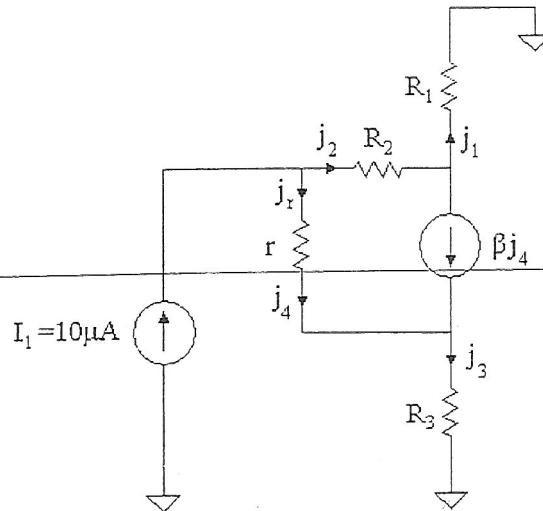


Figure 9-19c Physical network with small-signal model

From the physical network

$$I_1 = 10 \mu\text{A} = j_2 + j_r$$

$$j_2 = I_1 - j_r$$

$$j_3 = j_r + \beta j_r = j_r(\beta + 1)$$

$$j_1 = j_2 - \beta j_r$$

$$\hat{j}_1 * R_1 + \hat{j}_2 * R_2 - \hat{j}_r * r - \hat{j}_3 * R_3 = 0 \quad (\text{loop through all resistors})$$

$$(\hat{j}_2 - \beta \hat{j}_r) * R_1 + \hat{j}_2 * R_2 - \hat{j}_r * r - \hat{j}_r (\beta + 1) * R_3 = 0$$

$$(\hat{I}_1 - \hat{j}_r - \beta \hat{j}_r) * R_1 + (\hat{I}_1 - \hat{j}_r) * R_2 - \hat{j}_r * r - \hat{j}_r (\beta + 1) * R_3 = 0$$

$$(\hat{I}_1 - \hat{j}_r (\beta + 1)) * R_1 + (\hat{I}_1 - \hat{j}_r) * R_2 - \hat{j}_r * r - \hat{j}_r (\beta + 1) * R_3 = 0$$

$$(10\mu A - \hat{j}_r (50 + 1)) * (5k\Omega) + (10\mu A - \hat{j}_r) * (200k\Omega) - \hat{j}_r (50 + 1) * (2k\Omega) = 0$$

$$0.05V - \hat{j}_r (255k\Omega) + 2V - \hat{j}_r (200k\Omega) - \hat{j}_r (500\Omega) - \hat{j}_r (102k\Omega) = 0$$

$$\hat{j}_r (557.5k\Omega) = 2.05V$$

$$\hat{j}_r = 3.6771\mu A$$

$$\hat{j}_2 = \hat{I}_1 - \hat{j}_r = 10\mu A - 3.6771\mu A = 6.3228\mu A$$

$$\hat{j}_3 = \hat{j}_r (\beta + 1) = 3.6771\mu A * 51 = 187.534\mu A$$

$$\hat{j}_1 = \hat{j}_2 - \beta \hat{j}_r = 6.3228\mu A - 50 * 3.6771\mu A = -177.534\mu A$$

$$\hat{j}_4 = \hat{j}_r = 3.6771\mu A$$

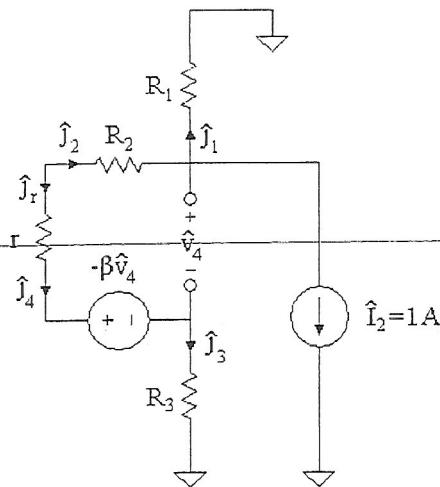


Figure 9-19d

From the adjoint network

$$\hat{I}_2 = 1A = \hat{j}_2 - \hat{j}_1$$

$$\hat{j}_1 = \hat{j}_2 + \hat{I}_2$$

$$\hat{j}_2 = -\hat{j}_r = -\hat{j}_4$$

$$\hat{j}_1 * R_1 + \hat{j}_2 * R_2 - \hat{j}_r * r + \beta \hat{v}_4 - \hat{j}_3 * R_3 = 0 \quad (\text{loop 1})$$

$$\begin{aligned} & (\hat{j}_2 + \hat{I}_2) * R_1 + \hat{j}_2 * R_2 + \hat{j}_2 * r + \beta \hat{v}_4 + \hat{j}_2 * R_3 = 0 \\ & \hat{j}_2 (R_1 + R_2 + R_3 + r) + \beta \hat{v}_4 = -\hat{I}_2 * R_1 \end{aligned} \quad (1)$$

$$\begin{aligned} & \hat{j}_1 * R_1 - \hat{v}_4 + \hat{j}_3 * R_3 = 0 \\ & (\hat{j}_2 + \hat{I}_2) * R_1 - \hat{v}_4 + \hat{j}_2 * R_3 = 0 \\ & \hat{j}_2 (R_1 + R_3) - \hat{v}_4 = -\hat{I}_2 * R_1 \\ & \hat{j}_2 \beta (R_1 + R_3) - \beta \hat{v}_4 = -\hat{I}_2 * \beta R_1 \end{aligned} \quad (2)$$

Adding (1) and (2) we get

$$\begin{aligned} & \hat{j}_2 (R_1(\beta + 1) + R_2 + R_3(\beta + 1) + r) = -\hat{I}_2 * R_1(\beta + 1) \\ & \hat{j}_2 (557.5k\Omega) = 255kV \\ & \hat{j}_2 = 0.45740A \\ & \hat{j}_1 = \hat{j}_2 + \hat{I}_2 = 0.45740A - 1A = -0.54260A \\ & \hat{j}_3 = \hat{j}_4 = \hat{j}_r = -0.45740A \\ & \hat{v}_4 = \hat{j}_2 (R_1 + R_3) + \hat{I}_2 * R_1 = (0.45740A)(5k\Omega + 2k\Omega) + (-1A)(5k\Omega) = -1.7982kV \end{aligned}$$

The sensitivities due to each element are

$$\frac{\partial v_o}{\partial R_1} = -\hat{j}_1 j_1 = -(-0.54260)(-177.534 * 10^{-6}) = -96.330 \mu V / \Omega$$

$$\frac{\partial v_o}{\partial R_2} = -\hat{j}_2 j_2 = -(0.45740)(6.3229 * 10^{-6}) = -2.8921 \mu V / \Omega$$

$$\frac{\partial v_o}{\partial R_3} = -\hat{j}_3 j_3 = -(-0.45740)(187.534 * 10^{-6}) = 85.778 \mu V / \Omega$$

$$\frac{\partial v_o}{\partial r} = -\hat{j}_r j_r = -(-0.45740)(3.6771 * 10^{-6}) = 1.6819 \mu V / \Omega$$

$$\frac{\partial v_o}{\partial \beta} = \hat{v}_4 j_4 = (-1789.2)(3.6771 * 10^{-6}) = -6.6122 mV$$

The maximum deviation of the resistances and β are

$$|\Delta R_1|_{\max} = 0.05 * R_1 = 0.05 * 5k\Omega = 250\Omega$$

$$|\Delta R_2|_{\max} = 0.05 * R_2 = 0.05 * 200k\Omega = 10k\Omega$$

$$|\Delta R_3|_{\max} = 0.05 * R_3 = 0.05 * 2k\Omega = 100\Omega$$

$$|\Delta r|_{\max} = 0.05 * r = 0.05 * 500\Omega = 25\Omega$$

$$|\Delta \beta|_{\max} = 0.05 * \beta = 0.05 * 50 = 2.5$$

The maximum deviation of the output voltage is

$$|\Delta v_o|_{\max} = \left| \frac{\partial v_o}{\partial R_1} \right| |\Delta R_1|_{\max} + \left| \frac{\partial v_o}{\partial R_2} \right| |\Delta R_2|_{\max} + \left| \frac{\partial v_o}{\partial R_3} \right| |\Delta R_3|_{\max} + \left| \frac{\partial v_o}{\partial r} \right| |\Delta r|_{\max} + \left| \frac{\partial v_o}{\partial \beta} \right| |\Delta \beta|_{\max}$$

$$\begin{aligned} |\Delta v_o|_{\max} &= (96.330 \mu V/\Omega) * (250\Omega) + (2.8921 \mu V/\Omega) * (10k\Omega) + (85.778 \mu V/\Omega) * (100\Omega) + \\ &\quad (1.6819 \mu V/\Omega) * (25\Omega) + (6.612mV/\Omega) * (2.5) \\ &= 24.083mV + 28.921mV + 8.578mV + 0.042mV + 16.530mV = 78.154mV \end{aligned}$$

$$v_o = j_1 * R_1 = (-177.53 \mu A)(5k\Omega) = -0.88767V$$

$$j_{o,\max} = -0.88767 + 78.154mA = -0.80952V$$

$$j_{o,\min} = -0.88767 - 78.154mA = -0.96582V$$

The range of the output voltage v_o due to sensitivity is

$$-0.96582V \leq v_o \leq -0.80952V$$
