
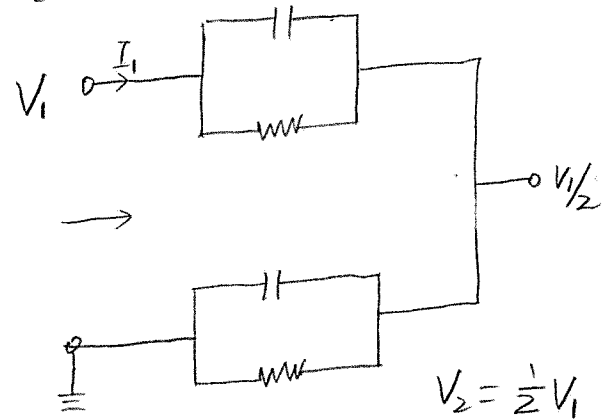


# HW1 Solution.

1. Every  $T = 0.1 \mu\text{s}$ , the  $C = 4\text{pF}$  is charged to  $5\text{V}$ . This requires  $C V^2$  energy, so the power is  $f_c \cdot C V^2 = 10^7 \times 4 \times 10^{-12} \times 25 = 1\text{mW}$

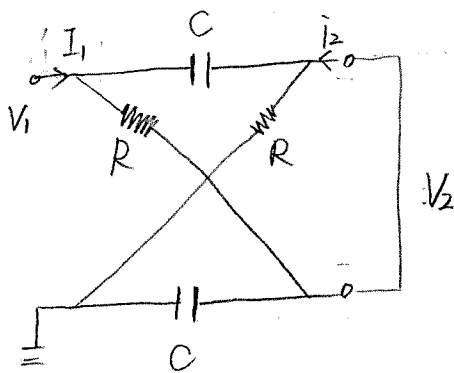2. When calculating  $Y_{11}$  and  $Y_{21}$ , the circuit becomes



$$I_1 = \frac{1}{2} (sC + \frac{1}{R}) V_1$$

$$\Rightarrow Y_{11} = \frac{1}{2} (sC + \frac{1}{R})$$

ALSO,  $i_2 = \frac{V_2}{R} + sC(V_2 - V_1)$

And  $V_2 = \frac{1}{2} V_1$

$$\Rightarrow Y_{21} = \frac{1}{2} (-sC + \frac{1}{R})$$


$$Y_{22} = Y_{11} = \frac{1}{2} (sC + \frac{1}{R})$$

$$Y_{21} = Y_{12} = \frac{1}{2} (-sC + \frac{1}{R})$$

SO

$$Y = \begin{bmatrix} \frac{1}{2} (sC + \frac{1}{R}) & \frac{1}{2} (-sC + \frac{1}{R}) \\ \frac{1}{2} (-sC + \frac{1}{R}) & \frac{1}{2} (sC + \frac{1}{R}) \end{bmatrix}$$

3.

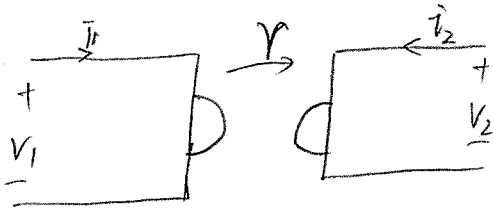


$$v_1 = -r i_2$$

$$v_2 = i_1 r$$

$$\Rightarrow \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$
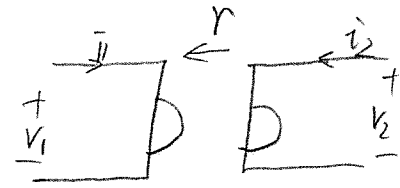
$$Z = \begin{bmatrix} 0 & -r \\ r & 0 \end{bmatrix} \quad \text{OR}$$



$$v_1 = i_2 r$$

$$v_2 = -r i_1$$

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$Z = \begin{bmatrix} 0 & r \\ -r & 0 \end{bmatrix}$$