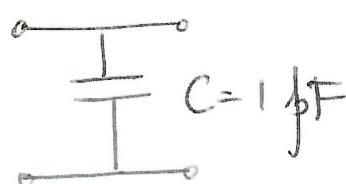


HOMEWORK 3 SOLUTIONS


To find the Y_{ab} and S matrix of the following circuit

Given $R_1 = R_2 = 50\Omega$ & $f = 10 \text{ GHz}$

a)


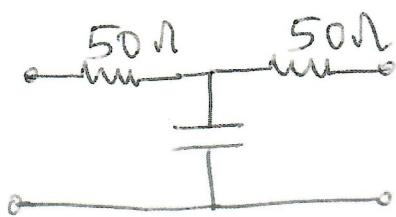
$$Z = \frac{1}{j\omega C} \begin{bmatrix} 1 & 1 \\ 1 & 1 \end{bmatrix}$$



$$Z_a = R + Z = \begin{bmatrix} R + \frac{1}{j\omega C} & j\omega C \\ j\omega C & R + \frac{1}{j\omega C} \end{bmatrix}$$

$$\therefore R = \begin{bmatrix} R & 0 \\ 0 & R \end{bmatrix}$$

$$\text{Let } x = \frac{1}{j\omega C}$$

$$Y_a = \frac{1}{R + 2Rx} \begin{bmatrix} x+R & -x \\ -x & x+R \end{bmatrix}$$

$$Y_{ab} = \frac{1}{R + 2x} \begin{bmatrix} x+R & -x \\ -x & x+R \end{bmatrix} = \frac{j\omega C}{2 + j\omega RC} \begin{bmatrix} \frac{1 + j\omega RC}{j\omega C} & -\frac{1}{j\omega C} \\ -\frac{1}{j\omega C} & \frac{1 + j\omega RC}{j\omega C} \end{bmatrix}$$

$$Y_{ab} = \begin{bmatrix} \frac{1 + 3.14j}{2 + 3.14j} & -\frac{1}{2 + 3.14j} \\ -\frac{1}{2 + 3.14j} & \frac{1 + 3.14j}{2 + 3.14j} \end{bmatrix}$$


$$S = I - 2Y_{ab} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - 2 \begin{bmatrix} \frac{x+R}{2x+R} & -\frac{x}{R+2x} \\ -\frac{x}{R+2x} & \frac{x+R}{2x+R} \end{bmatrix}$$

$$S = \frac{1}{R + \frac{2}{j\omega C}} \begin{bmatrix} -R & \frac{2}{j\omega C} \\ \frac{2}{j\omega C} & -R \end{bmatrix}$$

For $R = 50\Omega$, $C = 1\text{ pF}$ & $\omega = 2\pi \times 10 \times 10^9 \text{ rad/s}$

$$S = \frac{1}{50 - j31.83} \begin{bmatrix} 50 & j31.83 \\ j31.83 & 50 \end{bmatrix}$$

ii)

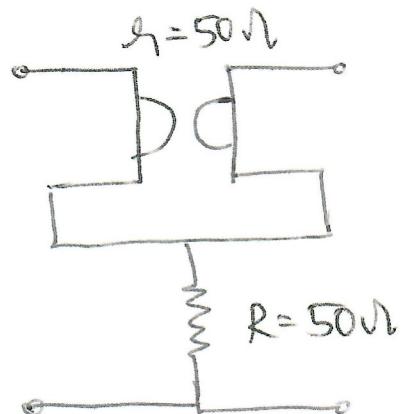

$$Z_{\text{gyrator}} = \begin{bmatrix} 0 & -g \\ g & 0 \end{bmatrix} \quad Z_R = \begin{bmatrix} R & R \\ R & R \end{bmatrix}$$

$$Z_{\text{gyrator}} + Z_R = \begin{bmatrix} R & R-g \\ R+g & R \end{bmatrix}$$

$$Z_a = Z_{\text{gyrator}} + Z_R + \begin{bmatrix} R_1 & 0 \\ 0 & R_2 \end{bmatrix} = \begin{bmatrix} R+R_1 & R-g \\ R+g & R+R_2 \end{bmatrix}$$

$$Z_a = \begin{bmatrix} 100 & 0 \\ 0 & 100 \end{bmatrix} \Omega \quad |Z_a| = (100)^2$$

$$Y_a = \frac{100}{(100)^2} \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix} = \frac{1}{100} \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix}$$

$$Y_{an} = \frac{50}{100} \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & 0 \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$

$$S = I - 2Y_{an} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ -1 & 1 \end{bmatrix}$$

$$S = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$