

HOMEWORK 4 SOLUTIONS

1. GmC biquad transfer function

$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = \frac{s^2 \left(\frac{C_X}{C_X + C_B} \right) + s \left(\frac{G_{m5}}{C_X + C_B} \right) + \left(\frac{G_{m2} G_{m4}}{C_A (C_X + C_B)} \right)}{s^2 + s \left(\frac{G_{m3}}{C_X + C_b} \right) + \left(\frac{G_{m1} G_{m2}}{C_A (C_X + C_B)} \right)}$$

We want a lowpass transfer function

$$H(s) = \frac{k_0}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

with $\omega_0 = 2\pi \cdot 10\text{MHz}$, $Q = 1$, and $k_0 / \omega_0^2 = 5$.

Take all capacitances in the circuit to be a reasonable value; for example $C = \frac{5}{\lambda} \text{pF}$. We must now find G_{m1-m4} :

$$\begin{aligned} G_{m1} = G_{m2} &= \omega_0 C = 0.314 \text{mA/V} \\ G_{m3} &= \omega_0 C / Q = 0.314 \text{mA/V} \\ G_{m4} &= k_0 C / \omega_0 = 5 G_{m1-m3} = 1.57 \text{mA/V} \end{aligned}$$

We have to choose $G_{m5} = 0$ and $C_X = 0$.

$$2. C_2 V_o(n) = C_2 V_o(n-1) - C_1 V_i(n)$$

$$\Rightarrow C_2 V_o(z) = C_2 z^{-1} V_o(z) - C_1 V_i(z) \Rightarrow \frac{V_o(z)}{V_i(z)} = \frac{-C_1/C_2}{1-z^{-1}}$$

1.5)

C_{P2} is always discharged since its voltage is virtually ground.

During ϕ_1 , C_{P1} is charged to $V_i(n)C_{P1}$.

This charge will be transferred

to C_2 during ϕ_2 . Therefore: $C_2 V_o(n) = C_2 V_o(n-1) - C_{P1} V_i(n-1) - C_1 V_i(n)$

$$\Rightarrow \frac{V_o(z)}{V_i(z)} = - \frac{\frac{C_1}{C_2} + \frac{C_{P1}}{C_2} z^{-1}}{1-z^{-1}}$$

