

HOMEWORK 2

ECE 580, 2022

1(a). Construct the modified node equations for the circuit Shown.

(b). Find the node voltages.

