

Make-Up Project

3. From the diagram, by KVL

$$I_{in} = \frac{s 2 C_X}{2} [V_{in} - V_{out}] = s C_X V_{in} [1 - H(s)]$$

From the formula

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{s^2 \left(\frac{C_X}{C_X + C_B} \right) + s \left(\frac{G_{m5}}{C_X + C_B} \right) + \left(\frac{G_{m2} G_{m4}}{C_A (C_X + C_B)} \right)}{s^2 + s \left(\frac{G_{m3}}{C_X + C_B} \right) + \left(\frac{G_{m1} G_{m2}}{C_A (C_X + C_B)} \right)}$$


$$H(\infty) = \frac{C_X}{C_X + C_B} \quad \text{and} \quad H(0) = \frac{G_{m4}}{G_{m1}}$$

Hence,

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{1}{s C_X [1 - H(s)]}$$

At high frequency ($s \rightarrow \infty$)
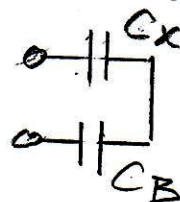
$$Z_{in} \rightarrow \frac{C_X + C_B}{s C_X C_B}$$



At low frequency ($s \rightarrow 0$)

$$Z_{in} \rightarrow \frac{G_{m1}}{s C_X (G_{m1} - G_{m4})}$$

