

# MAKE-UP PROJECT

ECE 580

Due November 30, 2022

1. Find the input impedance  $Z_{in}$  of the Gm-C biquad shown.
2. What is the value of  $Z_{in}$  at very high and at very low frequencies?

