

HOMWORK 2

ECE 580, 2023

Due October 23,2023

In the circuit shown $E = 4$ V. Find all node voltages as efficiently as possible.

