

HOMEWORK 3

ECE 580, 2023

Due October 30, 2023

1(a). Construct the modified node equations for the circuit shown below. It's similar to HW2, 2022, but the 1V source and the 5Ω resistor are interchanged.

(b). Find the node voltages.

