

HOMEWORK 6
ECE 580
 Due November 29, 2023


1. Design a Rauch filter with a dc gain = 1, $Q^2 = \frac{1}{2}$ and a pole frequency $f_0 = 20\text{kHz}$. Minimize the capacitance spread. Use $C_1 = 2\text{pF}$. Plot the gain vs. frequency response.
2. What is the -3 dB frequency of the Rauch filter with a given pole frequency and Q ?

Solution: 1

To minimize the capacitance spread:

CMOS Active Filters, slide 15:

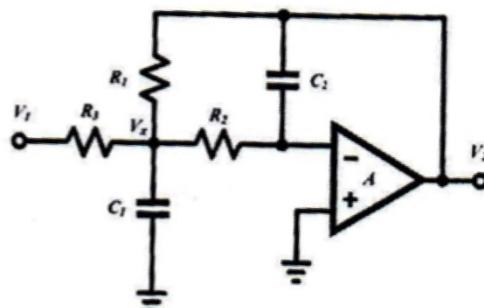Write the denominator in terms of the pole frequency and pole Q. Use $H(0)$. Equate the denominators. Express C_2/C_1 in terms of Q and G_1/G_2 . Find the maximum of C_2/C_1 .




- Transfer function:

$$H(s) = \frac{\frac{G_2 G_3}{C_1 C_2}}{s^2 + s(G_1 + G_2 + G_3)/C_1 + G_1 G_2/(C_1 C_2) + \varepsilon} \\ s^2 + s\omega_0/Q + \omega_0^2$$

$$H(0) = G_3/G_1 = 1 \quad | \quad \omega_0^2 = G_1 G_2 / C_1 C_2 \quad | \quad \omega_0/Q = (2G_1 + G_2)/C_1$$

$$Q^2 = \omega_0^2 C_1^2 / (2G_1 + G_2)^2 = G_1 G_2 (G_1/C_2) / (2G_1 + G_2)^2$$

$$y = C_2/C_1 = Q^{-2} x / (2x+1)^2, \quad x \triangleq G_1/G_2$$
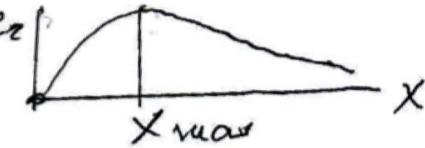
$$\frac{dy}{dx} = Q^{-2} \frac{(2x+1)^2 - x(2x+1)2 \times 2}{()^4}$$


$$4x_{\max}^2 + 4x_{\max} + 1 - 8x_{\max}^2 - 4x_{\max} = 0$$

$$4x_{\max}^2 = 1 \quad x_{\max} = \pm 1/2, \quad G_1 = G_2/2$$

$$C_2/C_1 = Q^{-2}/8 = 1/4, \quad C_1 = 4C_2$$

2.

$$-\omega_3^2 + j\omega_3\omega_0/Q + \omega_0^2$$

$$(\omega_0^2 - \omega_3^2)^2 + \omega_0^2 \omega_3^2 / Q^2 = 2\omega_0^4$$

$$\cancel{\omega_0^4} - 2\omega_0^2 \omega_3^2 + \omega_3^4 + \omega_0^2 \omega_3^2 / Q^2 = 2\omega_0^4$$


$$x \triangleq \left(\frac{\omega_3}{\omega_0}\right)^2 \quad | \quad -2x + x^2 + x/Q^2 = 1$$

$$x^2 - (2 - \cancel{Q^2})x - 1 = 0$$

$$x^2 \Rightarrow 1 \rightarrow \omega_3 = \omega_0$$

Solution

Let Z

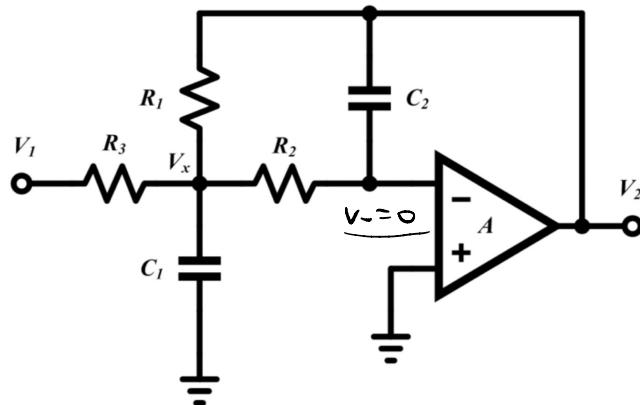

1. Assume ideal opamp,

$$\left. \begin{array}{l} \text{@ } V_x \quad V_1(s) G_3 + V_2(s) G_1 - V_x(s)(G_1 + G_2 + G_3 + sC_1) = 0 \quad \text{①} \\ \text{@ A negative input} \quad V_x(s) G_2 + V_2(s) sC_2 = 0 \end{array} \right\} \quad \text{②}$$

From ②, $V_{x(s)} = -V_2(s) \frac{sC_2}{G_2} \Rightarrow V_1(s) G_3 + V_2(s) G_1 + \frac{sC_2}{G_2} (G_1 + G_2 + G_3 + sC_1) V_2(s) = 0$

$$\begin{aligned} \Rightarrow \frac{V_2(s)}{V_1(s)} &= - \frac{G_3}{G_1 + \frac{sC_2}{G_2} (G_1 + G_2 + G_3 + sC_1)} = - \frac{G_3 G_2}{G_1 G_2 + sG_2(G_1 + G_2 + G_3) + s^2 C_1 C_2} \\ &= - \frac{G_2 G_3 / C_1 C_2}{s^2 + s \frac{G_1 + G_2 + G_3}{C_1} + \frac{G_1 G_2}{C_1 C_2}} \end{aligned}$$

DC gain: $\frac{G_3}{G_1} = 1 \Rightarrow G_1 = G_3$

Quality factor: $\frac{G_1 + G_2 + G_3}{C_1} = \frac{\omega_0}{Q} \Rightarrow C_1 = \frac{Q}{\omega_0} (G_1 + G_2 + G_3) = \frac{Q}{\omega_0} (2G_1 + G_2)$

Pole frequency: $\frac{G_1 G_2}{C_1 C_2} = \omega_0^2 \Rightarrow C_2 = \frac{G_1 G_2}{C_1 \omega_0^2} = \frac{G_1 G_2}{Q \omega_0 (2G_1 + G_2)}$

$$\Rightarrow \frac{C_1}{C_2} = \frac{Q^2 (2G_1 + G_2)^2}{G_1 G_2} = Q^2 (4 \frac{G_1}{G_2} + \frac{G_2}{G_1} + 4) = \frac{1}{2} (4 \frac{G_1}{G_2} + \frac{G_2}{G_1} + 4)$$

$\geq \frac{1}{2} (2 \sqrt{4 \frac{G_1}{G_2} * \frac{G_2}{G_1}} + 4) = 4$, [equal when $\frac{G_1}{G_2} = \frac{1}{2}$]. Therefore, C_1 is always larger than C_2 .

Capacitance spread is minimized when $\frac{C_1}{C_2}$ minimized, i.e. $\frac{G_1}{G_2} = \frac{1}{2}$


$G_2 = 2G_1$, $G_3 = G_1$ $\frac{C_1}{C_2} = 4$, $\Rightarrow G_2 = 0.5 \mu F$

pole frequency ω_0 . $\omega_0^2 = \frac{G_1 G_2}{C_1 C_2} \Rightarrow (2\pi \cdot 20 \times 10^3)^2 = \frac{G_1 \cdot 2G_1}{2\mu F \cdot 0.5 \mu F}$

$$\Rightarrow G_1 = 20 \sqrt{2} \pi nS \approx 88.86 nS, \quad G_2 = 2G_1, \quad G_3 = G_1$$

$R_1 = 11.25 M\Omega$ $R_2 = 5.63 M\Omega$ $R_3 = 11.25 M\Omega$ $C_1 = 2 \mu F$ $C_2 = 0.5 \mu F$

Gain vs. frequency :

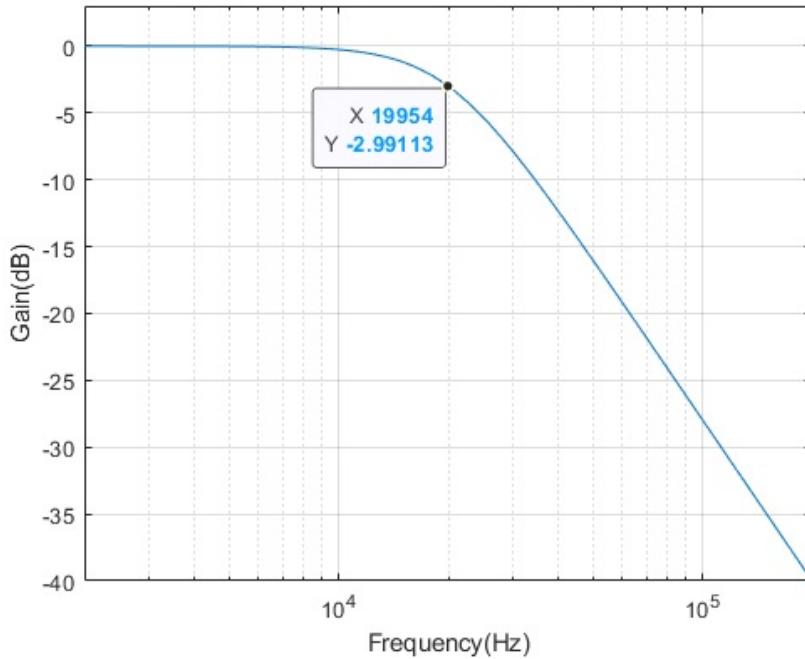

$$Z. \quad H(s) = A \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$|H(j\omega)| = \frac{1}{\sqrt{2}} |H_{dc}| \Rightarrow \left| A \frac{\omega_0^2}{(j\omega)^2 + \frac{\omega_0}{Q}j\omega + \omega_0^2} \right| = \frac{1}{\sqrt{2}} A$$

$$\Rightarrow Z \omega_0^4 = (\omega_0^2 - \omega^2)^2 + \left(\frac{\omega_0}{Q}\omega\right)^2$$

$$\Rightarrow \omega^4 + \left(\frac{1}{Q^2} - Z\right)\omega_0^2\omega^2 - \omega_0^4 = 0$$

$$\Rightarrow \omega^2 = \frac{\left(Z - \frac{1}{Q^2}\right)\omega_0^2 + \sqrt{\left(\frac{1}{Q^2} - Z\right)\omega_0^2\omega^2 + \omega_0^4}}{Z} = \frac{\left(Z - \frac{1}{Q^2}\right) + \sqrt{\left(\frac{1}{Q^2} - Z\right)^2 + 4}}{Z} \omega_0^2$$

$$\Rightarrow \omega_{3dB} = \omega_0 \left[\frac{\left(Z - \frac{1}{Q^2}\right) + \sqrt{\left(\frac{1}{Q^2} - Z\right)^2 + 4}}{Z} \right]^{\frac{1}{2}} = \omega_0 \sqrt{\left(1 - \frac{1}{ZQ^2}\right) + \sqrt{\frac{1}{4Q^4} - \frac{1}{Q^2} + Z}}$$

Specially, when $Q^2 = \frac{1}{Z}$, $\omega_{3dB} = \omega_0$, as in part 1.