

Make-up Project
ECE 580
Due November 22, 2023

1. Find the transfer function of the low-Q Tow-Thomas Biquad from the element values. Use the circuit shown in Slide 26 in CMOS Active Filters.

2. For a prescribed transfer function

$$H(s) = K/(s^2 + as + b)$$

Find the element values.