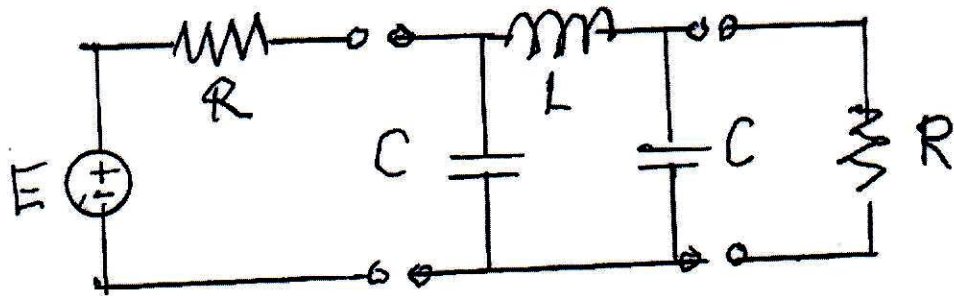


1. (a) Find the chain matrix of the two-port shown below.

(b) Find the voltage gain  $V_2/E$  if the two-port operates between two equal resistors  $R$ .



$$V_1 = AV_2 - BI_2 \quad I_1 = CV_2 - DI_2$$

$$A = (V_1/V_2)_{I_2=0} = \frac{sL + 1/sC}{1/sC} = s^2LC + 1$$

$$B = V_1 / -I_2 \big|_{V_2=0} = sL$$

$$C = I_1/V_2 \big|_{I_2=0} = sC(s^2LC + 2)$$

$$D = I_1 / -I_2 \big|_{V_2=0} = s^2LC + 1$$

$$AD - BC = (s^2LC + 1)^2 - s^2LC(s^2LC + 2) = 1$$


Lecture notes p. 67:

$$\frac{V_2}{E} = \frac{1}{A + B/R + CR + D}$$

$$V_2/E = 1 / [2(s^2LC + 1) + sL/R + sRC(s^2LC + 2)]$$

$$V_2/E = 1 / [s^3RLC^2 + s^22LC + s(L/R + 2RC) + 2]$$

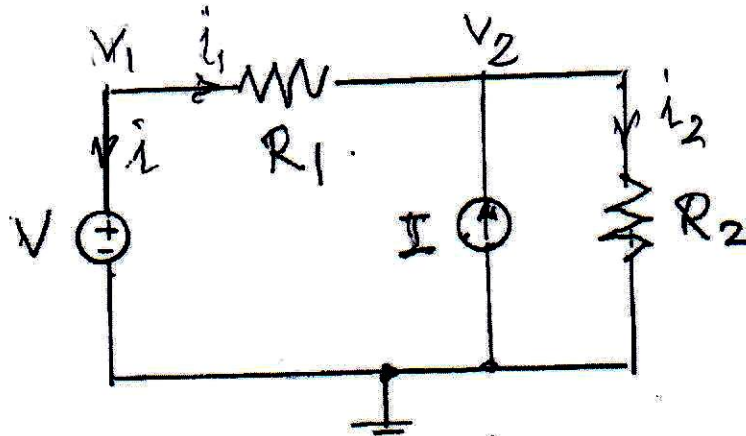2. Find all voltages and currents in the circuit below. The element values are  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $V = 3 \text{ V}$  and  $I = 1 \text{ mA}$ .



Note: Use MNA!

$$\text{KCL1: } (V_1 - V_2)/R_1 + i = 0$$

$$\text{KCL2: } (V_2 - V_1)/R_1 + V_2/R_2 = I$$

$$\text{KVL: } V_1 = V$$

$$\begin{bmatrix} -G_1 & -G_1 & -1 \\ -G_1 & G_1 + G_2 & 0 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ i \end{bmatrix} = \begin{bmatrix} 0 \\ I \\ V \end{bmatrix}$$

Solution:

$$-G_1 V_2 + i = -G_1 V$$

$$-G_1 V + (G_1 + G_2) V_2 = I$$

$$V_2 = (I + G_1 V) / (G_1 + G_2) = \frac{10^{-3} + 3 \times 10^{-3}}{1.5 \times 10^{-3}}$$

$$V_2 = 8/3 \text{ V}, \quad i = +10^{-3} (8/3 - 3) = -\frac{1}{3} \text{ mA}$$

$$i_2 = I - i = 4/3 \text{ mA} \quad V_2 = 8/3 \text{ V}$$