


## MIDTERM EXAMINATION

Open Book

October 26, 2015


Prof. G. Temes

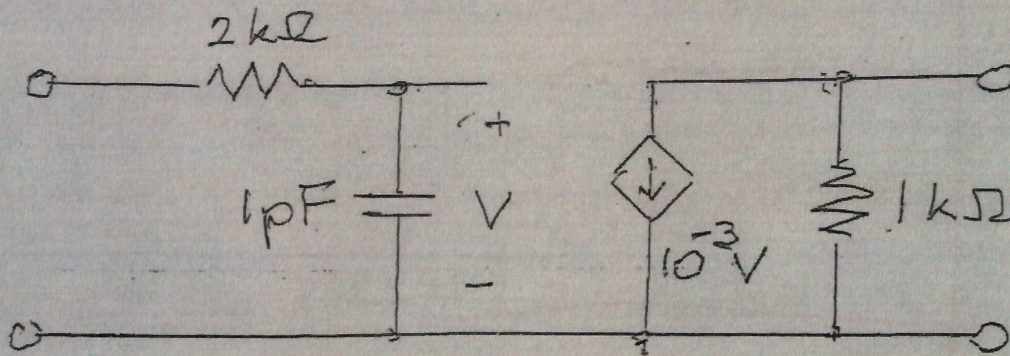1. Find the short-circuit admittance matrix of the circuit shown below at  $f = 100$  MHz.



2.a. Find the input impedance  $Z_{in}$  of the circuit shown.

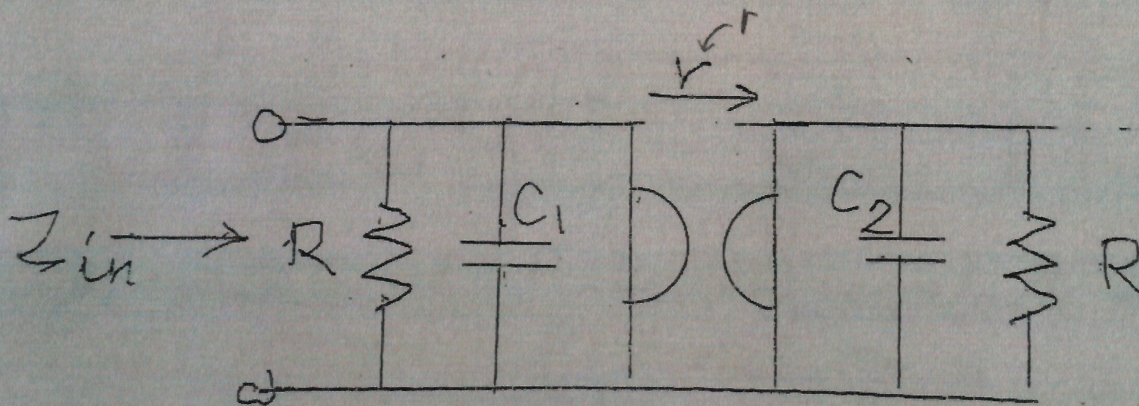b. Find a passive circuit realization of  $Z_{in}$ .



3. a. Show how a lattice can be split into two parallel two-ports  $N_a$  and  $N_b$ .

b. Prove that  $Y = Y_a + Y_b$  holds for the lattice.