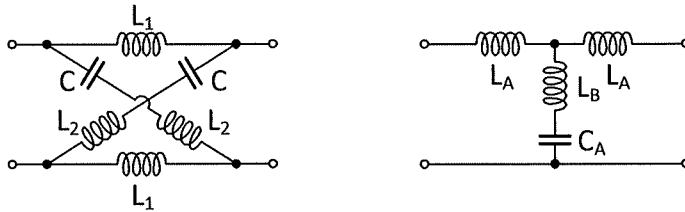


ECE 580


FINAL EXAMINATION

December 7, 2022, 2-4 pm

- The two-ports shown have the same impedance parameters.
 - What are the element values of the bridged-T in terms of those of the lattices?
 - Is the bridged-T always realizable? What is the condition for it?




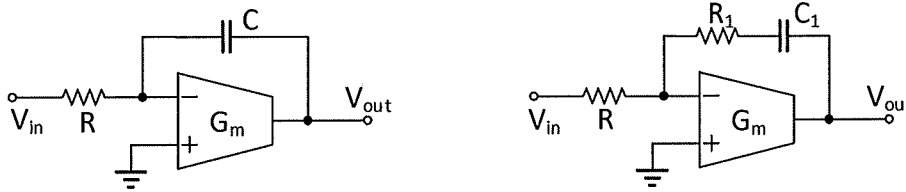
- Find the transfer function V_{out}/V_{in} of the first G_m -C stage shown.
 - Find the element values of the second stage to make $V_{out}/V_{in} = -1/sRC$.



- Find the transfer functions I_0/I_i , $i = 1, 2, 3, 4$ in the circuit shown.

Hint: use inter-reciprocity.

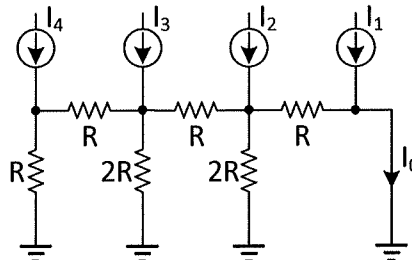

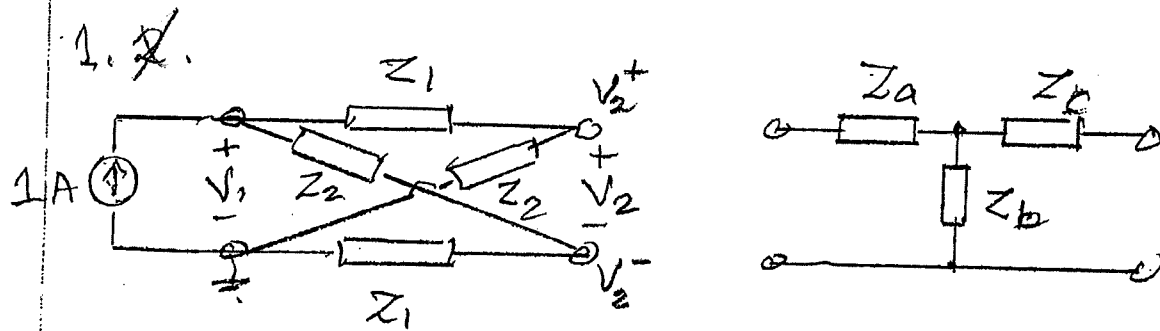

$$Z_{11} = \frac{V_1}{I} = \frac{1}{2} (Z_1 + Z_2) = Z_a + Z_b$$

$$Z_{21} = V_2^+ - V_2^- = \frac{Z_2 - Z_1}{Z_2 + Z_1} V_1 = \frac{Z_2 - Z_1}{2} = Z_b$$

$$Z_b = s(L_2 - L_1)/2 + 1/(2sC)$$


$$Z_a = Z_1 = sL_1 = Z_c$$

a. So $Z_a = Z_c = L_1$, $C' = 2C$

$$L_b = (L_2 - L_1)/2 \geq 0$$

b. $L_2 \geq L_1$ for realizability


2, (a)

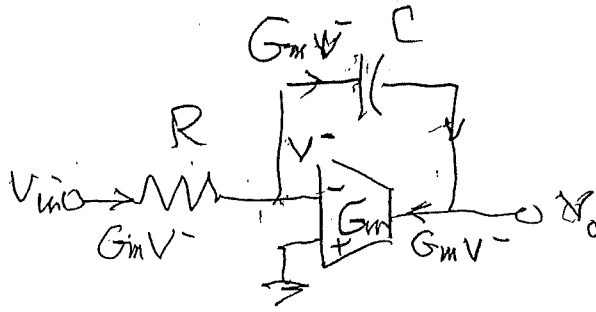

$$V^- = V_{in} - R G_m V^- \quad V_o = -V^- + \frac{1}{sC} G_m V^-$$

$$V^- = V_{in} / (1 + R G_m) \quad V_o = V^- / (1 + G_m / sC)$$
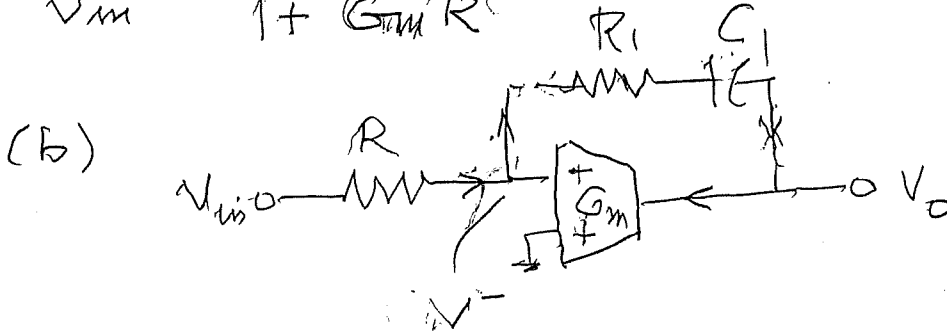
$$\frac{V_o}{V_{in}} = \frac{1 + G_m / sC}{1 + G_m R}$$



$$\begin{aligned} V^- &= V_{in} - R G_m V^- \\ V^- &= V_{in} / (1 + R G_m) \end{aligned} \quad \left| \begin{aligned} V_o &= V_o + (R_1 + \frac{1}{sC_1}) G_m V^- \\ V^- &= V_o / [1 - G_m (R_1 + 1/sC_1)] \end{aligned} \right.$$


$$\frac{V_o}{V_{in}} = \frac{1 - G_m (R_1 + 1/sC_1)}{1 + G_m R} \approx -\frac{1}{sRC}$$

$$-sRC + sG_m R_1 RC + G_m RC / C_1 = 1 + G_m R$$


$$-1 + G_m R_1 = 0 \quad C / C_1 = 1 / G_m R + 1$$

$$R_1 = 1 / G_m \quad C_1 = e \frac{G_m R}{G_m R + 1}$$

3.

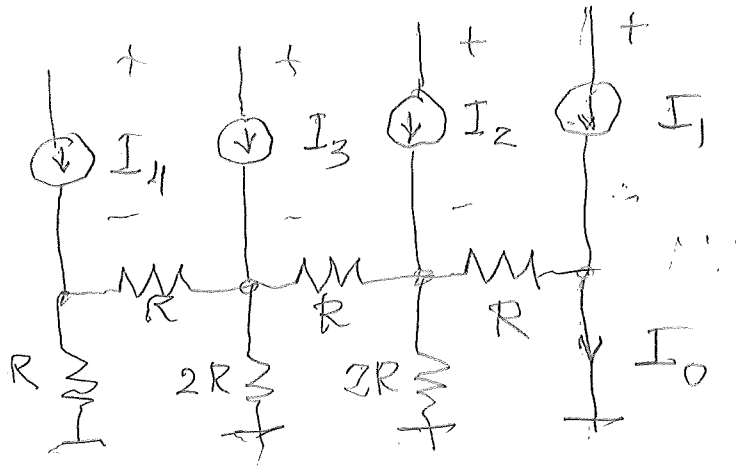

Inter-reciprocal

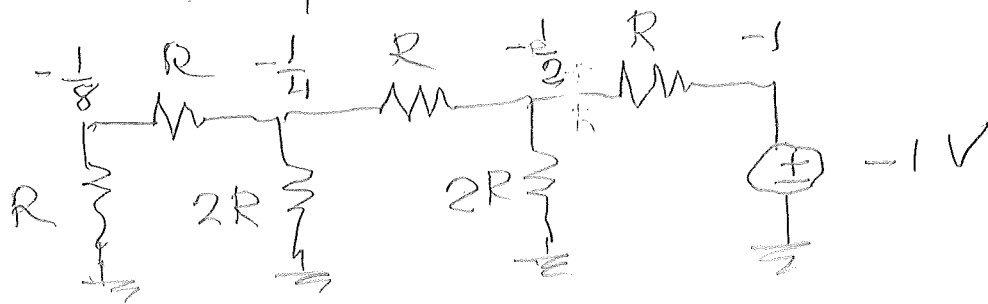

$$I_0 = \left[I_1 + I_2/2 + I_3/4 + I_4/8 \right]$$