

1(a) Assume that the transfer function of the second-order filter is

$$H_E(s) = -\frac{\omega_p^2}{s^2 + s \frac{\omega_p}{Q_p} + \omega_p^2}, \text{ then } E(s) = \frac{1}{H_E(s)} = -\frac{s^2 + s \frac{\omega_p}{Q_p} + \omega_p^2}{\omega_p^2}$$

Group delay $T_g(\omega) = \operatorname{Re} \left[\frac{dE(s)/ds}{E(s)} \right]_{s=j\omega}$

$$= \operatorname{Re} \left[\frac{2s + \frac{\omega_p}{Q_p}}{s^2 + s \frac{\omega_p}{Q_p} + \omega_p^2} \right]_{s=j\omega}$$

$$T_g(\omega_p) = \operatorname{Re} \left[\frac{2j\omega_p + \frac{\omega_p}{Q_p}}{-\omega_p^2 + j\omega_p \cdot \frac{\omega_p}{Q_p} + \omega_p^2} \right]$$

$$= \frac{2Q_p}{\omega_p} = \frac{2 \times 4}{2 \text{ rad/s}} = 4 \text{ us.}$$

15


b) $Q_p \gg 1$, $E(s) = -\frac{s^2 + \omega_p^2}{\omega_p^2}$

$$\Rightarrow E(j\omega) = -1 + (\omega/\omega_p)^2, \text{ real function of } \omega.$$

so $\angle E(j\omega) = 0^\circ$ for all frequencies, then $T_g(\omega_p) = 0$.

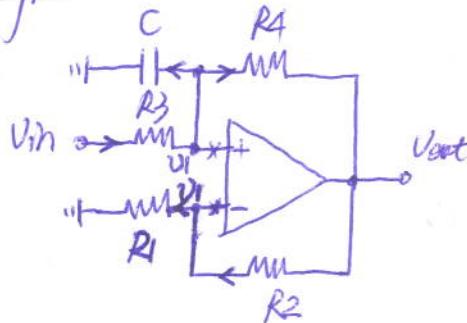2. Based on the characteristic of Amplifier
and use KCL at each node:

$$\left\{ \begin{array}{l} \frac{V_{in} - V_1}{R_3} = \frac{V_1}{1/sC} + \frac{V_1 - V_{out}}{R_4} \\ \frac{V_1}{R_1} = \frac{V_{out} - V_1}{R_2} \end{array} \right.$$




$$\Rightarrow H(s) = \frac{V_{out}}{V_{in}} = \frac{(G_1 + G_2)G_3}{sG_2C + G_2G_3 - G_1G_4}, \quad G_i = \frac{1}{R_i} \quad (i=1,2,3,4)$$

Since $R_1/R_2 = R_3/R_4$, $G_1 G_4 = G_2 G_3$, thus

$$H(s) = \frac{(G_1 + G_2)G_3}{sG_2C} \quad \checkmark \quad 15$$

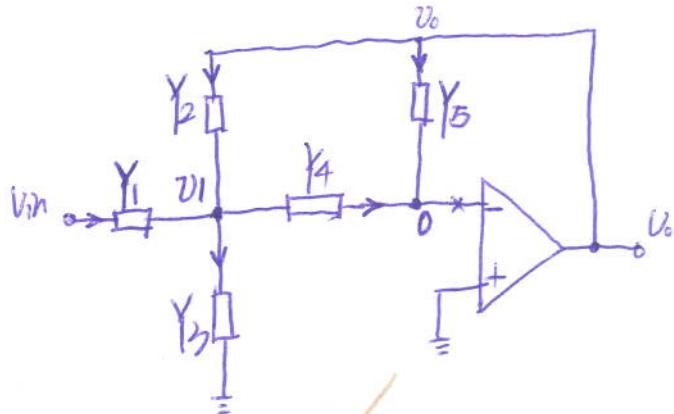3. a) use KCL at each node:

$$\left\{ \begin{array}{l} Y_1(V_{in} - V_1) + Y_2(V_o - V_1) \\ = Y_3V_1 + Y_4V_1 \\ Y_4V_1 + Y_5V_o = 0 \end{array} \right.$$



$$\Rightarrow H(s) = \frac{V_{out}}{V_{in}} = - \frac{Y_1 Y_4}{Y_1 Y_5 + Y_2 Y_4 + Y_2 Y_5 + Y_3 Y_5 + Y_4 Y_5}$$

b) to realize a high-pass filter, $H(s)$ should be in $\frac{a_2 s^2}{b_2 s^2 + b_1 s + b_0}$ form.

by choosing $Y_1 = S G_1$, $Y_2 = S G_2$, $Y_3 = G_3$, $Y_4 = S G_4$, $Y_5 = G_5$. we could get

$$H(s) = - \frac{S G_1 \times S G_4}{S G_1 G_5 + S G_2 \times S G_4 + S G_2 \times G_5 + G_3 G_5 + S G_4 G_5}, \quad \text{satisfying that form.}$$