


Power from generator $E_g i(t)$

Energy from gen.

$$E = E_g \int_0^{\infty} i(t) dt = E_g [q_c(\infty) - q_c(0)]$$

$$E = E_g C v(\infty) = C E_g^2$$
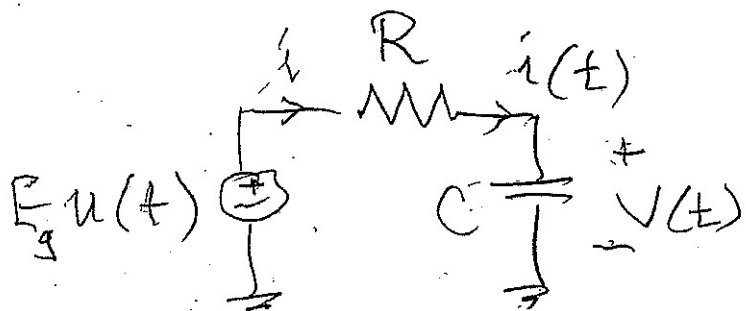
$$E = 2 \left\{ \frac{1}{2} E_g^2 \right\} = 2 \times \text{stored energy in } C$$



$$i(t) = C \, dv/dt$$

Power from gen. $E_g i(t)$

Energy from gen.

$$E = \int_0^{\infty} E_g C (dv/dt) dt = E_g C \int_{v(0)}^{v(\infty)} dv = \underline{CE_g^2}$$

Twice the energy stored in C!

Analysis:

$$E_g \frac{1}{s} = I(s) \left\{ R + 1/(sC) \right\} \rightarrow I(s)$$

$$i(t) = (E_g/R) e^{-t/RC}$$

Power in R: $i^2(t)R$

Energy lost in R:

$$E_R = \int_0^{\infty} i^2(t)R dt = CE_g^2/2$$

Doesn't depend on R!