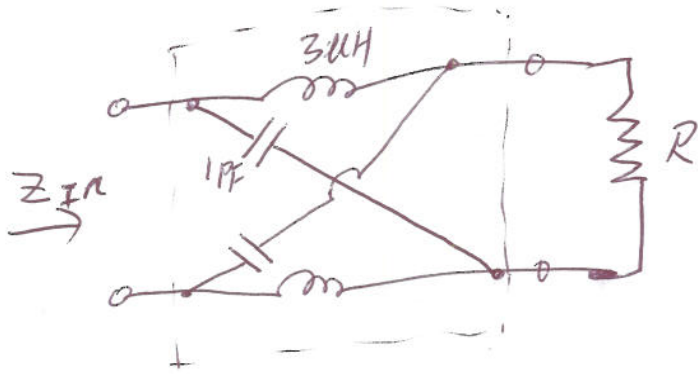


Midterm 2009 $\leftarrow \rightarrow$



$$Z_{11} = Z_{22} = \frac{1}{2} \left[\frac{1}{sC} + sL \right]$$

$$Z_{12} = Z_{21} = \frac{1}{2} \left[\frac{1}{sC} - sL \right]$$

From the material in class. in Page 65.

$$Z_{11} I_1 + Z_{12} I_2 = E \quad \dots \textcircled{1}$$

$$Z_{21} I_1 + Z_{22} I_2 + R I_2 = 0 \quad \dots \textcircled{2}$$

$$\textcircled{2} \Rightarrow I_2 = - \frac{Z_{21} I_1}{Z_{22} + R} \quad \dots \textcircled{3}$$

put $\textcircled{3}$ into $\textcircled{1}$

$$Z_{11} I_1 - \frac{Z_{12} Z_{21}}{Z_{22} + R} I_1 = E$$

$$\text{So } Z_{in} = \frac{E}{I_1} = Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22} + R} = \frac{Z_{22} + (\frac{L}{C})/R}{Z_{22} + R} \cdot R$$

as when $Z_{in} = R$, $\Rightarrow \frac{Z_{22} + (\frac{L}{C})/R}{Z_{22} + R} = 1$ which means $Z_{22} = \infty$

$$\frac{1}{sC} + sL \rightarrow \infty \Rightarrow s \rightarrow \infty \text{ or } s \rightarrow 0$$