
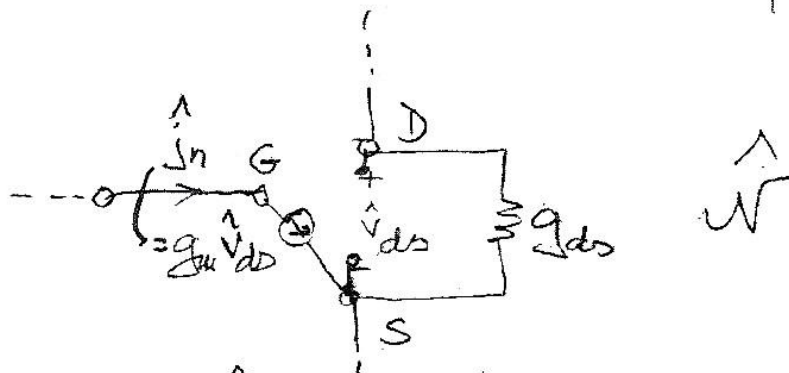


Noise analysis of MOSFET IC:

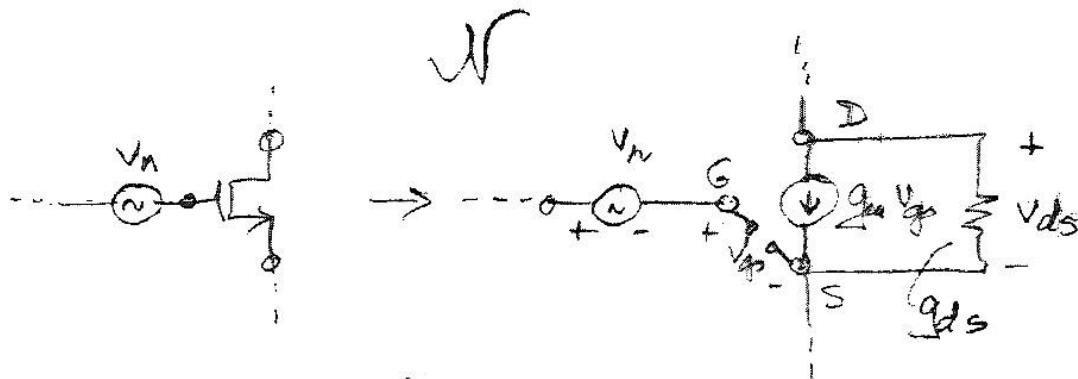


$$\frac{\partial V_{out}}{\partial v_n} = -\hat{i}_n = -g_m \hat{v}_{ds}$$

$$\bar{v}_{out,n}^2 \cong \sum_k \left(\frac{\partial v_{out}}{\partial v_{n_k}} \right)^2 \bar{v}_{n_k}^2 = \sum_k (g_{m_k} \hat{v}_{ds_k})^2 \bar{v}_{n_k}^2$$

Frequency resp. needed.

Sensitivity Calculations (DC) for Nonlinear Networks

Consider a nonlinear conductance:

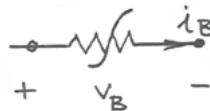

$$i \leftrightarrow j$$

where $i_B = i_B(V_B, P_1, P_2, \dots)$.




Here the P_i may be time (t), temperature (T), α , I_S , etc.

$$\text{Then } \Delta i_B \cong \frac{\partial i_B}{\partial V_B} \Delta V_B + \sum_k \frac{\partial i_B}{\partial P_k} \Delta P_k$$


The contribution to Δ is [diff. Tellegen theorem $\Delta = \sum_k (\hat{V}_k \Delta i_k - \hat{i}_k \Delta V_k) = 0$]

$$\hat{V}_B \Delta i_B - \hat{i}_B \Delta V_B = \left[\hat{V}_B \left(\frac{\partial i_B}{\partial V_B} \right) - \hat{i}_B \right] \Delta V_B + \hat{V}_B \sum_k \frac{\partial i_B}{\partial P_k} \Delta P_k \rightarrow \frac{\partial V_{out}}{\partial P_k} = \hat{v}_B \frac{\partial i_B}{\partial P_k}$$

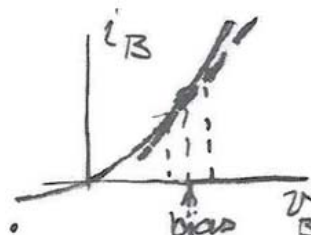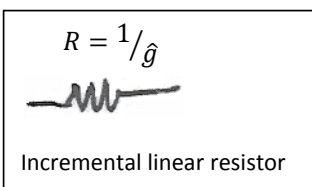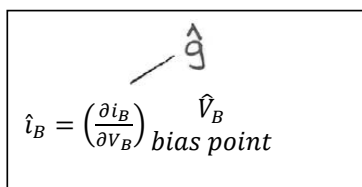The first term is eliminated if in \hat{N}



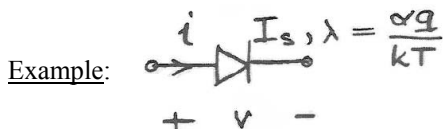This represents a linear time-variable conductance \hat{g} in \hat{N} . (Time-variable, since $\partial i_B / \partial V_B$ varies in N in time, even if the i_B - V_B characteristic is time-invariant, except of course for DC circuits.) Or for small signals!



n or α : production variable, 1~2.


$$i = I_S \left(e^{\left(\frac{\alpha q}{kT} \right) v} - 1 \right)$$

Hence, $\hat{g} = \frac{\partial i}{\partial v} = \lambda(i + I_S)$

$$P_1 = I_S, P_2 = T, P_3 = \alpha; \hat{g} = \frac{\partial i}{\partial v} = \frac{\alpha q I_S}{kT} e^{\frac{\alpha q v}{kT}} = \frac{\alpha q (i + I_S)}{kT} = \lambda(i + I_S)$$

The contribution to Δ is $\hat{v} \sum_k \frac{\partial i}{\partial P_k} \Delta P_k = \hat{v} \left[\frac{i}{I_S} \Delta I_S - \frac{\alpha q v (i + I_S)}{kT^2} \Delta T + \frac{q v (i + I_S)}{kT} \Delta \alpha \right] + \dots = \Delta v_o$

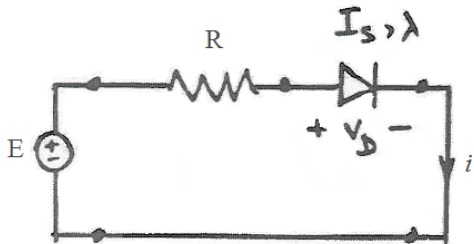
Example: Find the temperature sensitivity of i in the circuit:



Temp. sensor R is negligibly temp. sensitive

$$\Delta i = \frac{\partial i}{\partial T} \Delta T$$

Solution: now \hat{N} is

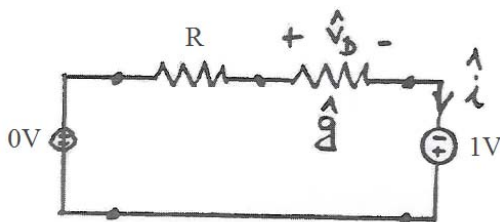

This gives $\frac{[\hat{i}_i^T]}{[\hat{j}_i^T]} \frac{[\Delta v_i]}{[\Delta v_i]} - \frac{[\hat{v}_D^T]}{[\hat{e}^T]} \frac{[\Delta i_V]}{[\Delta j_e]} = \Delta i$ on the LHS of the diff. Tellegen's Theorem.

If only T varies, the RHS is $\frac{\partial i}{\partial T} \Delta T = -\hat{v}_D \lambda \frac{\partial i / \partial T}{T} \Delta T$


where $\hat{v}_D = + \frac{1/\hat{g}}{R + 1/\hat{g}} = \frac{1}{R\hat{g} + 1} = \frac{1}{R\lambda(i + I_s) + 1}$, so that

$$\Delta i = \frac{\partial i}{\partial T} \Delta T = \frac{V_D \lambda (i + I_s)}{R\lambda(i + I_s) + 1} \frac{\Delta T}{T} = S_i^T \Delta T$$

Homework: find $\frac{\partial i}{\partial I_s}$ and $\frac{\partial i}{\partial R}$.

Let a nonlinear internal twoport (e.g., a transistor) inside N be described by

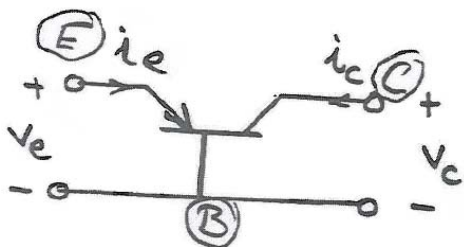
$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \mathbf{i} = \mathbf{h}(\mathbf{V}, P_1, P_2, \dots), \text{ where } \mathbf{h} \text{ is a non linear vector function of } \mathbf{V} \text{ and } P_i. \text{ For example,}$$



Nonlinear DC transistor model.

Using the Ebers-Moll equations (for pnp transistor) ←
$$\begin{bmatrix} i_e \\ i_c \end{bmatrix} = \begin{bmatrix} I_{es}(e^{\lambda v_e} - 1) - \alpha_r I_{cs}(e^{\lambda v_c} - 1) \\ -\alpha I_{es}(e^{\lambda v_e} - 1) + I_{cs}(e^{\lambda v_c} - 1) \end{bmatrix}$$


corresponding to the model:

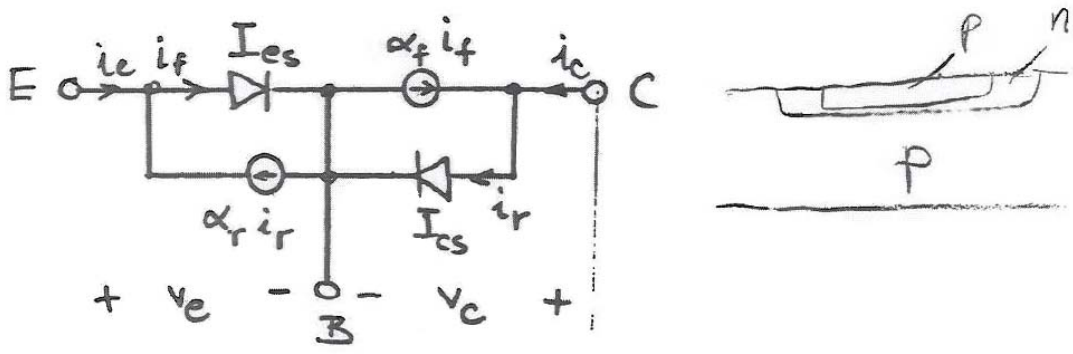

Here $\mathbf{i} \triangleq \begin{bmatrix} i_e \\ i_c \end{bmatrix}$, $\mathbf{V} \triangleq \begin{bmatrix} v_e \\ v_c \end{bmatrix}$, $P_1 = \lambda$, $P_2 = I_{es}$, $P_3 = \alpha_f$, etc., whichever can vary.

$$\mathbf{i} \triangleq \begin{bmatrix} i_e \\ i_c \end{bmatrix} \text{ As in the scalar case, } \Delta \mathbf{i} = \sum_{k=1}^2 \frac{\partial \mathbf{i}}{\partial v_k} \Delta v_k + \sum_i \frac{\partial \mathbf{i}}{\partial p_i} \Delta p_i$$

Defining the Jacobian matrix

$$[J_v] \triangleq \frac{\partial \mathbf{i}}{\partial \mathbf{v}} \triangleq \begin{bmatrix} \frac{\partial i_1}{\partial v_1} & \frac{\partial i_1}{\partial v_2} & \dots \\ \frac{\partial i_2}{\partial v_1} & \ddots & \vdots \\ \vdots & \dots & \frac{\partial i_k}{\partial v_l} \end{bmatrix} \quad \begin{array}{l} 2 \times 2 \text{ for transistor} \\ \textcircled{L} \end{array}$$


$$\begin{bmatrix} \frac{\partial i_1}{\partial v_1} & \frac{\partial i_1}{\partial v_2} \\ \frac{\partial i_2}{\partial v_1} & \frac{\partial i_2}{\partial v_2} \end{bmatrix} \begin{bmatrix} \Delta v_1 \\ \Delta v_2 \end{bmatrix}$$

$$\Delta \mathbf{i} = [J_v] \Delta \mathbf{v} + \sum_i \frac{\partial \mathbf{i}}{\partial p_i} \Delta p_i$$

Hence, in $\hat{\mathbf{v}}_B^T \Delta \mathbf{i}_B - \hat{\mathbf{i}}_B^T \Delta \mathbf{v}_B$, we get $\hat{\mathbf{v}}^T ([J_v] \Delta \mathbf{v} + \sum_i \frac{\partial \mathbf{i}}{\partial p_i} \Delta p_i) - \hat{\mathbf{i}}^T \Delta \mathbf{v}$

The factor of $\Delta \mathbf{v}$ (which is unknown and unwanted) is

$$\hat{\mathbf{v}}^T [J_v] - \hat{\mathbf{i}}^T \Rightarrow 0 \text{ for } \hat{\mathbf{i}} = [J_v^T] \hat{\mathbf{v}}.$$

$$\begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \end{bmatrix} = [J_v^T] \begin{bmatrix} \hat{v}_1 \\ \hat{v}_2 \end{bmatrix}$$

Hence, the nonlinear twoport in N becomes in \hat{N} a linear (time-varying) twoport given by a

$$[\hat{Y}_B] = [J_v^T]$$

$$\begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \end{bmatrix} = [J_v^T] \begin{bmatrix} \hat{v}_1 \\ \hat{v}_2 \end{bmatrix} = \begin{bmatrix} \frac{\partial i_1}{\partial v_1} & \frac{\partial i_2}{\partial v_1} \\ \frac{\partial i_1}{\partial v_2} & \frac{\partial i_2}{\partial v_2} \end{bmatrix} \begin{bmatrix} \hat{v}_1 \\ \hat{v}_2 \end{bmatrix}$$

This choice for \hat{N} leaves $\hat{v}^T \sum_i \frac{\partial i}{\partial p_i} \Delta p_i$ as contribution of the nonlinear twoport to Δ .

For the example on p. 337, if $i_1 = i_e, i_2 = i_c$


$$[U_v] = \begin{bmatrix} I_{es} \lambda e^{\lambda v_e} & -\alpha_r I_{cs} \lambda e^{\lambda v_c} \\ -\alpha_f I_{es} \lambda e^{\lambda v_e} & I_{cs} \lambda e^{\lambda v_c} \end{bmatrix}$$

$\frac{\partial i_e}{\partial v_e}$ $\frac{\partial i_c}{\partial v_c}$

So, denoting $I_{es} e^{\lambda v_e} = I'_e, I_{cs} e^{\lambda v_c} = I'_c$

$$[\hat{Y}_B] = \lambda \begin{bmatrix} I'_e & -\alpha_f I'_e \\ -\alpha_r I'_c & I'_c \end{bmatrix} \cdot \begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \end{bmatrix} = [\hat{Y}_B] \begin{bmatrix} \hat{v}_1 \\ \hat{v}_2 \end{bmatrix}$$

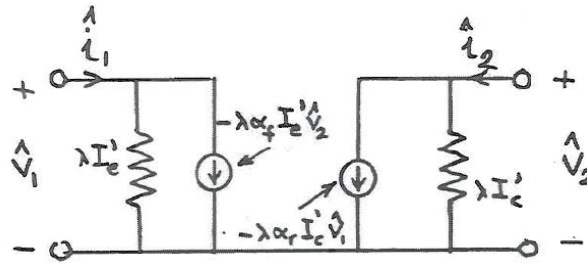This represents the linear (time-varying) twoport:



Since $I'_e = f_1(v_e)$ & $I'_c = f_2(v_c)$, the elements in this linear twoport vary with the voltages in N . Hence, N must be analyzed before \hat{N} ; then \hat{N} is easy to analyze, since it is linear.

The contribution to Δ is, with

$$\lambda = \frac{\alpha q}{kT}, \quad p_1 = I_{es}, \quad p_2 = \underbrace{\alpha}_{\text{prod. paramter}}, \quad p_3 = T, \quad p_4 = \alpha_r, \quad p_5 = I_{cs}, \quad p_6 = \alpha_f:$$

$$\begin{bmatrix} \hat{v}_1 \\ \hat{v}_2 \end{bmatrix} \begin{bmatrix} \sum_{l=1}^6 \frac{\partial i_e}{\partial p_l} \Delta p_l \\ \sum_{l=1}^6 \frac{\partial i_c}{\partial p_l} \Delta p_l \end{bmatrix} = \hat{v}_1 \sum_{l=1}^6 \frac{\partial i_e}{\partial p_l} \Delta p_l + \hat{v}_2 \sum_{l=1}^6 \frac{\partial i_c}{\partial p_l} \Delta p_l$$

Homework: calculate the terms under the summation signs.

Sensitivity Analysis of Dynamic Linear Active Circuits in the Frequency Domain

$$v(t), j(t) \rightarrow V(\omega), J(\omega)$$

$$v(t) = V_v \cos(\omega t + \phi) \rightarrow V e^{j\phi}, \quad V = V_v e^{j\phi}$$