


ECE-627 MIDTERM

May 22, 2001

Open Book

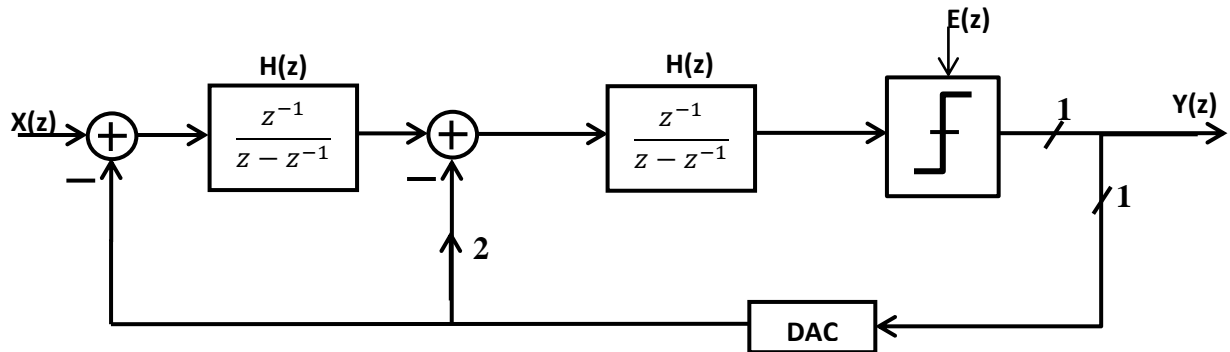Problem-1: For the $\Delta\Sigma$ ADC shown below:

- Find the NTF and STF.
- Show the zeros and poles of NTF in the z-plane and draw the frequency response of the NTF.
- Do you expect the loop to be stable? Why or Why not?



Part (a)

$$Y = E + H * [H * (X - Y) - 2Y]$$



$$\{H^2 + 2H + 1\} Y = (H + 1)^2 Y = H^2 X + E$$

$$H = \frac{z^{-2}}{1 - z^{-2}}; \quad (H + 1)^2 = \frac{1}{(1 - z^{-2})^2}$$

$$Y = z^{-4} X + (1 - z^{-2})^2 E$$

$$\text{So; STF} = z^{-4} \text{ and NTF} = (1 - z^{-2})^2$$

Part (b)

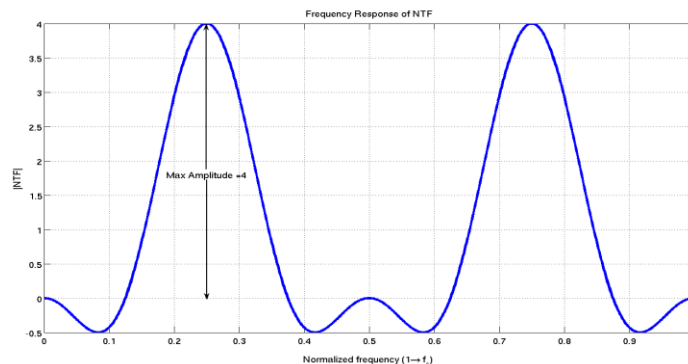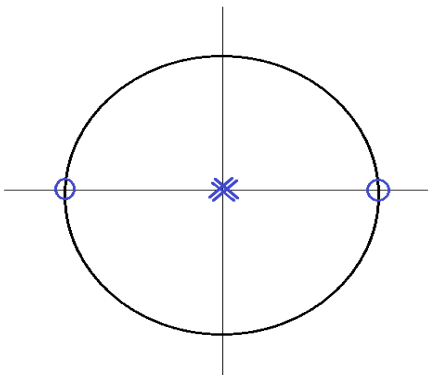Poles(4) at $z=0$; zeros (2) at $z=1$ and $z=-1$ 

Pole zero plot and Frequency Response


Part(c)

Yes, Since it can be obtained by mapping z with z^2 . Which form a stable 2nd-order loop.

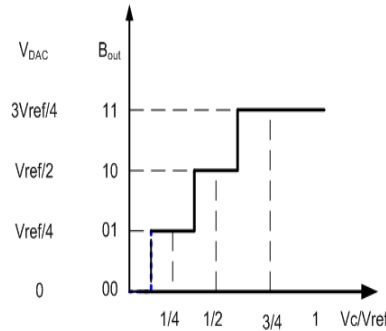Problem-2: The STF of a $\Delta\Sigma$ ADC is z^{-2} ; its NTF is

$$H_N(z) = \frac{(1 - z^{-1})^2}{1 - 0.1z^{-1}}$$

It uses a 2-bit internal quantizer, with the characteristics shown below, and $V_{ref} = 1V$. Assuming a dc input, what is the input voltage range which guarantees even in the worst case that the quantizer is not overloaded ?



Solution:

Suppose the signal appearing at the input port of the 2-bit quantizer is $v_c(n)$,
Then

$$\begin{aligned} V_c &= Y(z) - E(z) \\ &= X \text{ STF} + E \text{ [NTF-1]} \end{aligned}$$

So

$$\begin{aligned} V_c(z)(1 - 0.1z^{-1}) &= X(z) z^{-2}(1 - 0.1z^{-1}) + E(z)[(1 - z^{-1})^2 - (1 - 0.1z^{-1})] \\ &= X(z) z^{-2}(1 - 0.1z^{-1}) + E(z)(z^{-2} - 1.9z^{-1}) \end{aligned}$$

Finally we get,

$$V_c(z)(1 - 0.1z^{-1}) = X(z) z^{-2}(1 - 0.1z^{-1}) + E(z)(z^{-2} - 1.9z^{-1}) + V_c(z)0.1z^{-1}$$

in time domain

$$\begin{aligned} v_c(n) &= 0.9x + e(n-2) - 1.9e(n-1) + 0.1v_c(n-1) \\ &= 0.9x + e(n-2) - 2e(n-1) + 0.1y(n-1) \end{aligned}$$

to ensure the quantizer is not overloaded,

$$\begin{aligned} -\frac{V_{LSB}}{2} &\leq v_c(n) \leq V_{ref} - \frac{V_{LSB}}{2} \\ -0.125 &\leq v_c(n) \leq 0.875 \end{aligned}$$

and keep in mind that

$$\begin{aligned} -\frac{V_{LSB}}{2} &\leq e(n) \leq \frac{V_{LSB}}{2} \\ -0.125 &\leq e(n) \leq 0.125 \end{aligned}$$

that means in the worst case

$$\begin{aligned} 0.9x &\leq v_c(n)|_{max} - e(n-2)|_{max} + 1.9 e(n-1)|_{min} - 0.1 v_c(n-1)|_{max} \\ &= 0.875 - 0.125 + 1.9x(-0.125) - 0.1x0.875 \\ &= 0.425 \end{aligned}$$

and

$$\begin{aligned} 0.9x &\leq v_c(n)|_{max} - e(n-2)|_{max} + 1.9 e(n-1)|_{min} - 0.1 v_c(n-1)|_{max} \\ &= 0.125 - (-0.125) + 1.9x(-0.125) - 0.1x(-0.125) \\ &= 0.25 \end{aligned}$$

Eventually we get

$$0.2778 \leq x \leq 0.4722$$