

# Homework 1

ECE 627

Due April,26, 2024

Consider the 4-bit binary-weighted resistor DAC shown below.

1. Find  $R_F$  such that  $V_{out}$  can change from 0 to  $V_{ref} - V_{LSB}$ .
2. If the error in resistor values in the DAC is  $\pm 1\%$ , considering worst scenario, calculate maximum value of DNL and INL in terms of ideal LSB unit.
3. [Optional] What is the largest value of such error in the resistor values to keep the max INL below  $V_{LSB}/2$ ?  
[Note: Operational amplifier can be considered ideal]

