


ECE 627

Spring 2012

Final Examination


June 11, 2012, 9:30 – 11:20 am

1. In the multiplying DAC shown, the output signal v_o is proportional to v_{in} and to $|D|$, where $|D|$ is the value of the digital input word, $D = d_1d_2d_3d_4$.

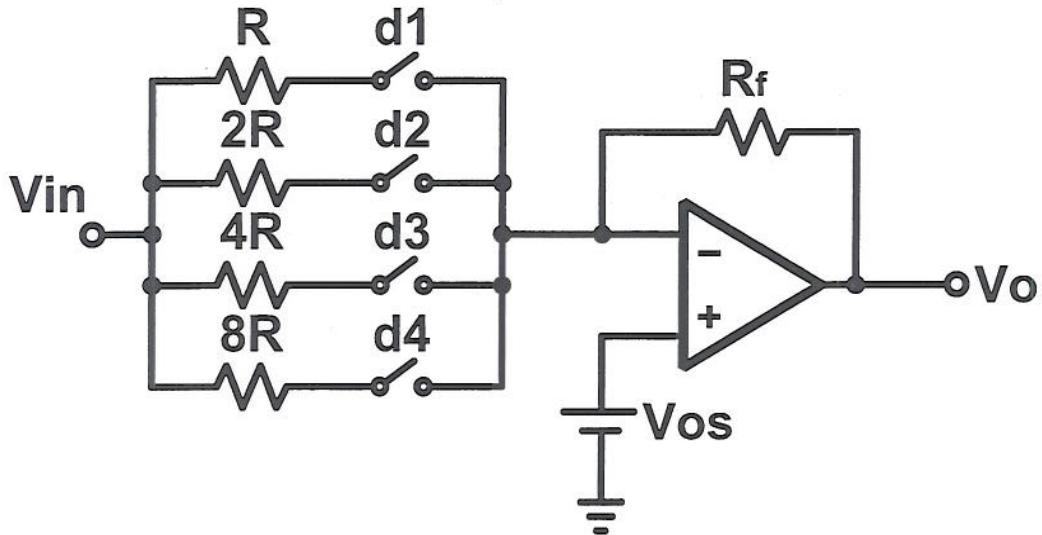

- Find the value of R_f such that for $V_{os}=0$ and $D=1111$, $v_o=-v_{in}$.
- What is v_o if $V_{os}=0$ and $D=0010$?
- How does a nonzero V_{os} affect v_o ?
- How large can $|V_{os}|$ be for a given v_{in} if the resulting error in v_o should be less than $\pm 1/2$ LSB?


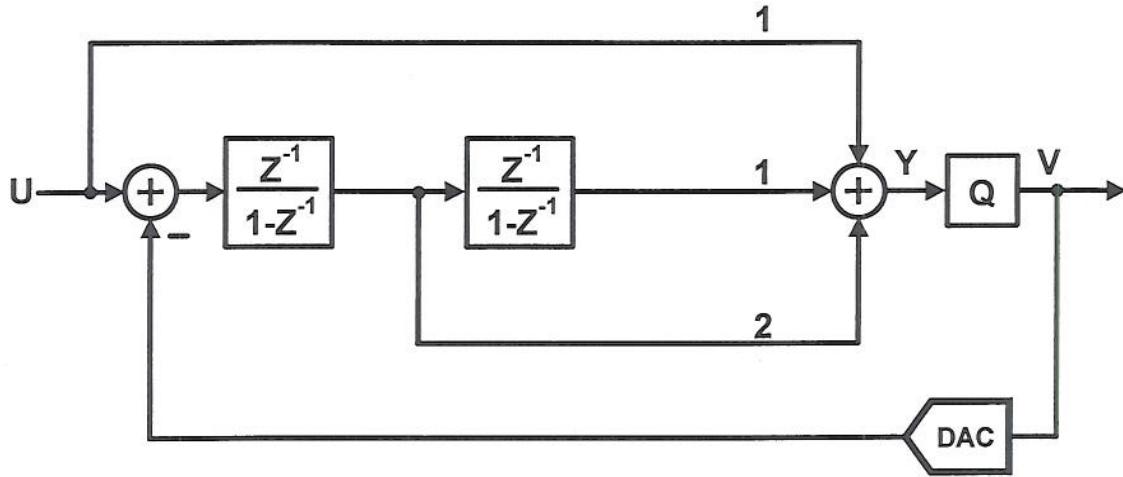
2. The modulator shown below has a 9-level quantizer, operating between ground and a reference voltage $V_{ref} = 1.3$ V. What is the largest peak-to-peak value of a sine-wave input voltage u for which the quantizer is not overloaded? Why?



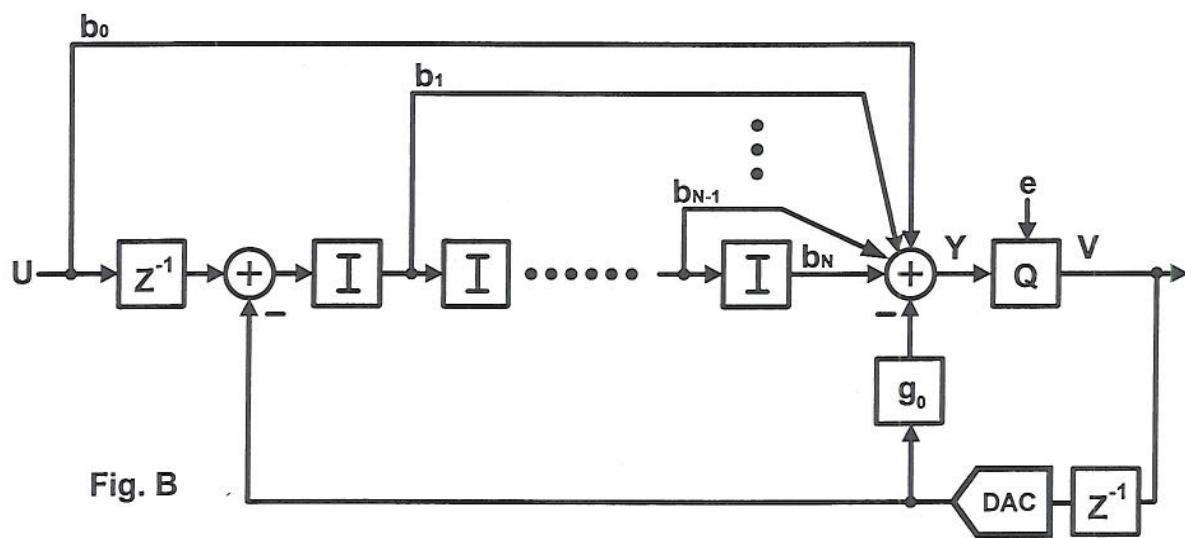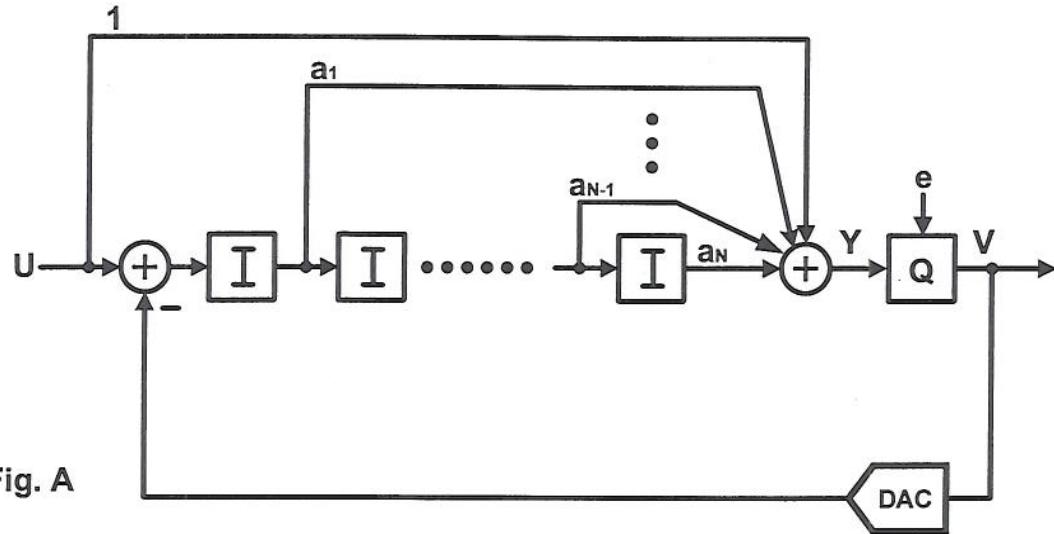3. The circuit of the $\Delta\Sigma$ modulator MODA shown in Fig. A is redesigned as illustrated in Fig. B, to allow more time for quantization. The integrator transfer function is $I = 1/(z - 1)$.

- What are the NTF and STF for MODA?
- Given the a_i , $i = 1, 2, \dots, N$, what should be the values of the parameters $b_0, b_1, \dots, b_N, g_0$ of MODB if the NTF is to be preserved?
- What is the STF for MODB?
- How should the transfer function of the feed-forward path from the input u and the quantizer in MODB be modified to make the STF the same as that of MODA?

Note: It is better to work in terms of I , not z , when solving this problem!



$$1a. \text{ For } D = 1111, R_{in}^{-1} = \frac{1}{R} \left[1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right]$$

$$R_f \stackrel{!}{=} R_{1111} = \frac{8R}{15} \approx 0.533R \quad = \frac{15}{8}R$$

$$b, R_{0010} = 4R, \text{ so}$$

$$V_o = -\frac{R_f}{R_{0010}} = -\frac{2}{15} V_{in} \approx -0.133 V_{in}$$

c. From KCL, infinite gain opamp,

$$(V_{in} - V_{os})/R_{in} = (V_{os} - V_o)/R_f$$

$$V_{os}(G_f + G_m) = G_m V_{in} + G_f V_o$$

$$V_o = \left(1 + \frac{R_f}{R_{in}}\right) V_{os} - \frac{R_f}{R_{in}} V_{in}$$

Largest effect for $R_{in} = R_{1111}$:

$$V_o = -V_{in} + 2V_{os}$$

$$d, V_{LSB} = V_{in} \frac{R_f}{R_{0010}} = V_{in} \frac{R_f}{8R} = \frac{V_{in}}{15}$$

$$|2V_{os}| \stackrel{!}{=} \frac{|V_{in}|}{30},$$

$$|V_{os}| \leq \frac{|V_{in}|}{60}$$

$$2. \quad V = E + u + I(2+I)(u-V)$$

$$V = u + E / [1+I]^2, \quad I \triangleq \frac{z^{-1}}{1-z^{-1}}$$


$$1+I = 1/(1-z^{-1}), \quad [1+I]^{-2} = 1-2z^{-1}+z^{-2}$$

$$v(n) = u(n) + e(n) - 2e(n-1) + e(n-2)$$

$$y(n) = u(n) - 2e(n-1) + e(n-2)$$

$$|y|_{\max} = |u|_{\max} \pm 3|e|_{\max} = |u|_{\max} \pm \frac{3N_{LSB}}{2}$$

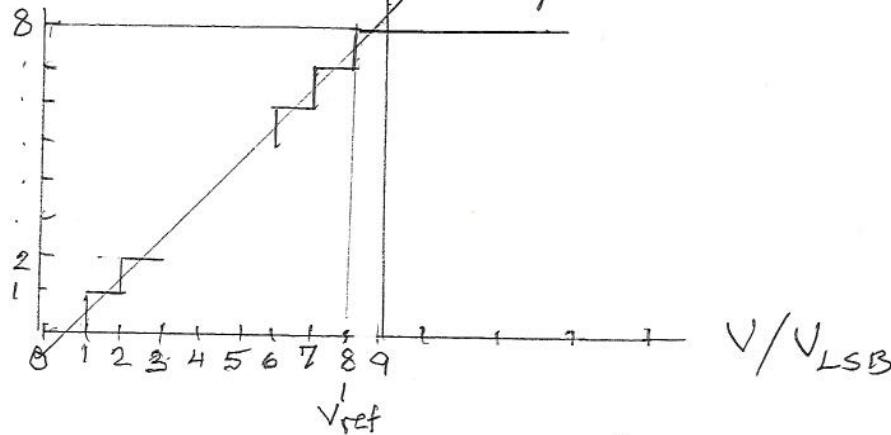Overload limits of Q: 0 - $N_{\text{level}} V_{LSB}$



So the peak-to-peak amplitude of $u(n)$ for no overload is

$$u_{P-P, \max} = 9V_{LSB} - 2 \times \frac{3}{2} V_{LSB} = 6V_{LSB} = 6 \frac{1.3}{8}$$

$$u_{P-P, \max} = \frac{3.9}{4} = 0.975 \text{ V}$$

(3.) Loop filter for MODA

$$H_A(z) = \sum_{i=1}^N a_i I^i ; \text{ for MODB, } a_i \rightarrow b_i$$


(a.) MODA

$$V = E + U + H_A(U - V)$$

$$V = U + E / (1 + H_A)$$

$$STF = 1, NTF = (1 + H_A)^{-1}$$

(b.)

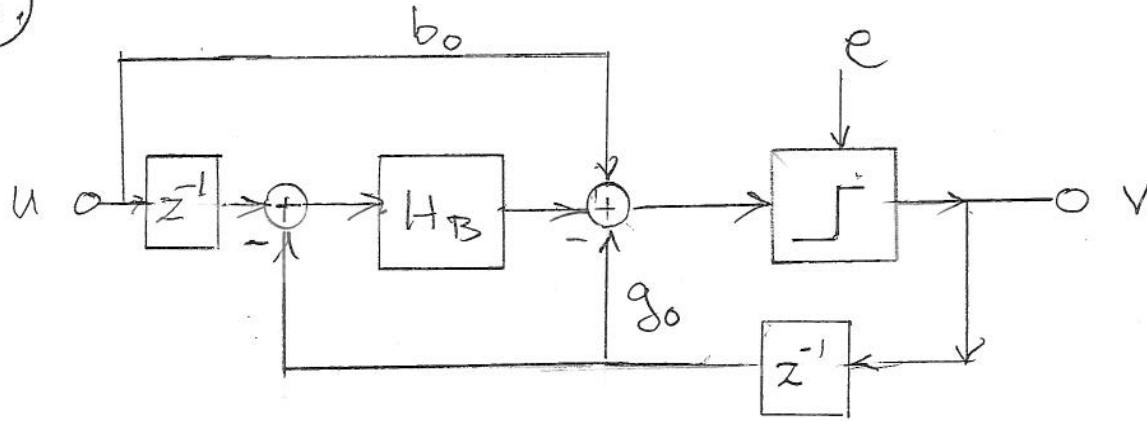

$$V = E + b_0 U - g_0 z^{-1} V + H_B(U - V)z^{-1}$$

$$V [1 + (g_0 + H_B)z^{-1}] = E + (b_0 + z^{-1}H_B)U$$

$$NTF_B = [1 + (g_0 + H_B)z^{-1}]^{-1} = (1 + H_A)^{-1}$$

$$g_0 + \sum_{i=1}^N b_i I^i \stackrel{!}{=} \sum_{i=1}^N a_i I^i$$

$$I = \frac{z^{-1}}{1 - z^{-1}} \rightarrow z = 1 + 1/I$$

$$g_0 + \sum_{i=1}^N b_i I^i = (1 + 1/I) \sum_{i=1}^N a_i I^i$$

$$g_0 = a_1$$

$$b_i = a_i + a_{i+1}, \quad i = 1, 2, \dots, N-1$$

$$b_N = a_N$$

c.) $STF_B = \frac{b_0 + H_B z^{-1}}{1 + (g_0 + H_B) z^{-1}} = \frac{b_0 + H_B z^{-1}}{1 + H_A}$

$$z^{-1} H_B = H_A - g_0 z^{-1} = H_A - a_1 z^{-1}$$

$$STF_B = \frac{b_0 - a_1 z^{-1} + H_A}{1 + H_A}$$

d.) To make $STF_B = STF_A = 1$, replace b_0 by an $F(z)$ such that

$$F(z) - a_1 z^{-1} = 1$$

$$F(z) = 1 + a_1 z^{-1}$$