

# FINAL EXAMINATION


ECE 627

June 11, 2010, 9:30 – 11:20 am


STAG 109

Open book, open notes

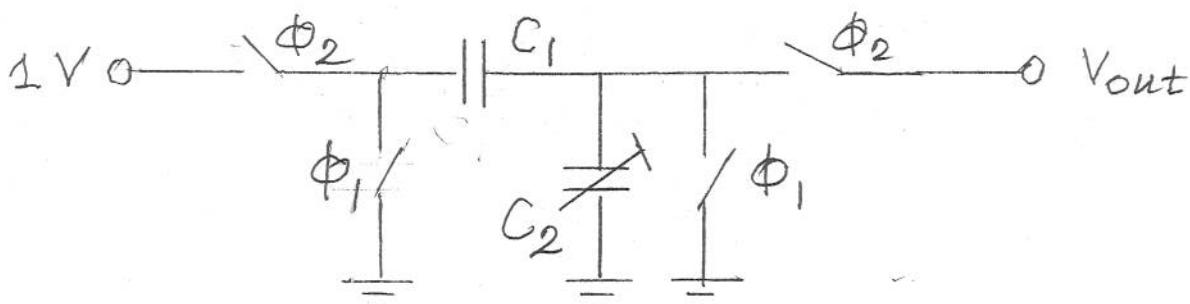
1. In the DAC shown,  $C_2$  is controlled by the digital input signal. Both capacitors have uncorrelated random errors, at most 0.1 % in magnitude.
  - a. Find the largest possible error in  $v_{out}$  as a function of  $C_1/C_2$ ;
  - b. For what value of  $C_1/C_2$  will the error in  $v_{out}$  reach its maximum? How large is this error?



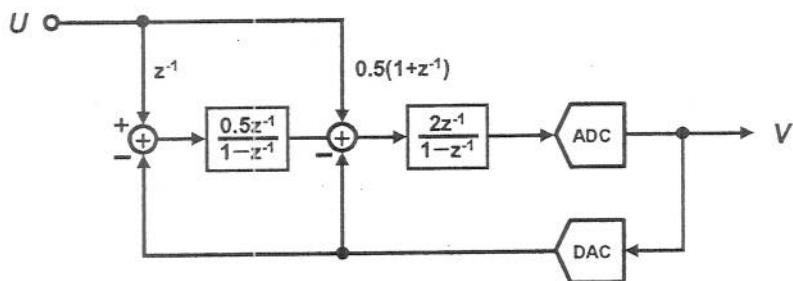2. In the delta-sigma ADC shown, the quantizer has 17 levels. The reference voltage is 2 V.
  - a. Find the STF and NTF of the ADC;
  - b. How large can the output of the first integrator be?
  - c. Estimate the largest input voltage for guaranteed absolute stability of the loop.



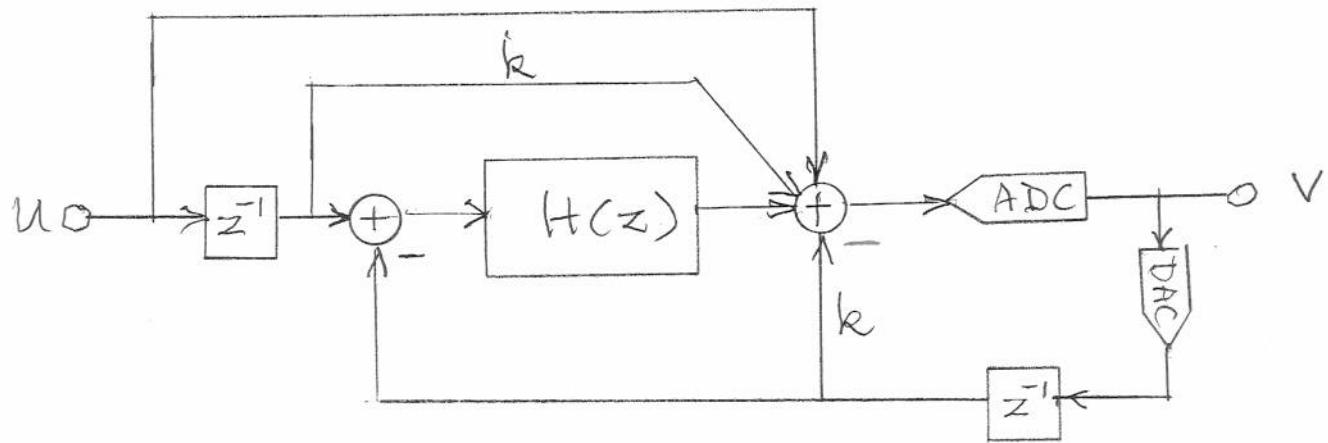3. Find the STF of the modulator shown below.



$$1. \text{ } \text{ } V_{\text{out, ideal}} = \frac{1}{1 + \frac{C_2}{C_1}}$$

assuming  $C_1$  has a random error of  $\alpha$   
 $C_2$  has a random error of  $\beta$

$$V_{\text{out, real}} = \frac{1}{1 + \frac{C_2(1+\beta)}{C_1(1+\alpha)}} = \frac{1}{1 + \theta \frac{C_2}{C_1}}$$

$$\text{here } \theta = \frac{1+\beta}{1+\alpha}$$

$$\text{so } V_{\text{out, error}} = V_{\text{out, ideal}} - V_{\text{out, real}}$$

$$\begin{aligned} &= \frac{1}{1 + \frac{C_2}{C_1}} - \frac{1}{1 + \theta \frac{C_2}{C_1}} = \frac{(1-\theta) \frac{C_2}{C_1}}{\left(1 + \frac{C_2}{C_1}\right) \left(1 + \theta \frac{C_2}{C_1}\right)} \\ &\approx \frac{(\theta-1) \frac{C_2}{C_1}}{\left(1 + \frac{C_2}{C_1}\right)^2} \end{aligned}$$

$$\text{if } |\alpha| < 0.001 \quad |\beta| < 0.001$$

$$\Rightarrow \frac{0.999}{1.001} < \theta < \frac{1.001}{0.999} \Rightarrow -\frac{0.002}{1.001} < \theta-1 < \frac{0.002}{0.999}$$

So the largest possible voltage error is

$$\frac{0.002}{0.999} \frac{\frac{C_2}{C_1}}{1 + \left(\frac{C_2}{C_1}\right)^2} = \frac{0.002}{0.999} \frac{\frac{C_1}{C_2}}{1 + \left(\frac{C_1}{C_2}\right)^2}$$

$$2) \frac{0.002}{0.999} \frac{\frac{C_1}{C_2}}{1 + \left(\frac{C_1}{C_2}\right)^2} = \frac{0.002}{0.999} \frac{1}{\frac{C_1}{C_2} + \frac{C_2}{C_1} + 2} \leq \frac{0.002}{0.999} \cdot \frac{1}{4}$$

when  $\frac{C_1}{C_2} = 1 \approx 5 \times 10^{-4} \checkmark$

$$V_r = \frac{C_1}{C_1 + C_2} V_0 = V_r \frac{C_1}{C_1 + C_2}, \quad \frac{\partial V_0}{\partial C_1} = V_r \frac{\Delta C_2}{C_t^2}, \quad \frac{\partial V_0}{\partial C_2} = V_r \frac{\Delta C_1}{C_t^2},$$

$$\Delta V_0 = \frac{V_r}{C_t^2} (C_1 \Delta C_2 + C_2 \Delta C_1) = V_r \frac{C_1 C_2}{C_t^2} \left( \frac{\Delta C_1}{C_1} - \frac{\Delta C_2}{C_2} \right)$$

$$\frac{\Delta V_0}{V_r} = \frac{C_1 C_2}{C_t^2} \left( \frac{\Delta C_1}{C_1} - \frac{\Delta C_2}{C_2} \right), \quad 1/a = \frac{(C_1 + C_2)}{C_1 C_2} = \left( \frac{C_1}{C_2} + \frac{C_2}{C_1} \right)^2 = (r + 1/r)^2$$

$$\frac{\partial a}{\partial r} = -2(r + 1/r)(1/r^2) \rightarrow 0, \quad r = 1/r = \pm 1, \quad C_1 = C_2$$

$$V_0 = V_r/2, \quad a = 1/4, \quad \left| \frac{\Delta V_0}{V_r} \right|_{max} = \frac{1}{4} \left( \left| \frac{\Delta C_1}{C_1} \right|_{max} + \left| \frac{\Delta C_2}{C_2} \right|_{max} \right) \rightarrow \frac{1}{2} \left| \frac{\Delta C_1}{C_1} \right|_{max} = \frac{10^{-3}}{2}.$$

$$2. \quad \left\{ (Uz^{-1} - V) \frac{0.5z^{-1}}{1-z^{-1}} + U \cdot 0.5(1+z^{-1}) - V \right\} \frac{2z^{-1}}{1-z^{-1}} + E = V$$

$$\Rightarrow V = Uz^{-1} + E(1-z^{-1})^2$$

$$STF = z^{-1} \quad NTF = (1-z^{-1})^2$$

$$3. \quad v_1 = -\frac{1}{2} z^{-1}(1-z^{-1})E \quad LSB = \frac{2}{16} V$$

$$= -\frac{1}{2} z^{-1}E + \frac{1}{2} z^{-2}E \quad |E| < \frac{1}{2} LSB = \frac{1}{16} V$$

$$So \quad v_{1 \max} = \frac{1}{16} V$$


$$3. \quad v_2 = z^{-1} \cdot U + E(z^{-2} - 2z^{-1})$$

$$\text{because } v_2 < 2 + \frac{1}{2} LSB = \frac{33}{16}$$

$$|E(z^{-2} - 2z^{-1})| < \frac{3}{16}$$

$$\therefore U_{\max} = \frac{30}{16} = \frac{15}{8} V$$

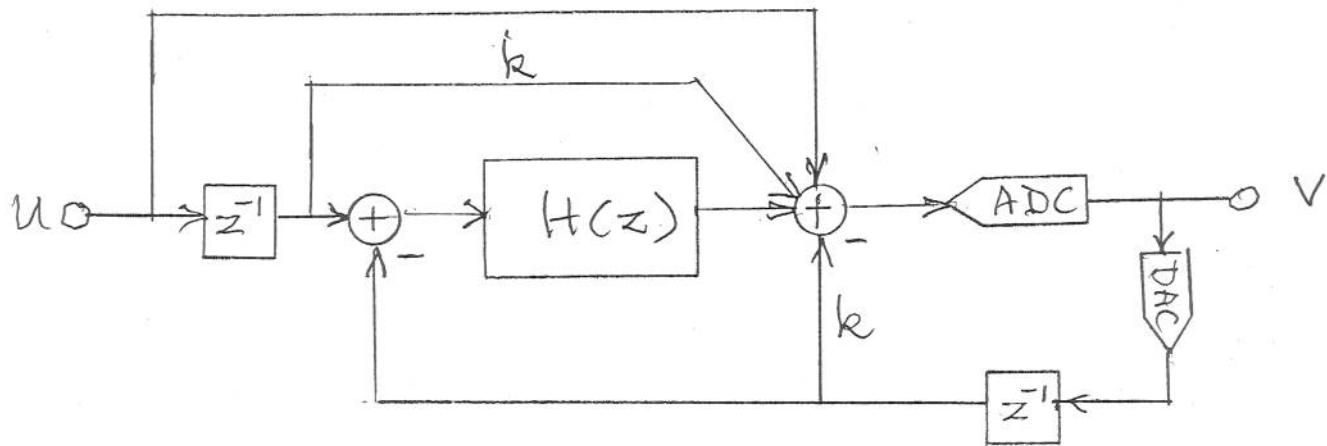3. Find the STF of the modulator shown below.



$$V|_{E=0} = -kz^{-1}V_o + (1+z^{-1}k)u + Hz^{-1}(u-V_o)$$

$$V_o(1+kz^{-1}+Hz^{-1}) = u(1+kz^{-1}+Hz^{-1})$$

$$STF = \frac{V_o}{u} = 1$$