

## MIDTERM EXAMINATION


May 11, 2012

Open book

In the segmented  $2N$ -bit DAC circuit shown, the value of the bridge capacitor was chosen as  $C_0$  (the unit capacitor of the array), instead of the fractional capacitance derived in class. This allows easier layout, but also changes the signals in the array, and thus introduces an error into the operation of the DAC. This problem deals with this error.


Initially, the top and bottom plates of all capacitors are at ground potential.

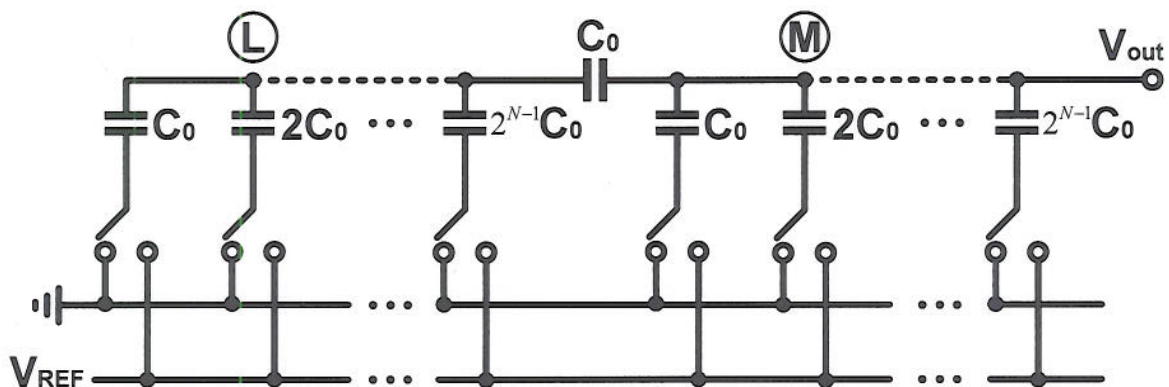1. Find the capacitance  $C_L$  between node **L** and ground, and the capacitance  $C_M$  between node **M** and ground.
2. Find the node voltages  $V_L$  and  $V_M$  when the bottom plate of the capacitor  $2C_0$  in the left-side (LSB) array is switched from ground to  $V_{REF}$ .
3. Repeat the calculation with the bottom node of the MSB array capacitor  $2C_0$  switched to  $V_{REF}$ .
4. How significant is the voltage error in  $V_L$  and  $V_M$  due to the change in the value of the bridge capacitor to  $C_0$ ?




1) Node (L) can be equivalently shown

as

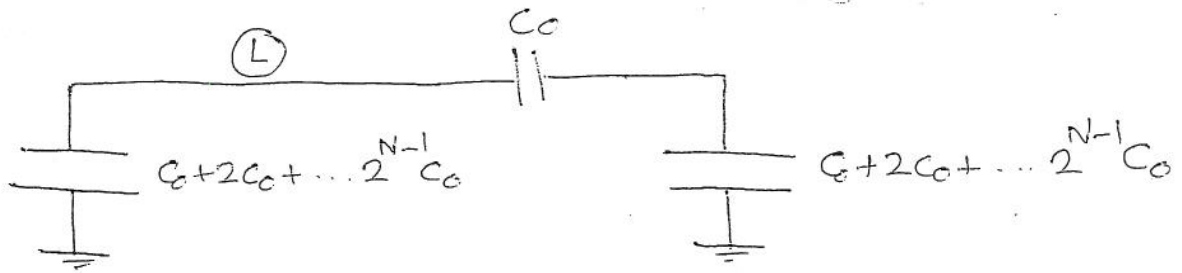
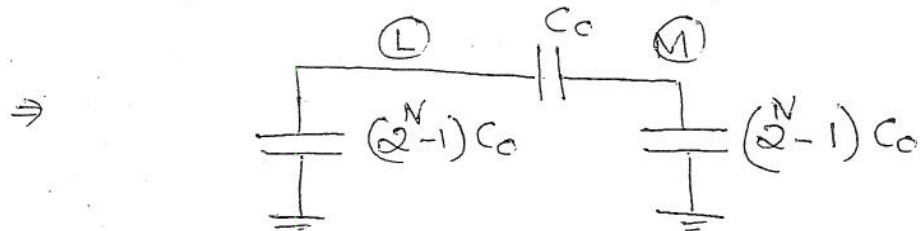
$$\text{Now } C_0 + 2C_0 + \dots + 2^{N-1}C_0 = (2^N - 1)C_0$$



$$\Rightarrow (2^N - 1)C_0 + C_0 \parallel (2^N - 1)C_0$$

Parallel operation  $\frac{C_A C_B}{C_A + C_B}$

$$\Rightarrow C_L = (2^N - 1)C_0 + \frac{C_0 \times (2^N - 1)C_0}{C_0 + 2^N C_0 - C_0}$$

But series connection

$$C_L = (2^N - 1)C_0 + \frac{(2^N - 1)C_0}{2^N}$$


$$\Rightarrow C_L = 2^N C_0 - C_0 + C_0 - 2^{-N} C_0$$

$$\Rightarrow C_L = (2^N - 2^{-N})C_0$$

By symmetry

$$C_M = C_L = (2^N - 2^{-N})C_0$$

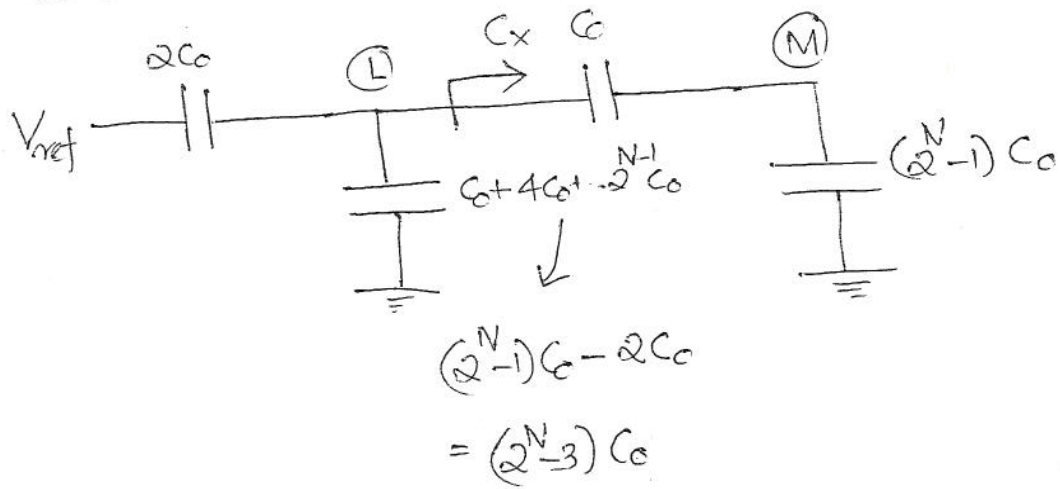2) Equivalent circuit when bottom plate of capacitor  $2C_0$  is switched to  $V_{ref}$




$$V_L = \frac{2C_0}{2C_0 + C_x + (2^N - 3)C_0} \cdot V_{ref} = V_{ref} \times \frac{2C_0}{(2^N - 1)C_0 + C_x}$$

$$C_x = \frac{C_0 \times (2^N - 1)C_0}{C_0 + (2^N - 1)C_0} = (1 - 2^{-N})C_0$$

$$\Rightarrow V_L = V_{ref} \times \frac{2C_0}{(2^N - 1)C_0 + (1 - 2^{-N})C_0}$$

$$= V_{ref} \times \frac{2C_0}{(2^N - 2^{-N})C_0}$$
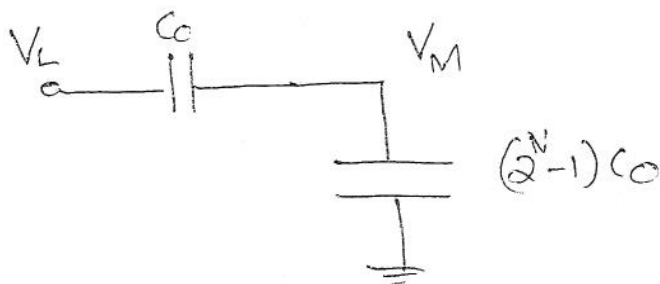
$$\Rightarrow V_L = V_{ref} \times \frac{2}{2^N - 2^{-N}}$$



$$V_M = V_L \times \frac{C_0}{C_0 + (2^N - 1)C_0}$$


$$\Rightarrow V_M = \frac{V_L}{2^N}$$

So

$$V_L = V_{ref} * \frac{2}{2^N - 2^{-N}}$$

$$V_M = V_{ref} * \frac{2}{2^{2N} - 1}$$

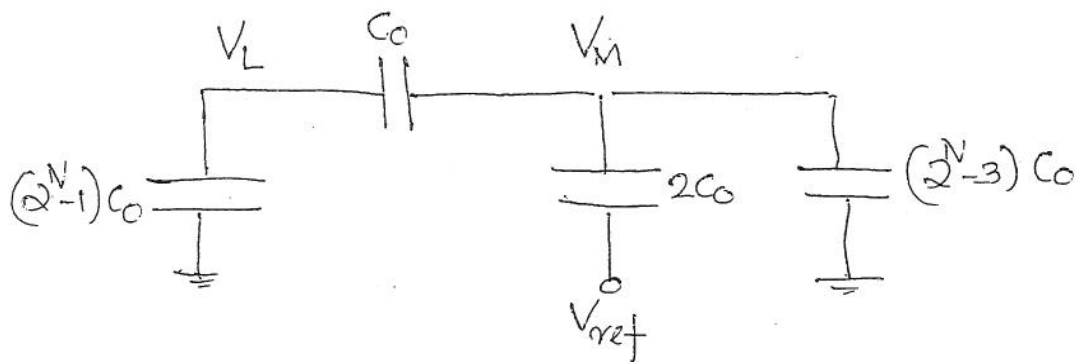3) When  $2C_0$  of MSB array is switched to  $V_{REF}$



This is exactly symmetrical to the previous case except that  $V_L$  and  $V_M$  are interchanged

$$V_M = V_{ref} * \frac{2}{2^N - 2^{-N}}$$

$$V_L = V_{ref} * \frac{2}{2^{2N} - 1}$$

4) If the bridge capacitor were exact value [the fractional one], we would ~~expect~~ expect  $V_L$  and  $V_M$  in case ② to be

$$V_L' = V_{ref} \cdot \frac{2}{2^N}$$

$$\text{LSB} = \frac{V_{ref}}{2^{2N}}$$

$$= \frac{V_{ref}}{2^{N-1}}$$

$$\text{and } V_{out}' = V_M = V_{ref} \cdot \frac{2}{2^{2N}} \quad \left[ \text{ie } 2 \text{ LSB} \right]$$

But since we had put bridge capacitor as  $C_0$

$$V_{out} = V_M = V_{ref} \times \frac{2}{2^{2N} - 1}$$

$$= \frac{V_{ref} \cdot 2}{2^{2N} [1 - 2^{-2N}]}$$

$$V_{out} \approx V_{out}' [1 + 2^{-2N}]$$

assuming  $2^{2N} \gg 1$

So error  $\frac{\Delta V_{out}'}{V_{out}'} = 2^{-2N}$  which is negligible for

large value of  $N$ .

For 12 bit DAC, this error = 0.024%.

$$\text{For } V_L = V_{\text{ref}} \cdot \frac{2}{2^N - 2^{-N}}$$

$$V_L' = V_{\text{ref}} \cdot \frac{2}{2^N}$$

$$V_L = V_{\text{ref}} \cdot \frac{2^{N+1}}{2^{2N} - 1}$$

$$\approx \frac{V_{\text{ref}} \cdot 2^{N+1}}{2^{2N}} \cdot (1 + 2^{-2N})$$

$$\approx V_L' (1 + 2^{-2N})$$

⇒ Error remains the same and of small value.